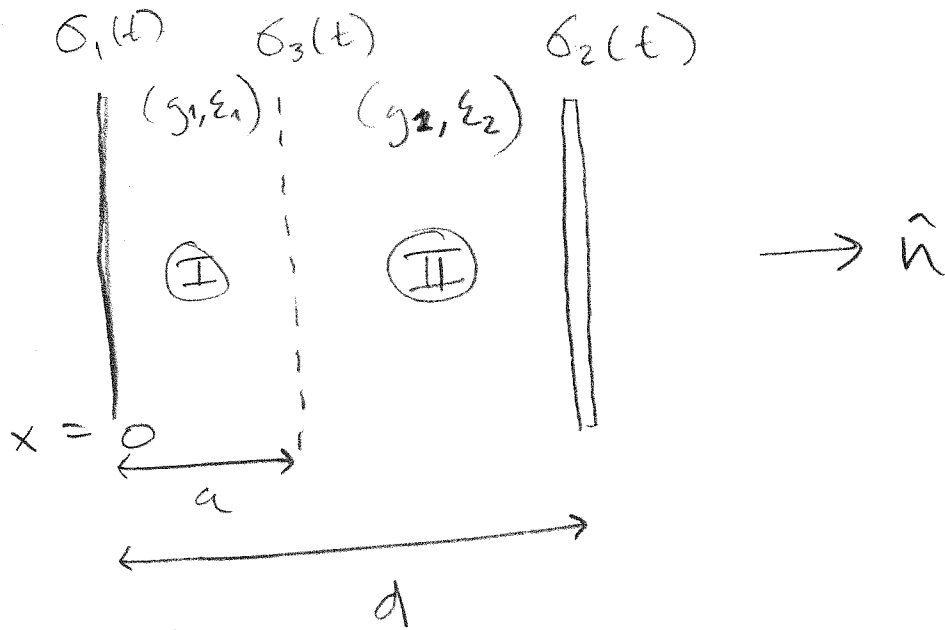


Ejercicio 1

IN.CO.



$$\rightarrow \vec{J}_1 \cdot \hat{n} \Big|_{x=0} = -\dot{\sigma}_1$$

$$\vec{J}_2 \cdot \hat{n} \Big|_{x=d} = \dot{\sigma}_2$$

$$\vec{J}_1 \cdot \hat{n} \Big|_{x=a} - \vec{J}_2 \cdot \hat{n} \Big|_{x=a} = \dot{\sigma}_3 = -(\dot{\sigma}_1 + \dot{\sigma}_2)$$

$$\rightarrow \vec{E}_1 = \frac{\sigma_1}{\epsilon_1} \hat{n}$$

$$\vec{E}_2 = -\frac{\sigma_2}{\epsilon_2} \hat{n}$$

$$\boxed{\begin{aligned} \sigma_3(t) &= -(\sigma_1(t) + \sigma_2(t)) \\ \sigma_3(t=0) &= -(\sigma_1(t=0) + \sigma_2(t=0)) \end{aligned}}$$

$$\dot{\sigma}_1 = -\frac{g}{\epsilon_1} \sigma_1 \Rightarrow \sigma_1(t) = \sigma_{01} e^{-\frac{g}{\epsilon_1} t}$$

$$\dot{\sigma}_2 = -\frac{g}{\epsilon_2} \sigma_2 \Rightarrow \sigma_2(t) = \sigma_{02} e^{-\frac{g}{\epsilon_2} t}$$

$$\Rightarrow \delta_3(t) = -\delta_{01} e^{-\frac{\sigma_1}{\epsilon_1} t} - \delta_{02} e^{-\frac{\sigma_2}{\epsilon_2} t}$$

$$b) \phi_I(x, t) = A_I x + B_I$$

$$\phi_{II}(x, t) = A_{II} x + B_{II}$$

$$\vec{E}_I = -\frac{\partial \phi_I}{\partial x} \hat{n} = -A_I \hat{n} = \frac{\sigma_1}{\epsilon_1} \hat{n}$$

$$A_I = -\frac{\sigma_1}{\epsilon_1}$$

$$A_{II} = \frac{\sigma_2}{\epsilon_2}$$

Continuidad $\phi_I(x=a) = \phi_{II}(x=a)$

$$A_I a + \underbrace{B_I}_0 = A_{II} a + B_{II}$$


$$B_{II} = (A_I - A_{II}) a$$

$$\phi_I = -\frac{\sigma_1}{\epsilon_1} x$$

$$\phi_{II} = \frac{\sigma_2}{\epsilon_2} x - \left(\frac{\sigma_1}{\epsilon_1} + \frac{\sigma_2}{\epsilon_2} \right) a$$

Ej 2

IN.CO.

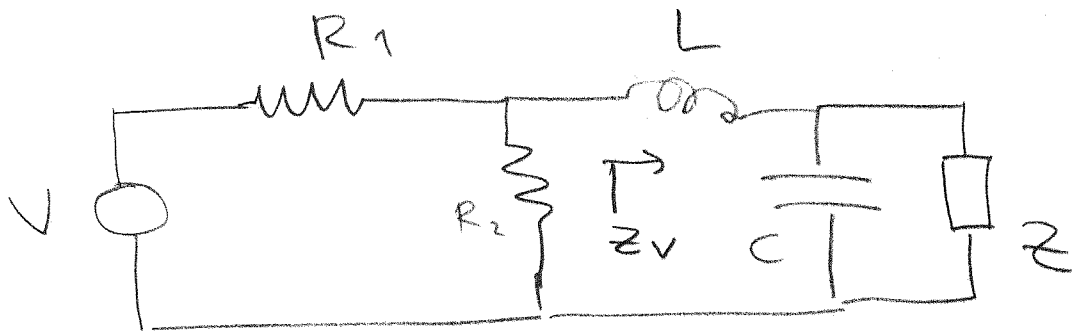

$$\rightarrow Z_v = R_1 + Lj\omega + \frac{\frac{1}{Cj\omega} Z}{Z + \frac{1}{Cj\omega}} =$$

$$Z_v = R_1 + Lj\omega + \frac{Z}{Cj\omega Z + 1}$$

a) Buscamos $Z_v = 0$ para potencia máxima


$$Z = -Lj\omega(Cj\omega Z + 1)$$
$$= LC\omega^2 Z - Lj\omega$$

$$Z = \frac{-Lj\omega}{1 - LC\omega^2} = \frac{jL\omega}{LC\omega^2 - 1}$$

b) Buscamos $Z_v = \infty$ para potencia mínima

$$Z = -\frac{1}{Cj\omega} = \frac{j}{C\omega}$$

Ej. 3

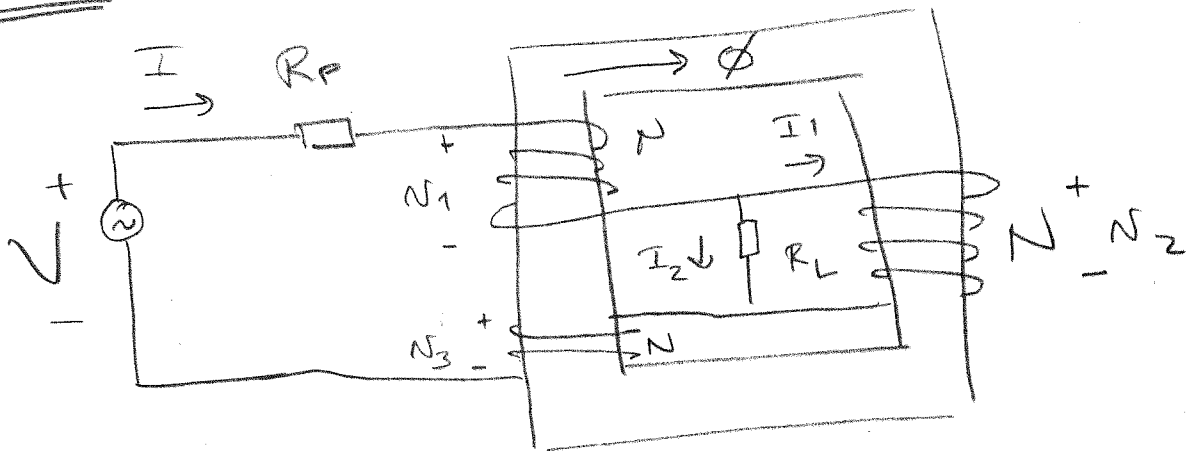

→ Circuito magnético

$$R\phi = 2N^2 i - N i_1$$

→ Faraday

$$V_1 = \frac{dN\phi}{dt} = V_3$$

$$V_2 = -\frac{dN\phi}{dt}$$

→ Mallas (Trabajo con fasores ahora)

$$V = IR_F + V_1 + V_2 + V_3$$

$$V = IR_F + V_3 = IR_F + V_1$$

$$V_1 = \frac{2N^2}{R} I j\omega - \frac{N^2}{R} I_1 j\omega$$

$$\Rightarrow V = I R_F + \frac{2N^2}{R} I_{j\omega} - \frac{N^2}{R} I_1 j\omega$$

$$\rightarrow I_2 R_L = \frac{N^2}{R} I_1 j\omega - \frac{2N^2}{R} I_{j\omega}$$

$$(I - I_1) R_L = \frac{N^2}{R} I_1 j\omega - \frac{2N^2}{R} I_{j\omega}$$

$$I_1 = \frac{\left(\frac{2N^2}{R} j\omega + R_L \right) I}{\left(\frac{N^2}{R} j\omega + R_L \right)}$$

$$V = I \left(R_F + \frac{2N^2}{R} j\omega \right) - \frac{N^2}{R} j\omega^H I$$

$$I = \frac{V}{R_F + \frac{2N^2}{R} j\omega - \frac{N^2}{R} j\omega^H}$$

$$= \frac{V \left(\frac{N^2}{R} j\omega + R_L \right)}{\left(\frac{N^2}{R} j\omega + R_L \right) \left(R_F + \frac{2N^2}{R} j\omega \right) - \frac{N^2}{R} j\omega \left(\frac{2N^2}{R} j\omega + R_L \right)}$$

$$= \frac{V \left(\frac{N^2}{R} j\omega + R_L \right)}{2R_L \frac{N^2}{R} j\omega + R_F \frac{N^2}{R} j\omega + R_L R_F - \frac{R_L N^2}{R} j\omega}$$

$$= \frac{V \left(\frac{N^2}{R} j\omega + R_L \right)}{R_L R_F}$$

$$\Rightarrow I = \frac{V \left(\frac{N^2}{R} j\omega + R_L \right)}{\frac{N^2}{R} j\omega (R_L + R_F) + R_L R_F}$$

$$I_1 = \frac{V \left(\frac{2N^2}{R} j\omega + R_L \right)}{\left(\right)}$$

$$\Rightarrow \Phi = \frac{N R_L V}{R \left[(R_L + R_F) \frac{N^2 j\omega}{R} + R_L R_F \right]}$$

$$\rightarrow I_2 = I - I_1$$

$$I_2 = - \frac{V \frac{N^2}{R} j\omega}{\left[\frac{N^2 j\omega}{R} (R_L + R_F) + R_L R_F \right]}$$

$$P = \frac{R_L}{2} |I_2|^2 = \frac{R_L}{2} \frac{\left(\frac{N^2}{R} \omega \right)^2 |V|^2}{\left[(R_L R_F)^2 + \left(\frac{N^2 \omega (R_L + R_F)}{R} \right)^2 \right]}$$

