


EJERCICIO 3

$$V_1(t) = V_0 \cos(\omega t)$$

$$V_2(t) = -V_0 \sin(\omega t)$$

1) $\omega / \lambda_L = 0$?

Circuito en fasores:

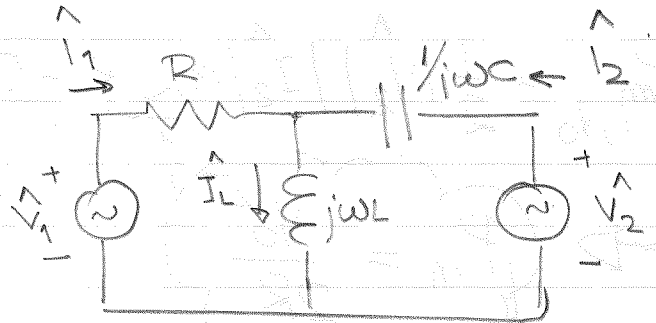


$$V_1(t) = \text{Re} \{ \hat{V}_1 e^{j\omega t} \} = V_0 \cos \omega t \Rightarrow |\hat{V}_1| = V_0$$

$$V_2(t) = \text{Re} \{ \hat{V}_2 e^{j\omega t} \} = -V_0 \sin(\omega t)$$

$$\text{Re} \{ |\hat{V}_2| e^{j\phi} e^{j\omega t} \} = V_0 \cos(\omega t + \pi/2)$$
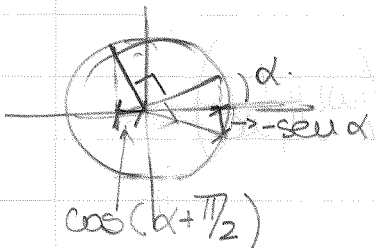
$$\Rightarrow \hat{V}_2 = V_0 e^{j\pi/2} = jV_0$$



Ley de nodos: $\hat{I}_1 + \hat{I}_2 = \hat{I}_L$

Ley de mallas: $\hat{V}_1 - R\hat{I}_1 - \hat{V}_L = 0$

$$\hat{V}_2 - \frac{1}{j\omega C}\hat{I}_2 - \hat{V}_L = 0$$

$$i_L(t) \equiv 0 \Leftrightarrow \hat{I}_L = 0 \Leftrightarrow \hat{V}_L = j\omega L \cdot \hat{I}_L = 0$$


$$\Rightarrow \begin{cases} \hat{V}_1 - R\hat{I}_1 = 0 \\ \hat{V}_2 - \frac{1}{j\omega C}\hat{I}_2 = 0 \\ \hat{I}_1 = -\hat{I}_2 \end{cases}$$

$$\Rightarrow \hat{V}_1 = V_0 = R\hat{I}_1 \Rightarrow \hat{I}_1 = -\hat{I}_2 = \frac{V_0}{R}$$

$$\hat{V}_2 = jV_0 = +\frac{1}{j\omega C} \cdot \left(-\frac{V_0}{R}\right) \Leftrightarrow 1 = \frac{1}{\omega RC} \Rightarrow \omega = \frac{1}{RC}$$

$$2) P_m \text{ fuentes} = P_{m_{V_0}} + P_{m_{jV_0}}$$

$$P_{m_{V_0}} = \frac{1}{2} |\hat{V}_1| \cdot |\hat{I}_1| \cos \varphi = \frac{V_0^2}{2R}$$

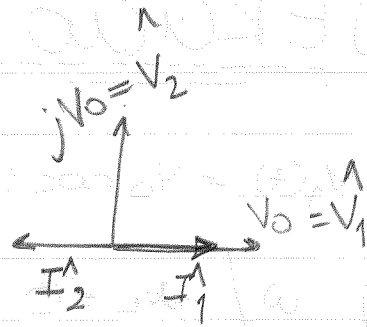


$$P_{m_{jV_0}} = \frac{1}{2} |\hat{V}_2| \cdot |\hat{I}_2| \cos \varphi = 0$$

$$\Rightarrow P_m = \frac{V_0^2}{2R}$$

$$3) V_1(t) = V_0 \cos(\omega t) \quad \omega / |\hat{I}_1| \text{ m\u00ednima?}$$

$$V_2(t) = 0$$

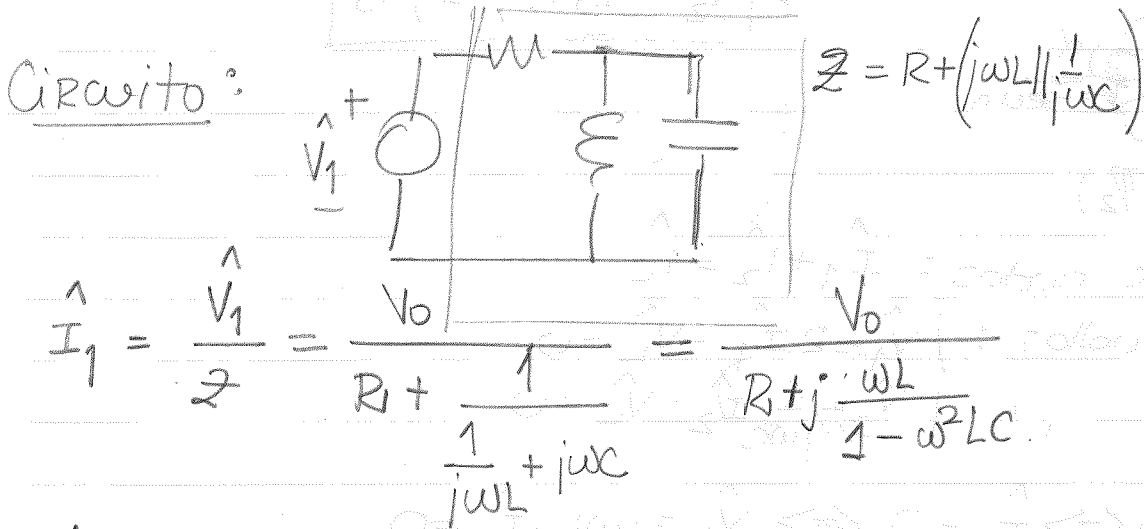

$|\hat{I}_1|$ es m\u00ednima si $\frac{\omega L}{1 - \omega^2 LC}$ es m\u00e1ximo.

$$\Leftrightarrow \omega^2 LC = 1 \Leftrightarrow \omega = \frac{1}{\sqrt{LC}}$$