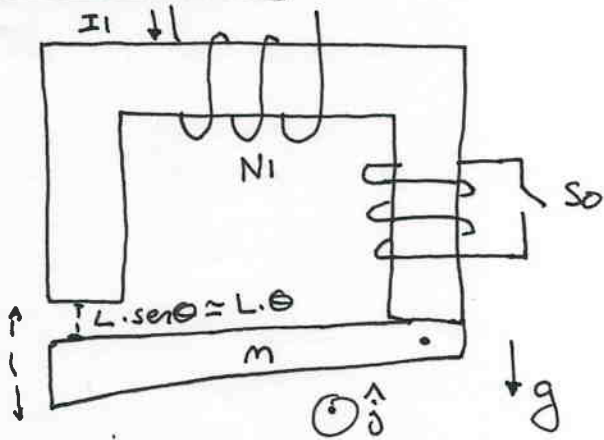


# SOLUCIÓN 2º PARCIAL 2009

## Problema 1:



Al cerrar la llave congelo el

$$\text{Flujo: } \mathcal{E} = \frac{d\phi}{dt} = 0$$

$$\Rightarrow \underline{\underline{\phi \text{ cte}}}$$

$$N_1 I_1 = \mathcal{R} \phi$$

$$\phi = B \cdot S \Rightarrow H_i = \frac{\phi}{\mu S} ; H_e = \frac{\phi}{\mu_0 S}$$

$$\Rightarrow U = \frac{\mu \cdot \phi^2 \cdot L \cdot \theta \cdot S}{2 \mu_0 S^2 \mu} + \frac{\mu_0 \cdot \phi^2 \cdot 4 L \cdot S}{\mu_0 2 \mu S^2}$$

$$= \frac{\phi^2 (L \theta \mu + 4 \mu_0 L)}{2 \mu_0 \mu \cdot S}$$

$$\tau = - \left. \frac{dU}{d\theta} \right|_{\phi = \text{cte}} = - \frac{L \phi^2}{2 \mu_0 S} = - \frac{L \left( \frac{N_1 I_1}{\mathcal{R}} \right)^2}{2 \mu_0 S}$$

$$|\vec{\tau}_{\text{peso}}| = mg \frac{L}{2}$$

$$\Rightarrow \frac{(N_1 I_1)^2 \mu^2 S}{32 \mu_0 L} = \frac{mg L}{2}$$

$$\Rightarrow I_1 = \sqrt{\frac{16 \mu_0 L^2 mg}{\mu^2 S \cdot N_1^2}}$$

## Problema 2:

$$\text{Ampere: } N_1 \cdot I_1 = 3L H_i + L \theta \cdot H_e + L \cdot \left( \frac{B}{\mu_0} + M \right)$$

$$\Rightarrow N_1 I_1 = \frac{3L \cdot \phi}{\mu S} + \frac{L \theta \cdot \phi}{\mu_0 S} + L \left( \frac{\phi}{\mu_0 S} + M \right)$$


$$\Rightarrow \boxed{\phi = \frac{(N_1 I_1 - LM) \cdot \mu_0 \mu S}{3L \mu_0 + \mu L \theta + \mu L}}$$

$$\tau = \frac{\phi^2 L}{2 \mu_0 S} = \frac{(N_1 I_1 - LM)^2 (\mu_0 \mu S)^2 L}{(3L \mu_0 + \mu L) \cdot 2 \mu_0 S} = \frac{mgL}{2}$$

$$(N_1 I_1 - LM)^2 = \frac{(3L \mu_0 + \mu L)^2 mg}{\mu_0 S \mu^2}$$

$$\boxed{I_1 = \frac{L |M|}{N_1} + \frac{(3\mu_0 + \mu) \cdot L}{\mu \mu_0 N_1} \cdot \sqrt{\frac{mg \mu_0}{S}}}$$

### Problema 3:

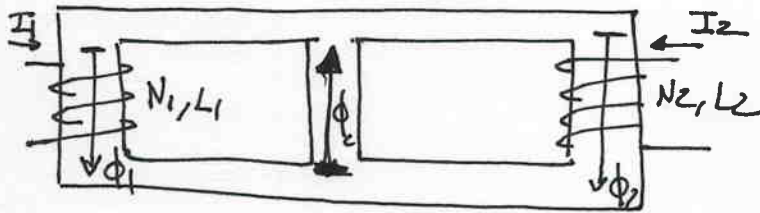

$$\Rightarrow \phi_c = \phi_1 + \phi_2$$

$$\begin{cases} N_1 I_1 = 3R\phi_1 + R\phi_c \\ N_2 I_2 = 3R\phi_2 + R\phi_c \end{cases}$$

$$N_1 I_1 + N_2 I_2 = 2R\phi_c + 3R(\phi_1 + \phi_2) = 5R\phi_c$$

$$\Rightarrow \phi_c = \frac{N_1 I_1 + N_2 I_2}{5R}$$

$$\Rightarrow 3R\phi_L = \frac{4}{5} \cdot N_1 I_1 - \frac{1}{5} \cdot N_2 I_2$$

$$3R\phi_R = \frac{4}{5} N_2 I_2 - \frac{1}{5} \cdot N_1 I_1$$

$$\left\{ \begin{aligned} \phi_L &= \frac{\frac{4}{5} \cdot N_1 I_1 - \frac{1}{5} \cdot N_2 I_2}{3R} \end{aligned} \right.$$

$$\left\{ \begin{aligned} \phi_R &= \frac{\frac{4}{5} \cdot N_2 I_2 - \frac{1}{5} \cdot N_1 I_1}{3R} \end{aligned} \right.$$

$$L_1 = \frac{4N_1^2 \mu S}{15l}$$

$$L_2 = \frac{4N_2^2 \mu S}{15l}$$


$$|M_{12}| = \frac{N_1 N_2 \mu S}{15l}$$

## Problema 4:

$$N_1 = N_2 ; \Phi_1 = \Phi_2$$

$$\rightarrow L_1 = L_2$$

Recordar que  $|M| \leq \sqrt{L_1 L_2} = L$ .

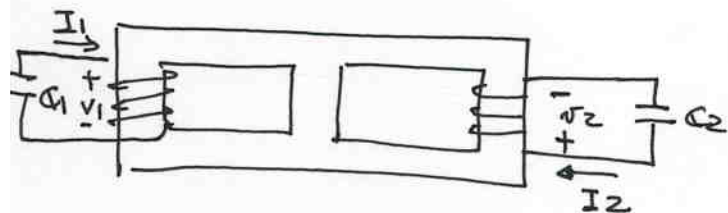

Ecuaciones del transformador:

$$N_1(t) = L \cdot \frac{di_1}{dt} + M \frac{di_2}{dt} = L \frac{d^2 q_1}{dt^2} + M \frac{d^2 q_2}{dt^2}$$

$$N_2 = L \frac{d^2 q_2}{dt^2} + M \frac{d^2 q_1}{dt^2}$$

Por otro lado:

$$N_1(t) = - \frac{q_1(t)}{\Phi}$$

$$N_2(t) = - \frac{q_2(t)}{\Phi}$$

(Por la conversi3n de signos utilizada).


A su vez de la parte anterior sabemos que  $M < 0$ .

$$\Rightarrow (L - |M|) \cdot \frac{d^2 (q_1 + q_2)}{dt^2} = - \left( \frac{q_1 + q_2}{\Phi} \right)$$

$$\Rightarrow q_1 = -q_2 - \underbrace{\frac{\Phi(L - |M|)}{\Phi}}_{\neq 0} \cdot \frac{d^2 (q_1 + q_2)}{dt^2}$$

$$\Rightarrow \boxed{q_1(t) = -a \cdot \frac{d^2 (q_1 + q_2)}{dt^2} - b \cdot q_2(t)}$$

# PROBLEMA 5:

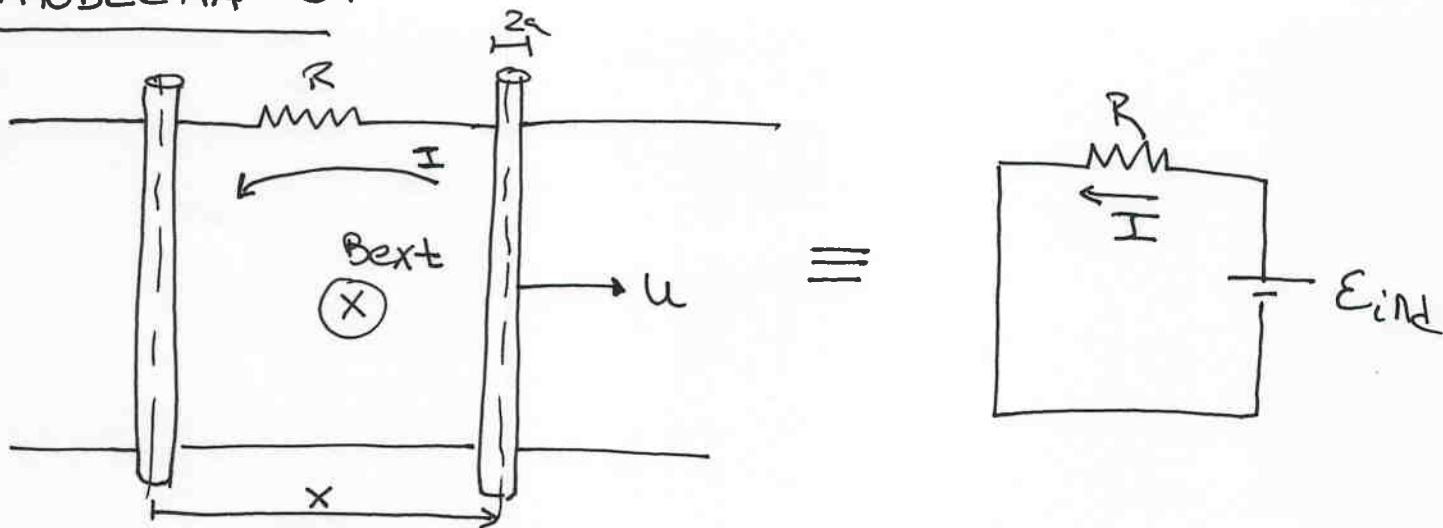

$$\phi = B_{ext} \cdot D \cdot (x(t) - 2a) + \phi \text{ autoinducido}$$

$$|\phi_{\text{autoinducido}}| = 2 * \int_a^{x-a} \frac{\mu_0 I}{2\pi x'} \cdot D \cdot dx' = \frac{\mu_0 D}{\pi} \cdot I \cdot \ln\left(\frac{x-a}{a}\right)$$

$$\phi = B_{ext} \cdot D \cdot (x(t) - 2a) - \frac{\mu_0 D}{\pi} \cdot I \cdot \ln\left(\frac{x-a}{a}\right)$$

$$\frac{d\phi}{dt} = B_{ext} \cdot D \cdot \dot{x} - \frac{\mu_0 D I}{\pi} \cdot \frac{a}{x-a} \cdot \frac{\dot{x}}{a} - \frac{\mu_0 D}{\pi} \cdot \ln\left(\frac{x-a}{a}\right) \cdot \frac{dI}{dt}$$

$\swarrow$   
0

$$E_{ind} = \frac{d\phi}{dt} ; \text{ y adem\u00e1s } E_{ind} = R I$$

$$\Rightarrow B_{ext} \cdot D \cdot \dot{x} - \frac{\mu_0 D I}{\pi} \cdot \frac{\dot{x}}{x-a} = R \cdot I$$


$$\Rightarrow I(t) = \frac{B_{ext} \cdot D \cdot \dot{x}}{R + \frac{\mu_0 D \cdot \dot{x}}{\pi (x-a)}}$$

## Problema 6 :

$$\mu = \text{cte.}$$

$$P_R = R i^2$$

$$P_u = F_{\text{ext}}(t) \cdot u$$

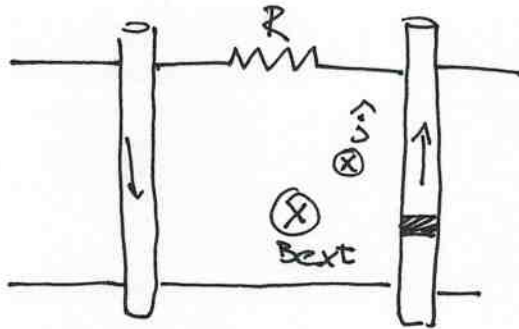

$$dF = I \cdot d\vec{\ell} \wedge \vec{B}$$


$$\vec{B} = \vec{B}_{\text{ext}} - \frac{\mu_0 I}{2\pi x} \hat{z}$$

$$F_{\text{ext}}(t) = \int_0^D I \cdot d\ell \left( \frac{\mu_0 I}{2\pi x} + B_{\text{ext}} \right) = D \cdot I \cdot \left( B_{\text{ext}} - \frac{\mu_0 I}{2\pi x} \right)$$

$$P_u = B_{\text{ext}} \cdot D I \cdot u - \frac{D \cdot \mu_0 I^2}{2\pi x} \cdot \mu$$

$$P_u - P_R = B_{\text{ext}} \cdot D \cdot u \cdot i(t) - \left( \frac{D \cdot \mu_0 \cdot u}{2\pi \cdot x} + R \right) i(t)^2$$

# PROBLEMA 7:

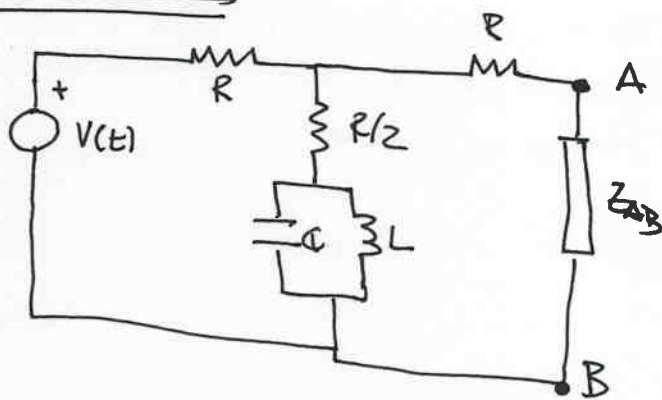

$$\bar{V}(t) = V_0 e^{j\omega t}$$

$$\omega = R/L = 1/\sqrt{LC}$$

$$V_A - V_B = \frac{(1+j)\bar{V}(t)}{2}$$


Veamos la impedancia de la rama central:

$$\bar{Z}_c = \frac{R}{2} + C // L = \frac{R}{2} + \frac{Lj\omega \cdot \frac{1}{Cj\omega}}{Lj\omega + \frac{1}{Cj\omega}}$$

$$\bar{Z}_c = \frac{R}{2} + \frac{Lj\omega}{-L^2\omega^2 + 1}$$

evaluando  $Z_c$  en  $\omega = 1/\sqrt{LC}$

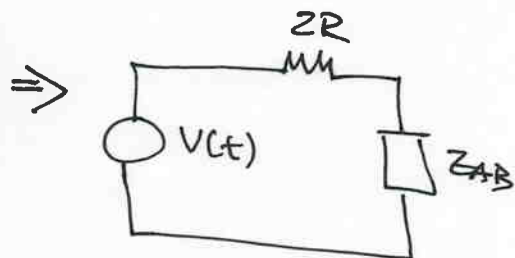$Z_c = \infty \Rightarrow$  NO PASA corriente por la rama central.



$\Rightarrow$  Divisor resistivo:

$$V_{AB} = \frac{V(t) \cdot Z_{AB}}{2R + Z_{AB}} = \left(\frac{1+j}{2}\right) \cdot V(t)$$

$$2 Z_{AB} = (1+j) \cdot [2R + Z_{AB}]$$

$$Z_{AB}(1-j) = 2R \cdot (1+j)$$

$$\Rightarrow Z_{AB} = \frac{2R(1+j)}{(1-j)} = \frac{2R(1+j)^2}{2}$$


$$Z_{AB} = \frac{2R(1-1+2j)}{2}$$

$$\Rightarrow \boxed{Z_{AB} = 2jR}$$



## Problem 8:

$$Z_{AB} = R + j\omega L$$

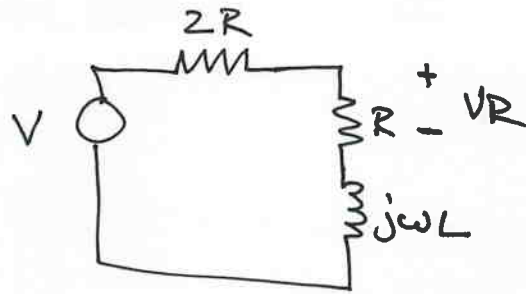

Divisor resistivo:

$$V_R = \frac{V \cdot R}{3R + j\omega L} = \frac{V R}{3R + j \frac{R \cdot \cancel{L}}{\cancel{L}}} = \frac{V}{3 + j}$$

$$|V_R| = \frac{V_0}{\sqrt{9 + 1}} = \frac{V_0}{\sqrt{10}}$$

$$\Rightarrow P_{OT} = \frac{1}{2} \cdot \frac{V_R^2}{R}$$

$$\boxed{P_{OT} = \frac{V_0^2}{20R}}$$