

$$V_1(t) = V_I \cos(\omega t) \Rightarrow \hat{V}_1 = V_I$$

$$Z = \frac{j\omega L_1(j\omega L_2 + 1/j\omega C)}{j\omega(L_1 + L_2) + 1/j\omega C} = j\omega L_1 \frac{(1 - \omega^2 L_2 C)}{1 - \omega^2 C(L_1 + L_2)}$$

↑
L1 || (L2 + C)

↑
imaginario!
Puro

a) $i(t) = ?$

$$\hat{I} = \frac{V_I}{Z_{TOT}} = \frac{V_I}{R + j\omega L_1 \frac{(1 - \omega^2 L_2 C)}{1 - \omega^2 C(L_1 + L_2)}}$$

$$= \frac{[1 - \omega^2 C(L_1 + L_2)] V_I}{R[1 - \omega^2 C(L_1 + L_2)] + j\omega L_1 (1 - \omega^2 L_2 C)}$$

denominador

$$= \frac{[] V_I}{W e^{i\varphi}}$$

en cuadrantes I y IV si $1 > \omega^2 L_2 C$

con $\varphi = \begin{cases} \text{atan}(\alpha) & \text{si } 1 < \omega^2 L_2 C \\ \pi + \text{atan}(\alpha) & \text{si } 1 > \omega^2 C(L_1 + L_2) \\ \pi - \text{atan}(\alpha) & \text{si } 1 < \omega^2 C(L_1 + L_2) \end{cases}$


$$\alpha = \frac{\omega L_1 (1 - \omega^2 L_2 C)}{[1 - \omega^2 C(L_1 + L_2)] R}$$

$$i(t) = \frac{1 - \omega^2 C(L_1 + L_2)}{R^2 [1 - \omega^2 C(L_1 + L_2)]^2 + (\omega L_1)^2 (1 - \omega^2 L_2 C)^2} V_I \cos(\omega t - \varphi)$$

$$i(t) = \text{Re} \{ \hat{I} e^{j\omega t} \} \Rightarrow I_0$$

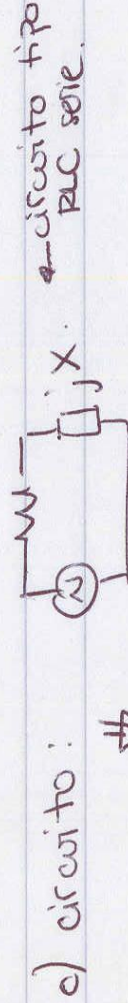b) $P_{\text{m}} = R \cdot I_0^2 / 2$

(la potencia que entrega la fuente es la disipada en la resistencia)



ω_{\min} si $I = 0 \Leftrightarrow X = \infty \Leftrightarrow 1 - \omega^2 C(L_1 + L_2) = 0 \Rightarrow \omega_{\min} = \frac{1}{\sqrt{L_1 + L_2} C}$

ω_{\max} si $X = 0 \Leftrightarrow \omega_{\max} = \frac{1}{\sqrt{L_2} C}$