

Calibración de transformadores de voltaje

Daniel Slomovitz


Instituto de Ingeniería Eléctrica

Facultad de Ingeniería

UNIVERSIDAD DE LA REPÚBLICA

2021

Errores

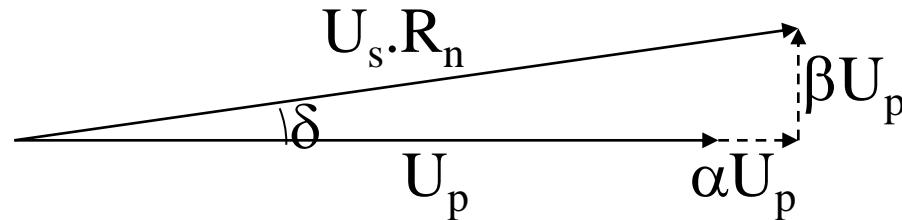


$$U_s R_n = U_p (1 + \alpha + j\beta) \approx U_p (1 + \alpha)$$

$$\delta \approx Ar \operatorname{tg} \beta \approx \beta$$

Si $\alpha > 0$, la tensión de salida es mayor que la que debería ser.

Puente diferencial

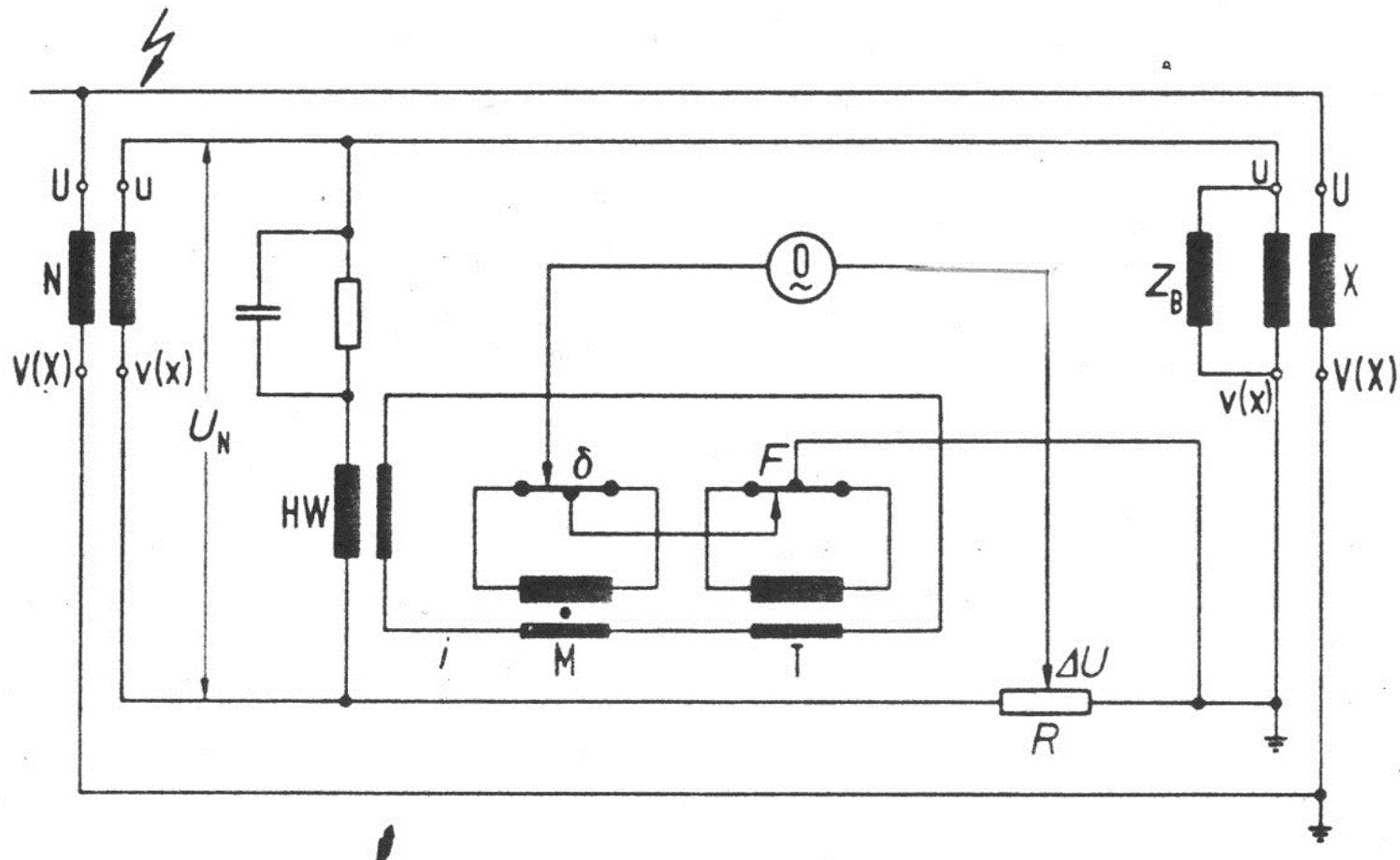

Puente de transformadores diferencial LABUTE



Calibracion TV

Puente de medida

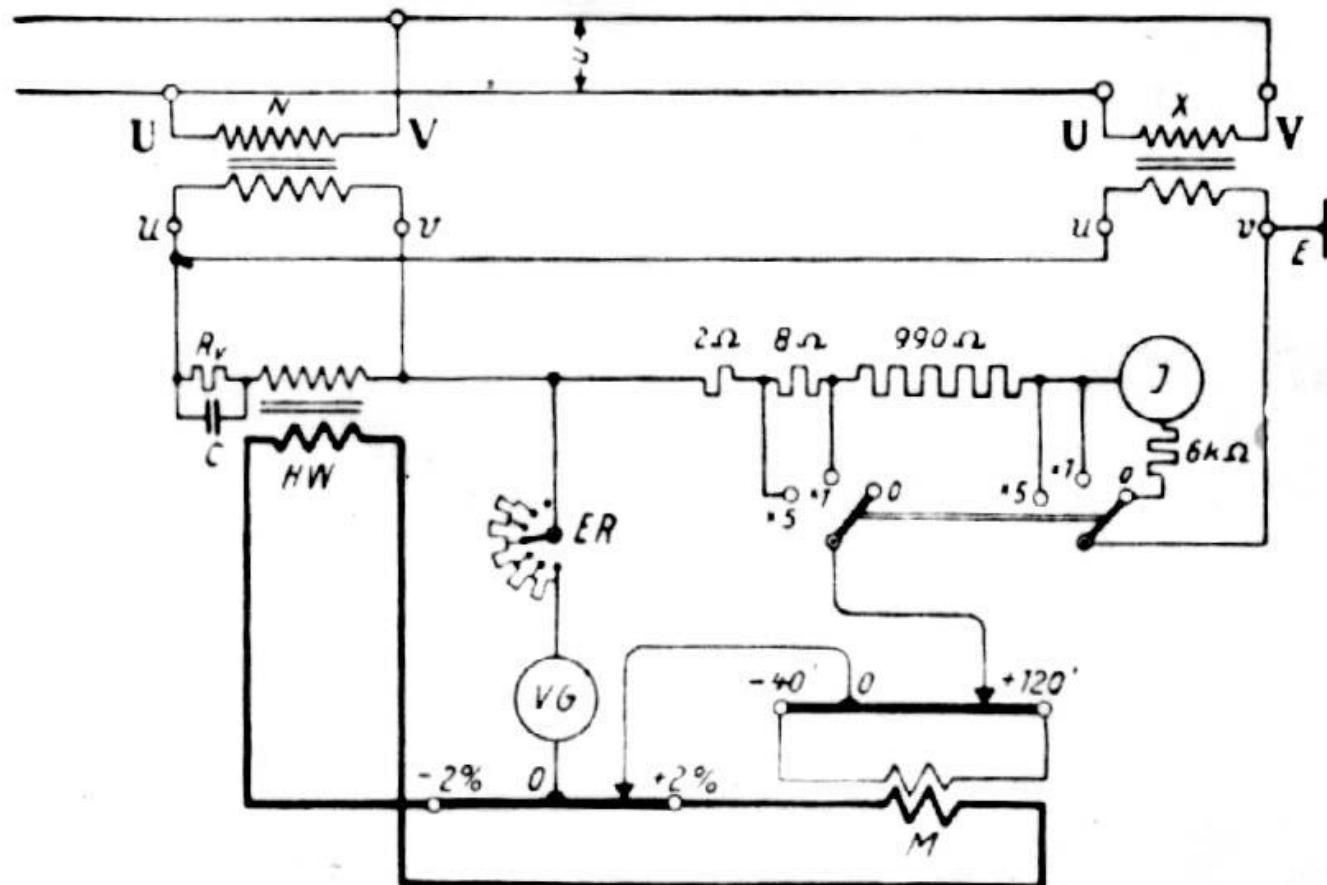


Abb. 2. Schaltbild der Spannungswandler-Prüfeinrichtung
nach Dr. Hohle.

Galvanómetro electrónico



Método diferencial con IVD


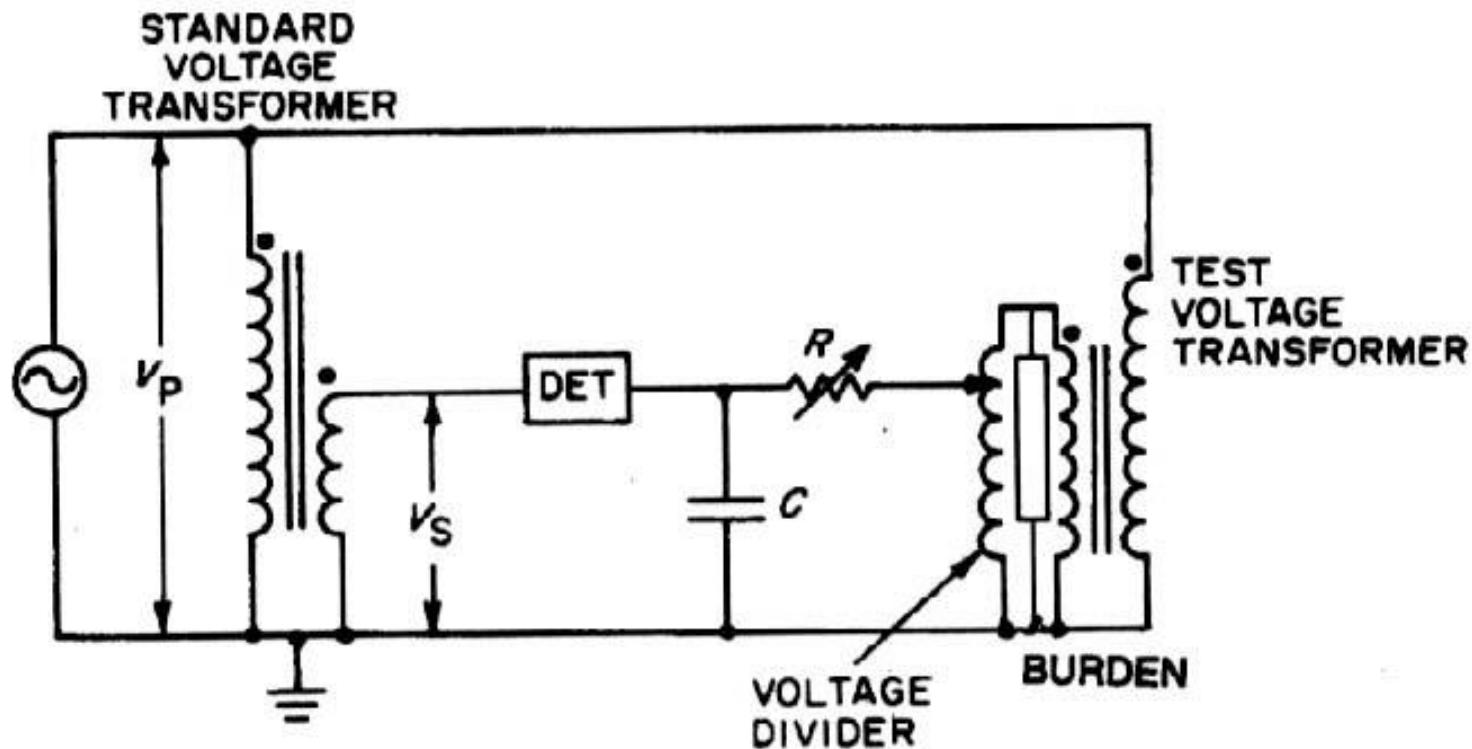


Figure 17 —Voltage transformer accuracy test—Comparative-null method

Desfasador

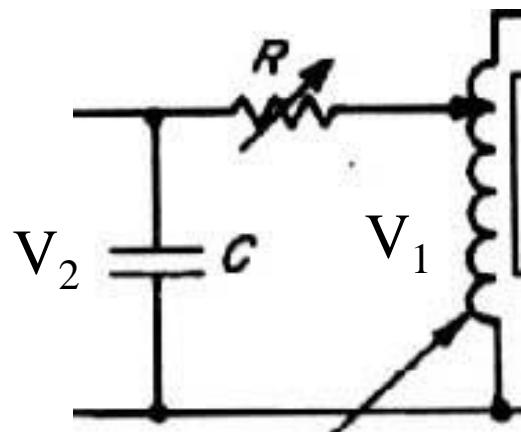

Sea V_1 : tensión de entrada
 V_2 : tensión de salida

$$\frac{V_2}{V_1} = \frac{1}{1 + j\omega RC}$$

$$Arg\left(\frac{V_2}{V_1}\right) = -\omega RC$$


$$\left| \frac{V_2}{V_1} \right| = \frac{1}{\sqrt{1 + (\omega RC)^2}} \approx 1 - \frac{(\omega RC)^2}{2} \approx 1$$

IVD




Precisión: $\pm 0,0005 \%$, $\pm 20 \mu\text{rad}$

Puente basado en comparador de corriente

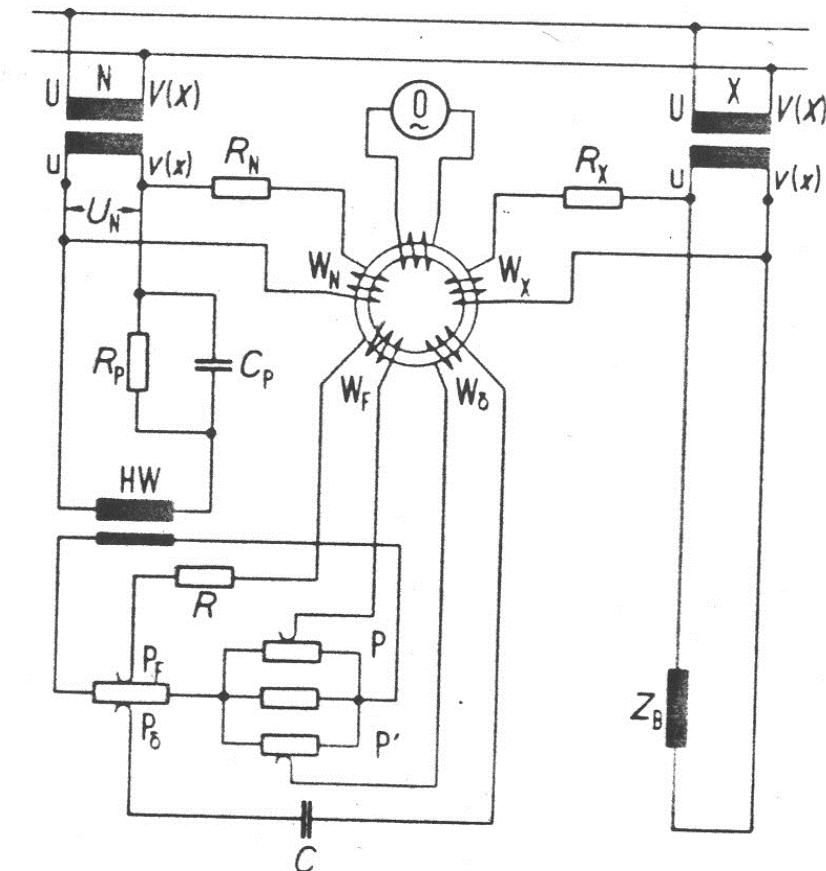

Puente electrónico automático

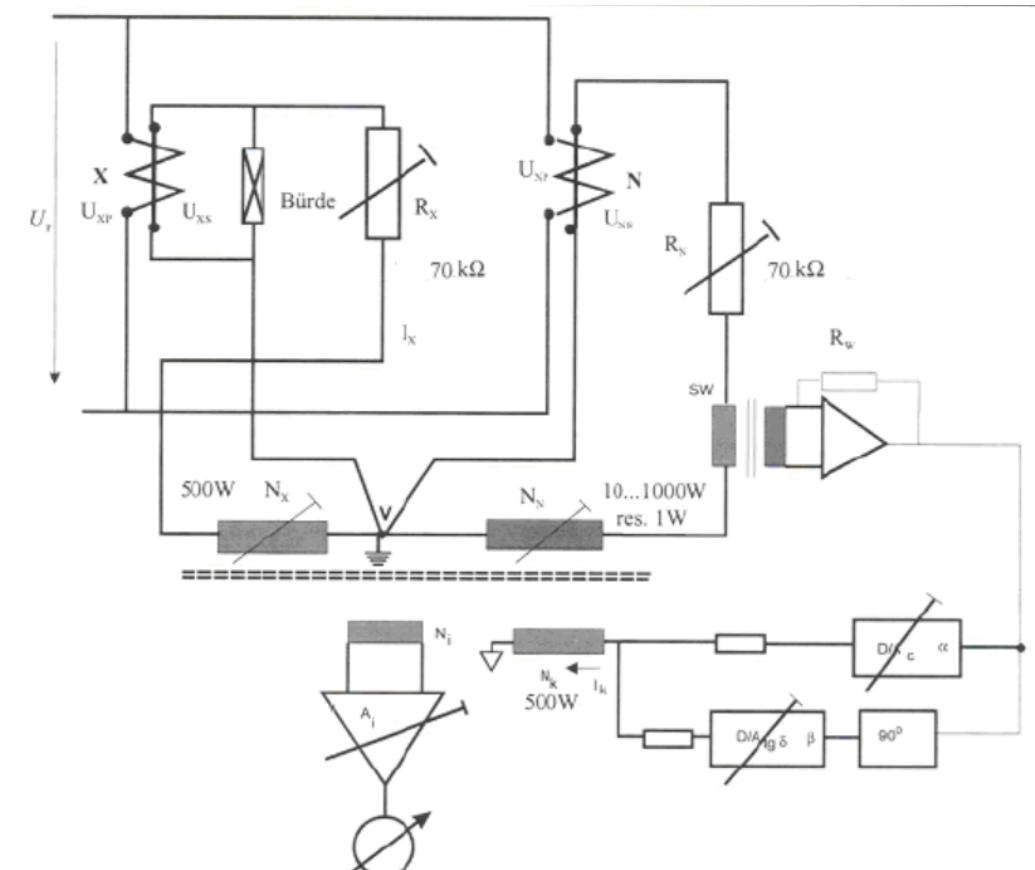

Calibracion TV

Puente electrónico



Puente electrónico

Potential Transformer test part

Nominal voltage of the PT to be tested (X)	30 ... 350 V with factors 1, $\frac{1}{2}$, $\frac{1}{3}$, $\frac{1}{\sqrt{3}}$
Nominal voltage of the standard PT (N)	30 ... 350 V with factors 1, $\frac{1}{2}$, $\frac{1}{3}$, $\frac{1}{\sqrt{3}}$
Matching	0.5 ... 1.6
Working range	1 ... 210% of nominal current
Input voltage range N and X	1 V ... 350 V
Frequency	50 and 60 Hz
Measuring range ratio error	$\pm 20 \%$
Resolution ratio error	0.001 %
Measuring range phase angle	$\pm 200 \text{ crad}$
Resolution phase angle	0.001 Min or 10 μrad
Uncertainty of ratio measurement	$\pm 100 \text{ ppm} \pm 1\% \text{ of reading}$
Uncertainty of phase measurement	$\pm 100 \mu\text{rad} \pm 1 \% \text{ of reading}$
Inherent burden of X- and N-Side	30 k Ω ... 110 k Ω
Resolution voltage measurement	0.1 % / 0.01 kV
Uncertainty voltage measurement	$\pm 1\% \text{ reading} \pm 1\% \text{ of range}$

Método con comparador de corriente con capacitores

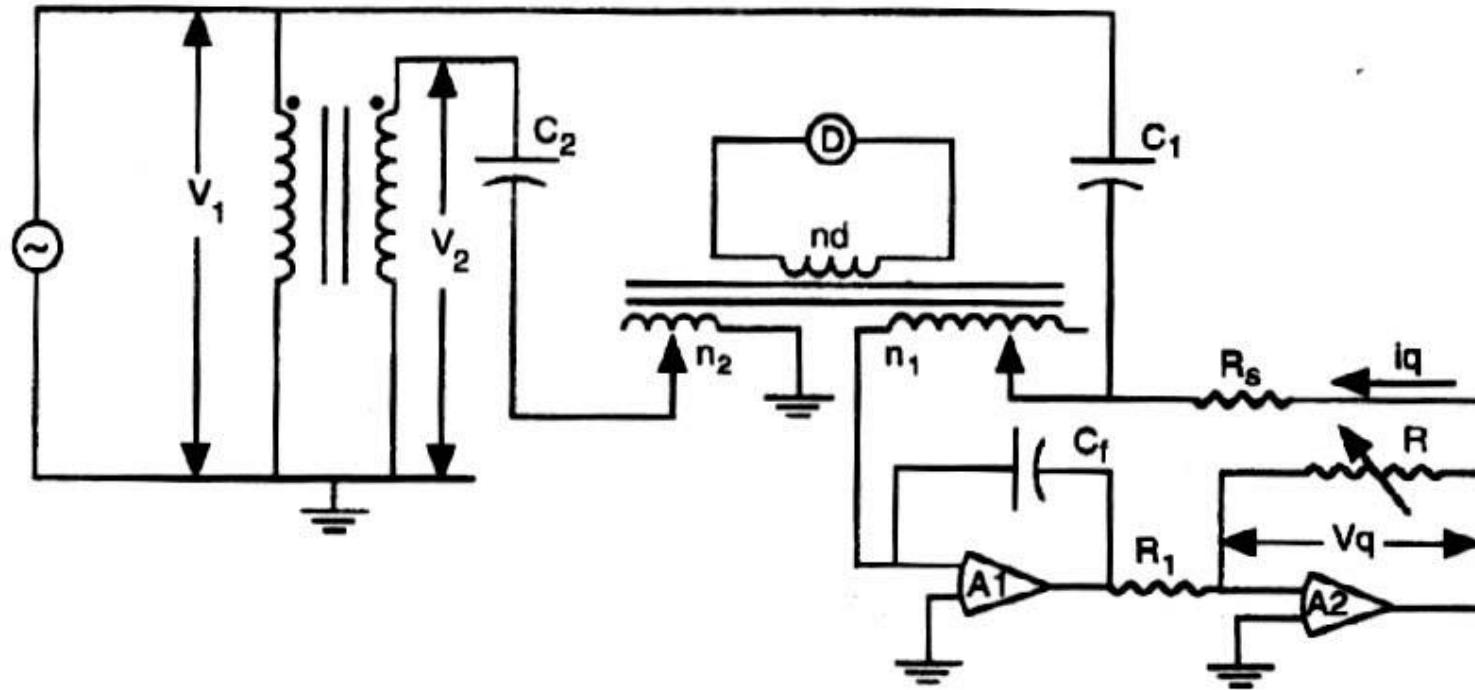


Figure 13 —Voltage transformer accuracy test (direct-null) current comparator—Capacitance ratio method

Método con comparador de corriente con capacitores

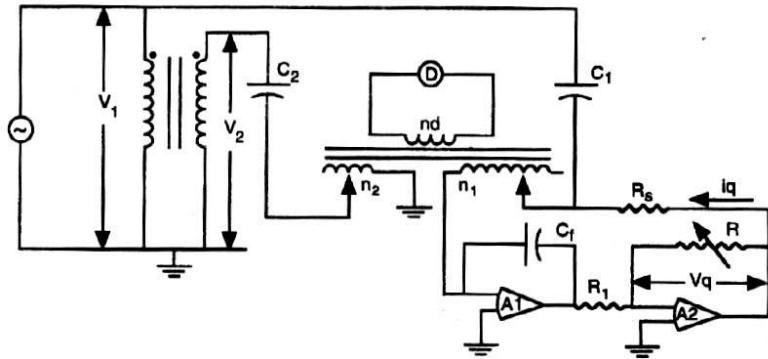


Figure 13 —Voltage transformer accuracy test (direct-null) current comparator—
Capacitance ratio method

$$I_{C1} = V_1 j\omega C_1 \quad I_{C2} = V_2 j\omega C_2$$

$$I_q \approx \frac{1}{R_s} \frac{R}{R_1} \frac{C_1}{C_f} V_1$$


$$n_1 I_{C1} + n_1 I_q - n_2 I_{C2} = 0$$

$$n_1 V_1 \left(j\omega C_1 + \frac{1}{R_s} \frac{R}{R_1} \frac{C_1}{C_f} \right) = n_2 V_2 j\omega C_2$$

$$\frac{V_2}{V_1} = \frac{n_1}{n_2} \left(\frac{C_1}{C_2} - j \frac{RC_1}{\omega R_s R_1 C_f C_2} \right)$$

$$\text{Relación} \approx \frac{n_1 C_1}{n_2 C_2} \quad \text{Angulo} = -\frac{R}{R_1} \frac{1}{R_s \omega C_f}$$

Método con divisor de tensión capacitivo

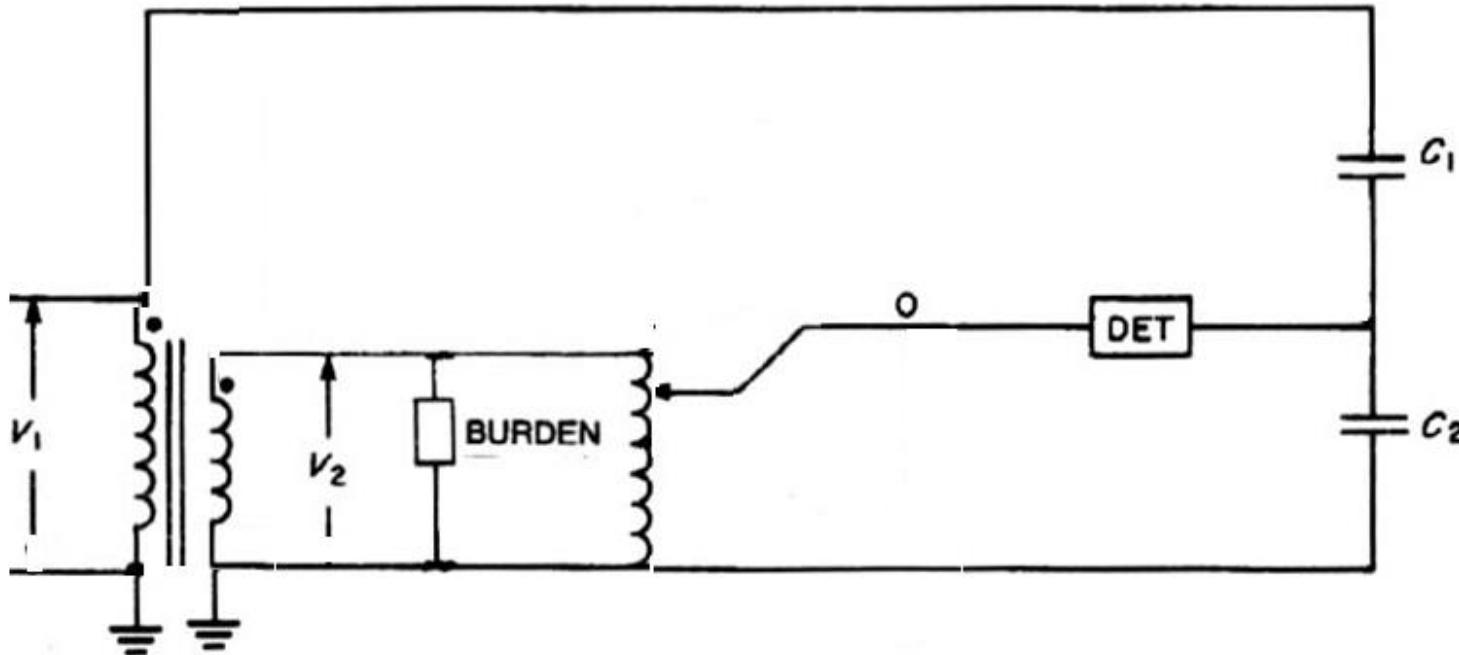

Ajuste de divisor hasta minimizar lectura en DET

Error relación: lectura de divisor, C_1 , C_2


Error desfasaje: lectura DET

Capacitor patrón de gas de 200 kV




Capacitor patrón de AT

Placa de características

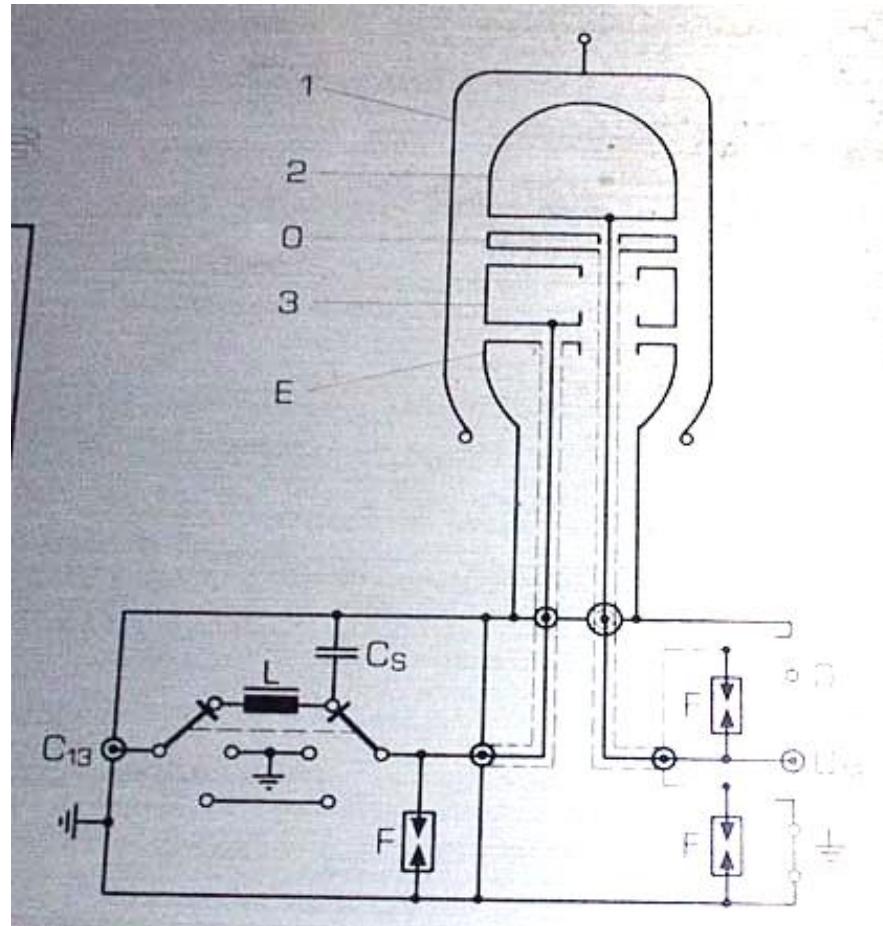


Calibracion TV

Transformador patrón 15 kV

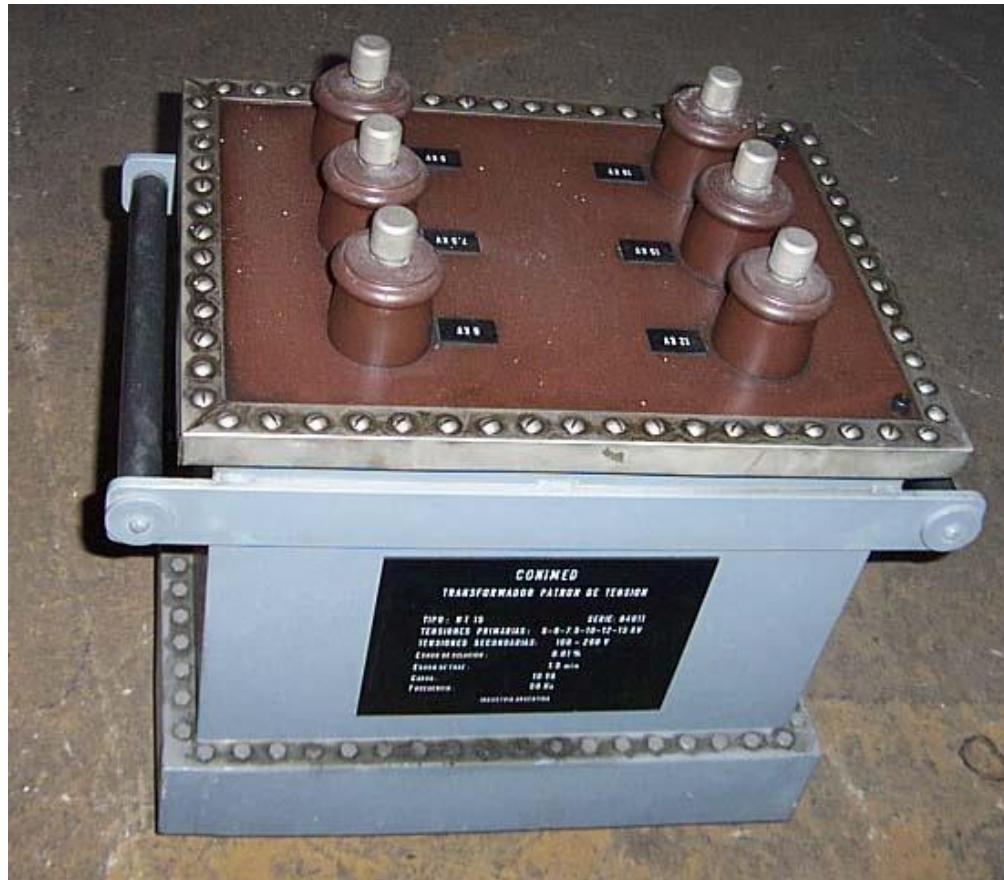


Transformador patrón 100 kV

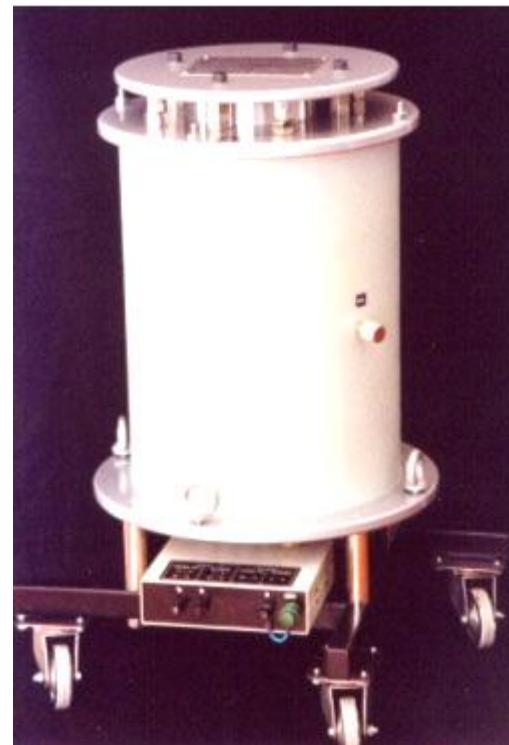

Exactitud: $\pm 0,01\%$ $\pm 1'$ para $0,3 < U/U_n < 1,2$

Transformador patrón, doble etapa

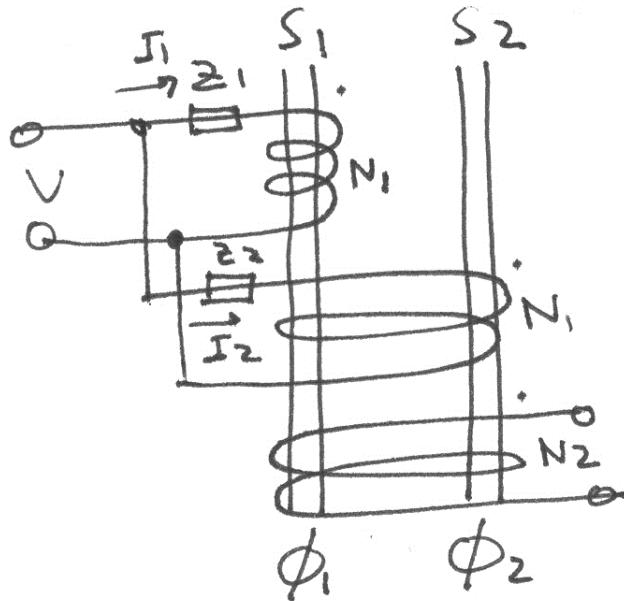

$$E = -jN\dot{\phi}\omega$$

$$NI = Hl = \frac{Bl}{\mu} = \dot{\phi}l / (\mu A)$$

$$V - E = Z \cdot I$$

$$\dot{\phi}_1 = \dot{\phi}(1 - e_1)$$

$$E_1 = -jN\dot{\phi}_1\omega$$

$$E_2 = -jN\dot{\phi}_2\omega$$

$$I_2 = \dot{\phi}_2 \cdot l_2 / (\mu \cdot A_2 \cdot N)$$

$$V - (E_1 + E_2) = Z_2 \cdot I_2$$

Sustituyendo

$$V \cdot e_1 = \dot{\phi}_2 \cdot N \cdot \omega \left(\frac{Z_2}{jX_{L2}} + 1 \right), \quad X_{L2} = \mu \cdot A \mu_2 \cdot N^2 \omega / l$$

$$V \cdot e_1 (1 - e_2) = \dot{\phi}_2 \cdot N \cdot \omega$$

Finalmente

$$\dot{\phi}_1 + \dot{\phi}_2 = \frac{jV}{N\omega} (1 - e_1 \cdot e_2)$$

Fin