

Solución ejercicio 2do parcial 2020

Parte a)	R _a =	4	Ω
	R _{1J} =(ρ/2.π.L) . Ln(4.L/d)	36,62	Ω
	ρ	80	Ω.m
	L	2	m
	d	0,0254	m
	espaciamento=	3	m
	Req=K . R _{1J} < Ra		
	K<Ra/R _{1J} =	0,109	

Se precisan 14 jabilinas


Ra'=	3,92
------	------

<i>L = 2m d = 1"</i>		2 m	3 m	4 m	5 m
Número de jabilinas	K	K	K	K	K
2	0,577	0,554	0,542	0,534	
3	0,420	0,394	0,380	0,371	
4	0,335	0,309	0,296	0,287	
5	0,281	0,257	0,243	0,235	
6	0,243	0,220	0,207	0,200	
7	0,215	0,193	0,181	0,174	
8	0,194	0,173	0,161	0,154	
9	0,176	0,156	0,145	0,139	
10	0,162	0,143	0,133	0,126	
11	0,150	0,132	0,122	0,116	
12	0,140	0,122	0,113	0,107	
13	0,131	0,114	0,105	0,100	
14	0,124	0,107	0,099	0,093	
15	0,117	0,101	0,093	0,088	

Parte b)

- i) $\Delta In < Id$
- ii) $Ra \cdot \Delta In \leq U_L (t \rightarrow \infty)$
- iii) $t_{ap} \leq t_{max_seg} @ U_c$
- iv) $I_{fugas} < \Delta In / 2$

i) $\Delta In < Id = 25,9 \text{ A}$

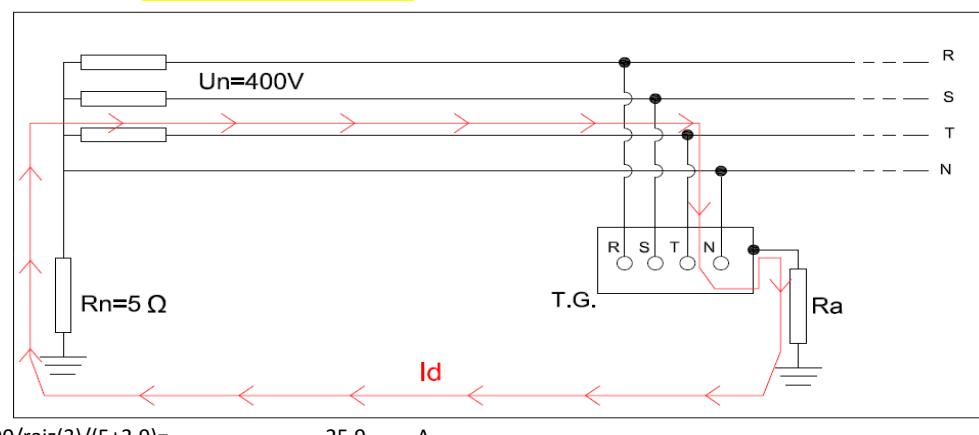

Id≈Un/radiz(3)/(Rn+Ra)= 400/radiz(3)/(5+3,9)= 25,9 A

ii) $Ra \cdot \Delta In < U_L$, $\Delta In < U_L / Ra = 50 / 3,92 = 12,8 \text{ A}$

Estado seco, por tanto, $U_L = 50 \text{ V}$

iii) $t_{ap} \leq t_{max_seg} @ U_c$

$$\begin{aligned} U_c(V) &= Ra \cdot Id = \\ &= 3,92 \cdot 25,9 = \\ &= 101,5 \quad V \\ t_{max_seg} @ U_c &= 0,34 \text{ s} \\ \text{entonces: } t_{ap} &\leq 0,34 \text{ s} \end{aligned}$$

Tensión de contacto (V)	Tiempos máximos (s)	
	Estado seco	Estado mojado
25	∞	∞
50	∞	0,48
75	0,60	0,30
90	0,45	0,25
120	0,34	0,18
150	0,27	0,12
220	0,17	0,05
280	0,12	0,02
350	0,08	-
500	0,04	-

Corriente falla	ΔIn	2ΔIn	5ΔIn
Tiempo máximo de apertura (s):	0,3	0,15	0,04

Por tanto, $\Delta In < Id$

$\Delta In < Id = 25,9 \text{ A}$

iv) $I_{fugas} < \Delta In / 2$



$2 * I_{fugas} < \Delta In$

$I_{fugas}=2,5 \text{ mA} * (6+5)=$

27,5mA

$55 \text{ mA} < \Delta In$


De las 4 condiciones:

55mA < ΔI_n < 12,8 A

Parte c)

P=	45	kW
$\cos \varphi_1 =$	0,83	
$\tan \varphi_1 =$	0,672	
$\cos \varphi_2 =$	0,98	
$\tan \varphi_2 =$	0,20	
$Q_c =$	21,1	kVAr
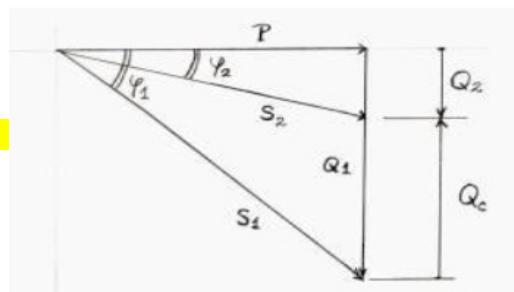
$$Q_C = P \cdot (\tan \varphi_1 - \tan \varphi_2)$$



d)

Un= 400 V

w=	314,16	rad/s
P=	45	kW
$\cos \varphi_1 =$	0,83	
$\tan \varphi_1 =$	0,67	
$\cos \varphi_2 =$	0,98	
$\tan \varphi_2 =$	0,20	

$Q_{C_triangulo} = 21,10$ kVAr

$$Q_{C_triangulo} = 3 \cdot U_n^2 \cdot w \cdot C$$

$$Q_{C_estrella} = U_n^2 \cdot w \cdot C$$

C= 1,3994E-04 F = 139,9 uF

$Q_{C_estrella} = 7,03$ kVAr

P= 45 kW S= 45,92 kVA
 $Q = Q_1 - Q_{C_estrella} = 9,14$ kVAr $\cos \varphi_2 = 0,98$

P= 45 kW S= 50,6312014 kVA
 $Q = Q_1 - Q_{C_estrella} = 23,21$ kVAr $\cos \varphi_2 = 0,89$

e.i) Q= $Q_1 - Q_{C_estrella}$
e.ii) Si, ya que $\cos \varphi_2 < 0,92$

f)

■ IEC 60831 → Establece (entre otros) los siguientes requerimientos:

- $U_{rms} < 1,1 Un$
- $I_{rms} < 1,3 In$

En este caso: $U_5 = 15\% U_1$

$U_7 = 10\% U_1$

$$U_{rms} = \sqrt{\sum U_i^2} \approx \sqrt{U_1^2 + U_5^2 + U_7^2} = U_n \cdot \sqrt{1^2 + 0,15^2 + 0,1^2} = U_n \cdot 1,016 < 1,1 Un \quad \checkmark$$

$$I_{rms} = \sqrt{\sum I_i^2} \approx \sqrt{I_1^2 + I_5^2 + I_7^2} = I_n \cdot \sqrt{1^2 + (0,15 \cdot 5)^2 + (0,1 \cdot 7)^2} = I_n \cdot 1,43 > 1,3 In \quad \text{X}$$

NO CUMPLE

$$I_1 = \frac{U_1}{X_{C_1}} = \frac{U_1}{(\frac{1}{w_1 C})} = U_n \cdot w_1 \cdot C = I_n$$

$$I_5 = \frac{U_5}{X_{C_5}} = \frac{(0,15 \cdot U_n)}{(\frac{1}{w_5 C})} = 0,15 \cdot U_n \cdot w_5 \cdot C = 0,15 \cdot U_n \cdot (5 \cdot w_1) \cdot C = (0,15 \cdot 5) \cdot I_n$$

$$I_7 = \frac{U_7}{X_{C_7}} = \frac{(0,1 \cdot U_n)}{(\frac{1}{w_7 C})} = 0,1 \cdot U_n \cdot w_7 \cdot C = 0,1 \cdot U_n \cdot (7 \cdot w_1) \cdot C = (0,1 \cdot 7) \cdot I_n$$