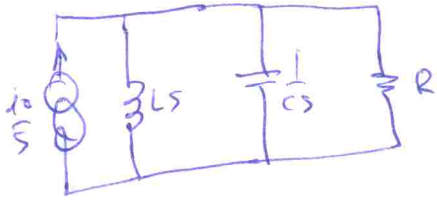


4.

a



$$Z_T := \frac{1}{1/R + cs + \frac{1}{Ls}} = \frac{RLs}{Ls + R + RLcs^2} = \frac{\frac{1}{c}s}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

$$\frac{1}{LC} = \frac{R}{L} \cdot \frac{1}{RC} = \omega_n^2 \Rightarrow Z_T = \frac{\frac{1}{c}s}{s^2 + \omega_n s + \omega_n^2}$$

$$V_c(s) = Z_T \cdot \frac{i_0}{s} \Rightarrow V_c(s) = \frac{\frac{i_0}{c}}{s^2 + \omega_n s + \omega_n^2}$$

dimensions:

$$[V_c] = \frac{i_0}{c s^2} = \frac{R i_0}{RC s^2} = \frac{V}{T s^2} = \frac{V}{s} \checkmark$$

$$I_L(s) = I_c + I_R = Cs V_c(s) + \frac{V_c(s)}{R} = \frac{1+RCs}{R} V_c(s) = \frac{s + \frac{1}{RC}}{\frac{1}{c}} V_c(s)$$

$$\Rightarrow I_L(s) = \frac{s + \omega_n}{1/c} \frac{i_0/c}{s^2 + \omega_n s + \omega_n^2}$$

$$\Rightarrow I_L(s) = \frac{(s + \omega_n) i_0}{s^2 + \omega_n s + \omega_n^2}$$

b) TVI  $f(0) = \lim_{s \rightarrow \infty} sF(s)$

TVF  $f(+\infty) = \lim_{s \rightarrow 0} sF(s)$  si  $sF(s)$  no tiene polos RHP.

$$i_L(0) = \lim_{s \rightarrow \infty} sI_L(s) = i_0 \quad \checkmark$$

$$i_L(+\infty) = \lim_{s \rightarrow 0} sI_L(s) = 0 \quad \checkmark \quad \text{cierra pues la energía se disipa por la resistencia.}$$

$$v_C(0) = \lim_{s \rightarrow \infty} sV_C(s) = 0 \quad \checkmark \quad \text{c.f. nula.}$$

$$v_C(+\infty) = \lim_{s \rightarrow 0} sV_C(s) = 0 \quad \checkmark \quad \text{idem}$$

c. & la tabla :  $\frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} \rightarrow \frac{\omega_n}{\sqrt{1-\zeta^2}} e^{-\zeta\omega_n t} \sin(\omega_n \sqrt{1-\zeta^2} t)$

$$2\zeta\omega_n = \omega_n \Rightarrow \zeta\omega_n = 1/2 \Rightarrow \sqrt{1-\zeta^2} = \sqrt{3/4} = \frac{\sqrt{3}}{2}$$

$$\omega_d \stackrel{D}{=} \frac{\sqrt{3}}{2} \omega_n.$$

$$\Rightarrow v_C(t) = \frac{i_0}{C\omega_n^2} \int_0^t \left[ \frac{\omega_n^2}{s^2 + \omega_n s + \omega_n^2} \right] = \frac{i_0}{C\omega_n^2} \frac{\omega_n^2}{\sqrt{3}} e^{-\frac{\omega_n}{2}t} \sin \omega_d t$$

$$\Rightarrow v_C(t) = \frac{2R i_0}{\sqrt{3}} e^{-\frac{\omega_n}{2}t} \sin \omega_d t \quad \forall t \in [0, +\infty)$$

$\uparrow$   
 $C\omega_n = \frac{1}{R}$

$$I_L(s) = C(s + \omega_n) V_C(s)$$

$$\Rightarrow i_L(t) = C \frac{dv_C(t)}{dt} + C\omega_n v_C(t)$$

$$= C \cdot \frac{2}{\sqrt{3}} R i_0 \left[ -\frac{\omega_n}{2} e^{\frac{\omega_n t}{2}} \sin \omega_d t + e^{\frac{\omega_n t}{2}} \cos \omega_d t \cdot \omega_d \right]$$

$$+ C\omega_n \frac{2}{\sqrt{3}} R i_0 e^{\frac{\omega_n t}{2}} \sin \omega_d t$$

$$= R C \omega_n \frac{2}{\sqrt{3}} i_0 \cdot \left[ \left( -\frac{1}{2} + 1 \right) \sin \omega_d t + \frac{\sqrt{3}}{2} \cos \omega_d t \right] e^{\frac{\omega_n t}{2}}$$

$$\omega_d = \frac{\sqrt{3}}{2} \omega_n \quad \Rightarrow \quad i_L(t) = \frac{2}{\sqrt{3}} i_0 \left[ e^{\frac{\omega_n t}{2}} \right] \left[ \frac{1}{2} \sin \omega_d t + \frac{\sqrt{3}}{2} \cos \omega_d t \right]$$

$$\Rightarrow \boxed{i_L(t) = \frac{i_0}{\sqrt{3}} e^{\frac{\omega_n t}{2}} (\sin \omega_d t + \sqrt{3} \cos \omega_d t) \quad \forall t \in [0, \infty]}$$

El primer máximo de  $v_C(t)$  se da en  $\sin \omega_d t^0 = 1 \Rightarrow \omega_d t^0 = \pi/2$

$$\Rightarrow t^0 = \frac{\pi/2}{\frac{\sqrt{3}}{2} \omega_n} \quad \boxed{t^0 = \frac{\pi}{\sqrt{3} \omega_n}}$$

$$e^{-\frac{\omega_n t^0}{2}} = e^{-\frac{\pi}{\sqrt{3} \cdot 2}} \quad \Delta = \rho$$

$$\sin \omega_d t^0 = 1$$

$$\cos \omega_d t^0 = 0$$

$$\text{En } t^0 \quad N_c(t^0) = \frac{2R i_0}{\sqrt{3}} \beta, \quad i_L(t^0) = \frac{\beta i_0}{\sqrt{3}}$$

$\forall t > t^0$

$$\boxed{i_L(t) = 0 \quad \forall t > t^0}$$

$$N_c(t) = N_c(t^0) e^{-\frac{(t-t^0)}{R_c}}$$

$$\Rightarrow \boxed{N_c(t) = \frac{2}{\sqrt{3}} \beta R i_0 e^{-\frac{(t-t^0)}{R_c}} \quad \forall t > t^0}$$

$$N_s(t) = \underset{\uparrow}{N_c(t)} + L \frac{di_c}{dt} = \begin{cases} 0 & \forall t < t^0 \\ N_c(t) & \forall t > t^0 \end{cases} + L \left[ -\frac{\beta i_0}{\sqrt{3}} \right] \delta(t-t^0)$$

