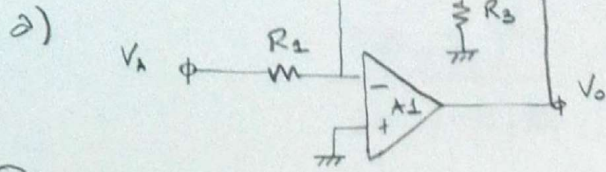


Ej. 3




$$G = \frac{V_O}{V_A} ; A_1 \text{ ideal}$$

(N):

$$\left. \begin{aligned} \frac{V_A}{R_1} &= \frac{V_N}{R_3} + \frac{(V_N - V_O)}{R_4} \\ V_N &= -\frac{R_2}{R_1} V_A \end{aligned} \right\} \Rightarrow \frac{V_O}{V_A} = -\frac{R_2}{R_1} \left( 1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right) = G$$

b)
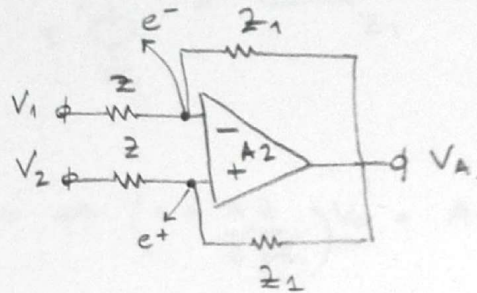
$$A_2 \begin{cases} R_i = \infty \\ r_o = 0 \\ A \text{ finita} \end{cases}$$




b)

$$V_O = A(e^+ - e^-)$$

$$\left. \begin{aligned} e^+ &= V_O + \frac{z_1}{z_1 + z_2} (V_2 - V_O) = \frac{z_2}{z_1 + z_2} V_O + \frac{z_1}{z_1 + z_2} V_2 \\ e^- &= \frac{z_2}{z_1 + z_2} V_O + \frac{z_1}{z_1 + z_2} V_1 \end{aligned} \right\} \Rightarrow V_O = \frac{A z_1}{z_1 + z_2} (V_2 - V_1)$$

bii)

$$z_{Th1} = \frac{E}{I}$$

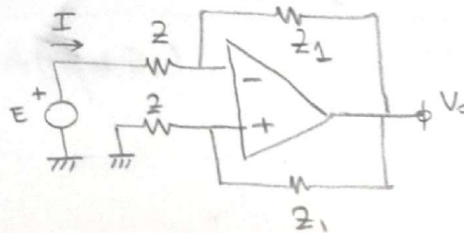

$$\left. \begin{aligned} e^+ &= \frac{z_2}{z_1 + z_2} V_O \\ e^- &= E - z_2 I \end{aligned} \right\} \Rightarrow \begin{aligned} V_O &= \frac{A z_2}{z_1 + z_2} V_O - A E + A z_2 I \\ V_O &= E - (z_1 + z_2) I \end{aligned} \Rightarrow$$

$$\Rightarrow z_{Th1} = \frac{E}{I} = \frac{(z_1 + z_2)^2}{z_1 + (1+A)z_2}$$


Análogamente,

$$z_{Th2} = \frac{(z_1 + z_2)^2}{z_2 + z_1(1-A)}$$



Ej 3 (P12016)

c)

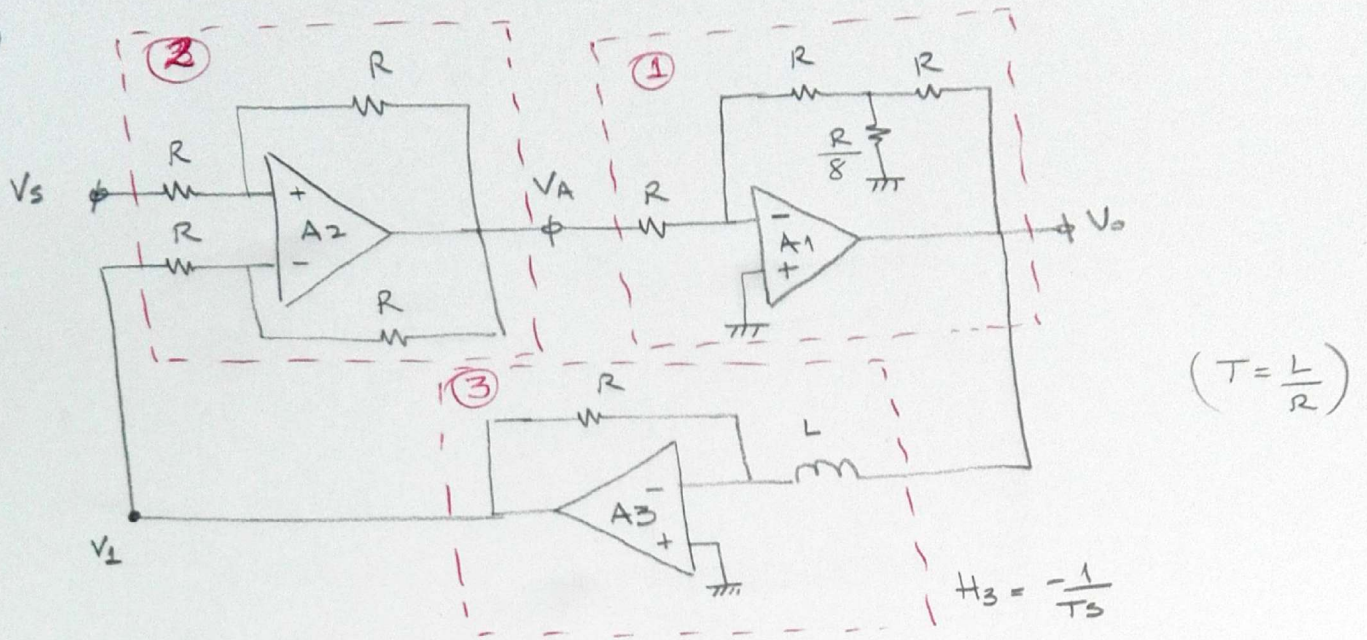

③:  $V_1 = -\frac{V_o}{Ts}$

②:  $V_A = \frac{A}{2} (V_s - V_1)$

①:  $G = -\frac{R}{R} \left( 1 + \frac{R}{R} + \frac{8R}{R} \right) = -10$

$V_o = G V_A$

$\Rightarrow V_o = G \frac{A}{2} V_s + G \frac{A}{2} \frac{V_o}{Ts}$

$\Rightarrow \left[ \frac{V_o}{V_s} = \frac{\frac{GA}{2} \cdot s}{s - \frac{GA}{2T}} \right]$