
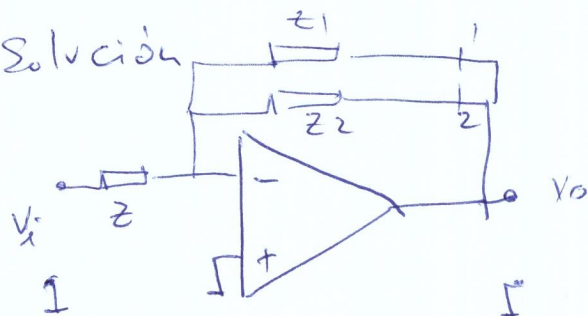


Problema 3. Solución

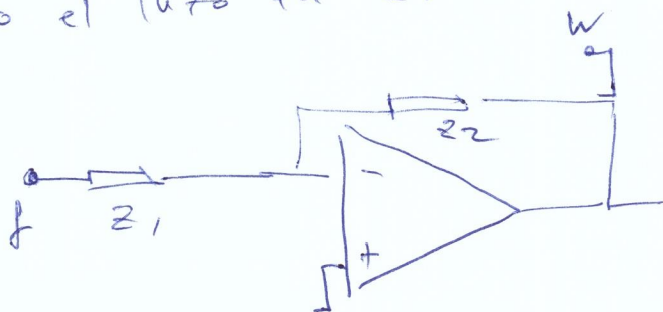

a. abro el lazo en 1:



$$G_{ol1} = \frac{W(s)}{F(s)} = - \frac{Z_2(s)}{Z_1(s)}$$

b. Caso 2: $G_{ol2} = - \frac{Z_1(s)}{Z_2(s)}$

c. $1 + A\beta_1 = 1 - G_{ol1} = 1 + \frac{Z_2}{Z_1}$

$$1 + A\beta_2 = 1 - G_{ol2} = 1 + \frac{Z_1}{Z_2}$$

$$\left\{ \text{ceros de } 1 + A\beta_1 \right\} = \left\{ \text{ceros de } 1 + A\beta_2 \right\} = \left\{ \text{ceros de } Z_1 / Z_2(s) \right\}$$

d $Z_1 = \frac{R + 1/s}{R + 1/s} = \frac{1 + RCs}{Cs} = \frac{1 + Ts}{Cs}$

$$Z_2 = \frac{RLs}{R + Ls} = \frac{Ls}{1 + \frac{L}{R}s} = \frac{Ls}{1 + Ts}$$

d. (cont).

$$L_1 = -G_{ol1} = + \frac{Z_2(s)}{Z_1(s)} = \frac{L C s^2}{(1+Ts)^2}$$



$$L_2 = -G_{ol2} = \frac{Z_1(s)}{Z_2(s)} = \frac{(1+Ts)^2}{L C s^2}$$

$$\lim_{s \rightarrow \infty} L_1(s) = \frac{L C}{T^2} \neq -1$$

⇒ ambas bien plantados.

$$\lim_{s \rightarrow \infty} L_2(s) = \frac{T^2}{L C} \neq -1$$

e. $L_1(s) = \frac{L C s^2}{(1+Ts)^2}$

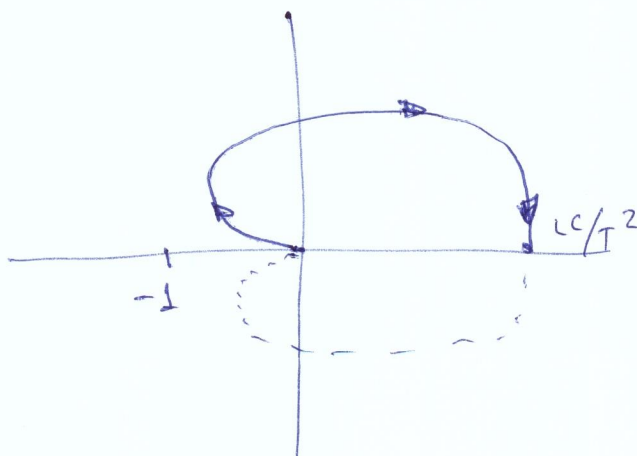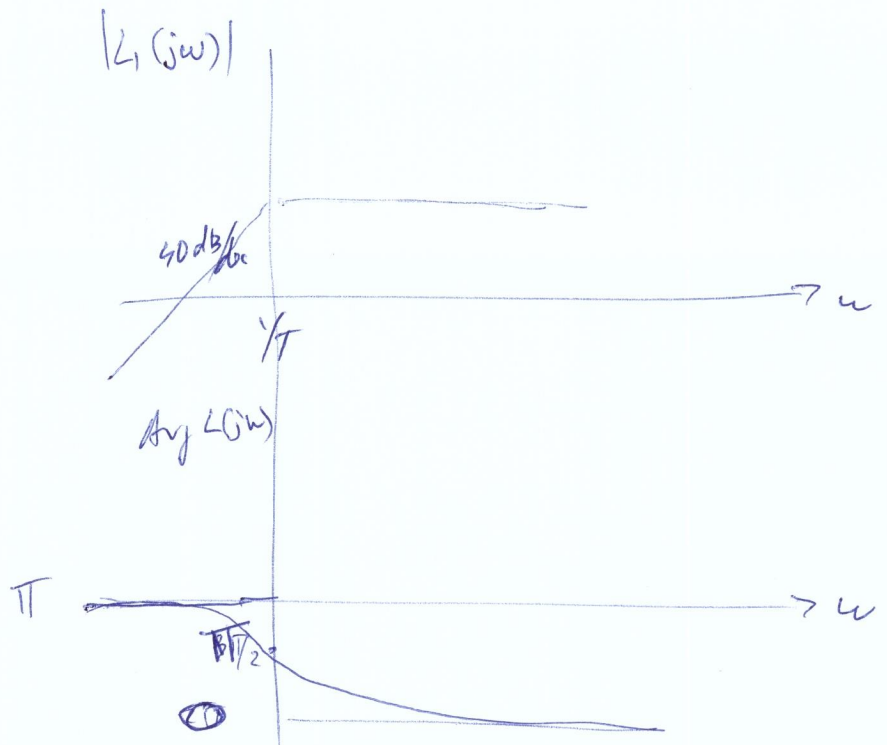


$$L_1(j\infty) = \frac{L C}{T^2}$$

$$N=0, \text{ como } P=0$$

$$\Rightarrow Z=0$$



$$f. L_2(s) = \frac{(1+Ts)^2}{LCs^2}$$

polo doble en el origen

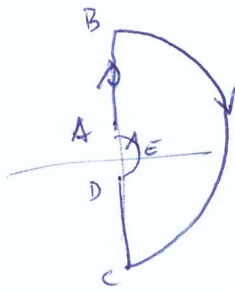

Arro E-A
 $s = re^{j\theta} \quad \theta \in [0, \pi/2]$
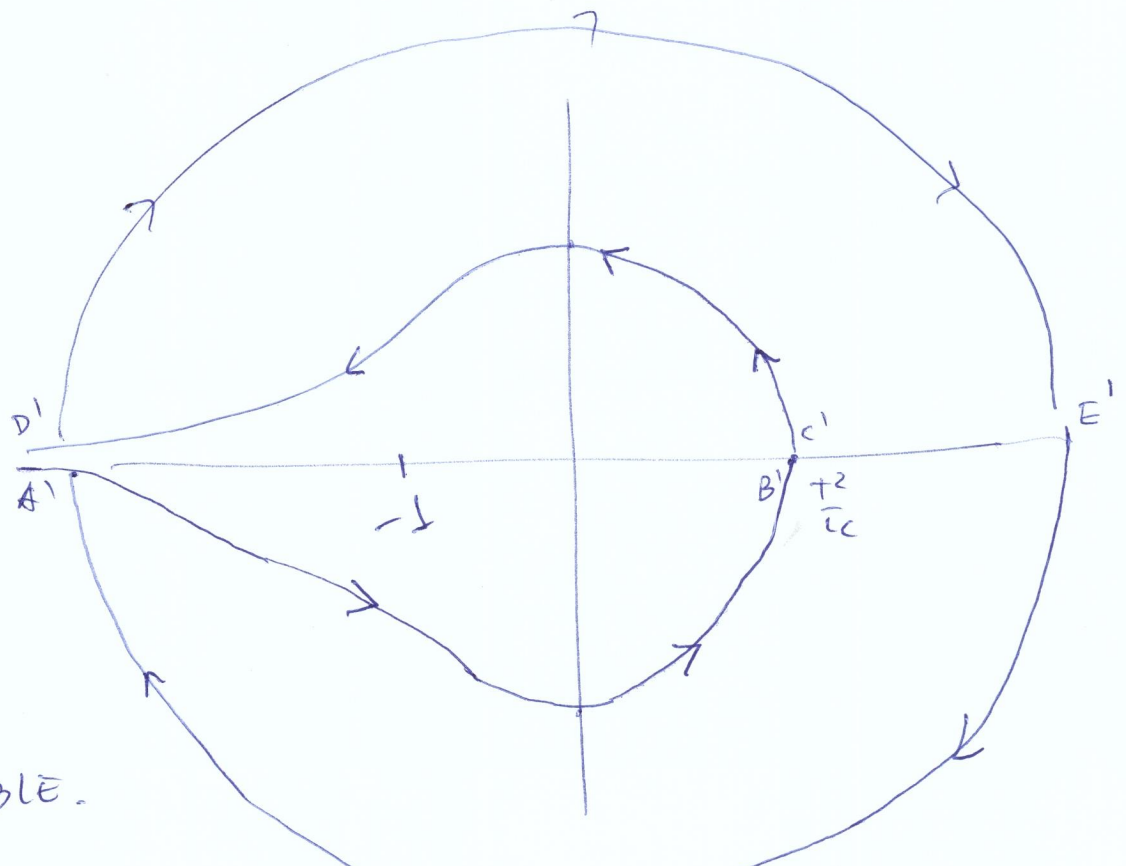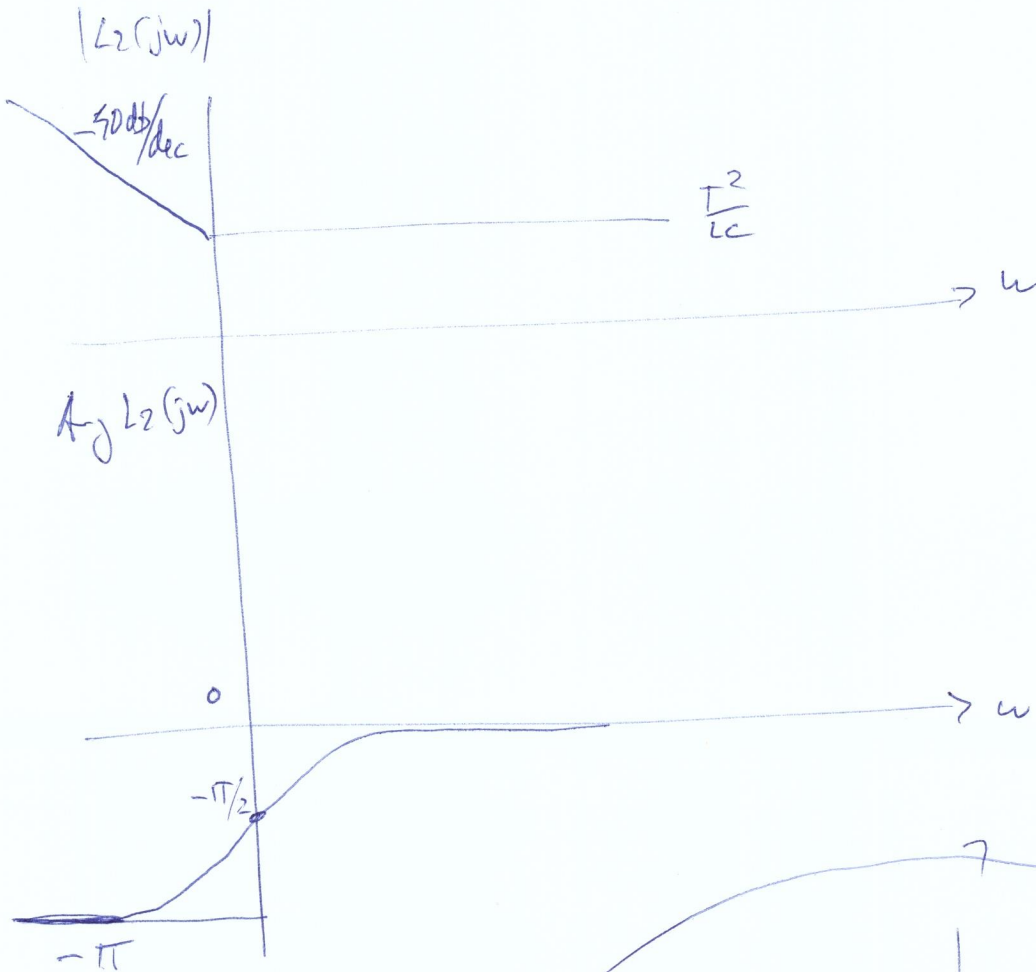
$$L(s) = \frac{1}{LCr^2} e^{-2j\theta} \quad r \rightarrow 0$$



$N=0$
 Como $P=0$

\Rightarrow BIBO ESTABLE.