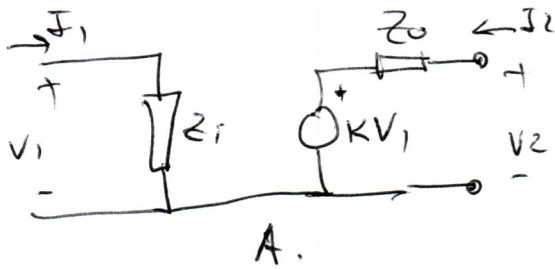


Problema 3. Die 2017. Solución

†


a.



$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \mathcal{Z} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


$$\mathcal{Z}_A = \begin{bmatrix} z_i & 0 \\ k z_i & z_o \end{bmatrix}$$

NO
Reciprocó
si $k z_i \neq 0$.

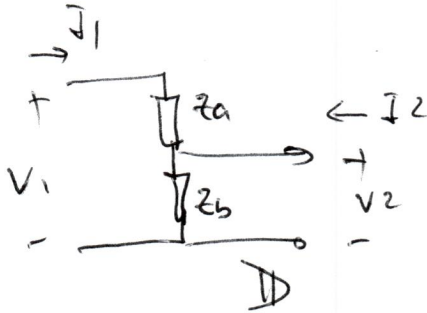

$$\mathcal{Z}_D = \begin{bmatrix} z_a + z_b & z_b \\ z_b & z_b \end{bmatrix} \text{ Reciprocó}$$

b. AD

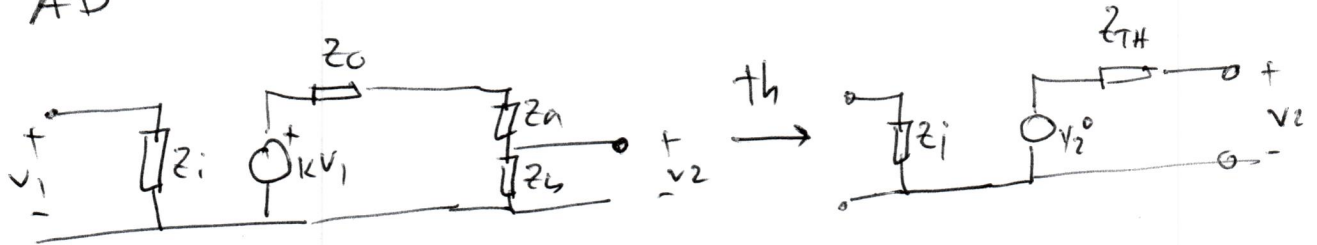


$$V_2 \text{ en vacío : } V_2^0 = \frac{z_b}{z_a + z_b + z_o} \cdot k V_1$$

$$z_{TH} = z_b \parallel z_a + z_o$$

$$\mathcal{Z}_{AD} = \begin{bmatrix} z_i & 0 \\ \frac{k z_b z_i}{z_a + z_b + z_o} & z_b \parallel z_a + z_o \end{bmatrix}$$

DA



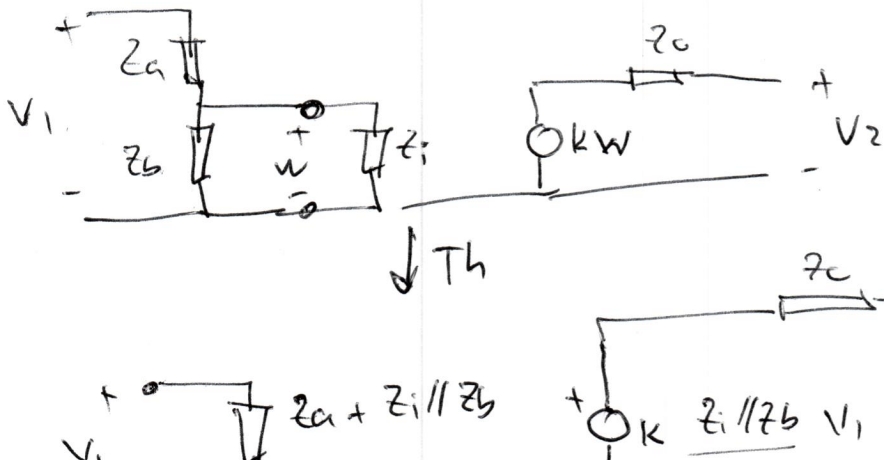


$$\mathcal{Z}_{DA} = \begin{bmatrix} z_a + z_i \parallel z_b & 0 \\ z_{21} & z_o \end{bmatrix}$$



b.

AA

#

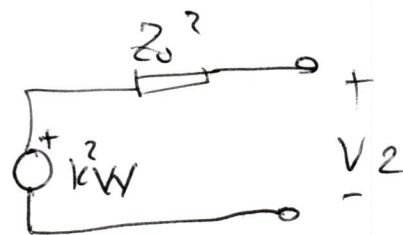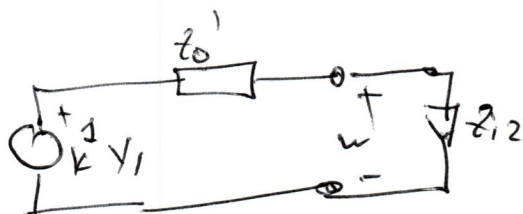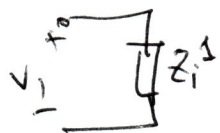



↓ TH

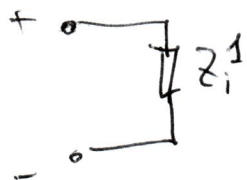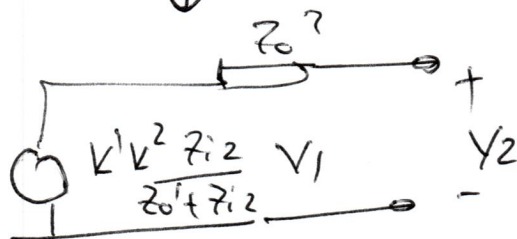

$$k^2 W = \frac{k^2 Zi2}{Zo1 + Zi2} k^1 V1$$

$$Z_{AA} = \begin{bmatrix} Zi1 & 0 \\ \frac{k^1 k^2 Zi2 Zi1}{Zo1 + Zi2} & Zo2 \end{bmatrix}$$

c

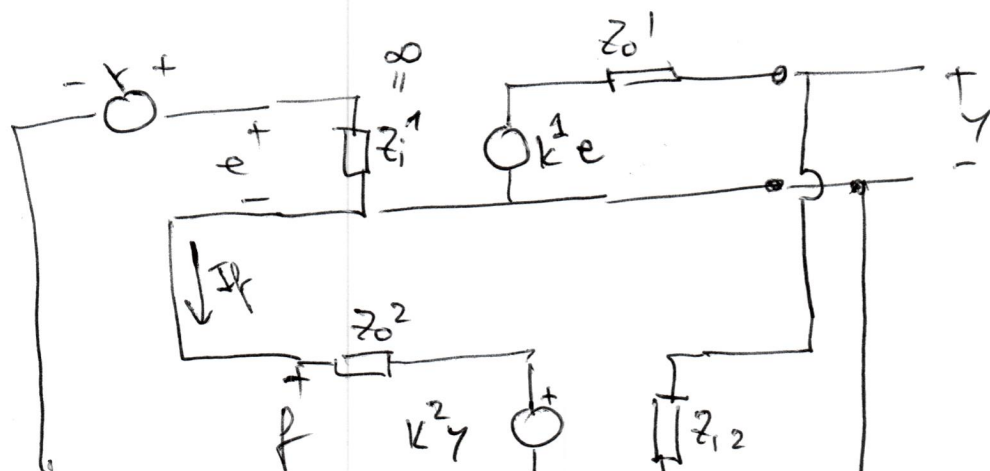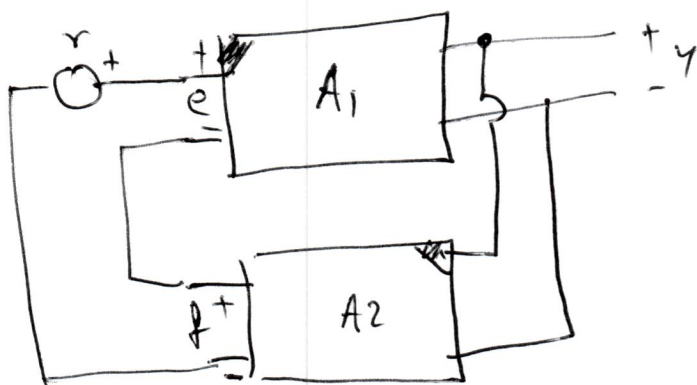

EN LA MALA DE LA IZQUIERDA:

III

$$E(s) = R(s) - F(s) \quad (1)$$

$$I_f = 0 \text{ ya que } Z_1 = \infty \Rightarrow F(s) = k^2 Y(s)$$


$$C(s) = \frac{F(s)}{Y(s)} = k^2 \quad (2)$$

k^2 es la ganancia k del cuadripolo 2, y no $k \times k$!



$$Y(s) = k^1 E(s) \frac{Z_{12}}{Z_{12} + Z_{01}}$$

$$\Rightarrow H(s) = \frac{Y(s)}{E(s)} = \frac{k^1 Z_{12}}{Z_{12} + Z_{01}} \quad (3)$$

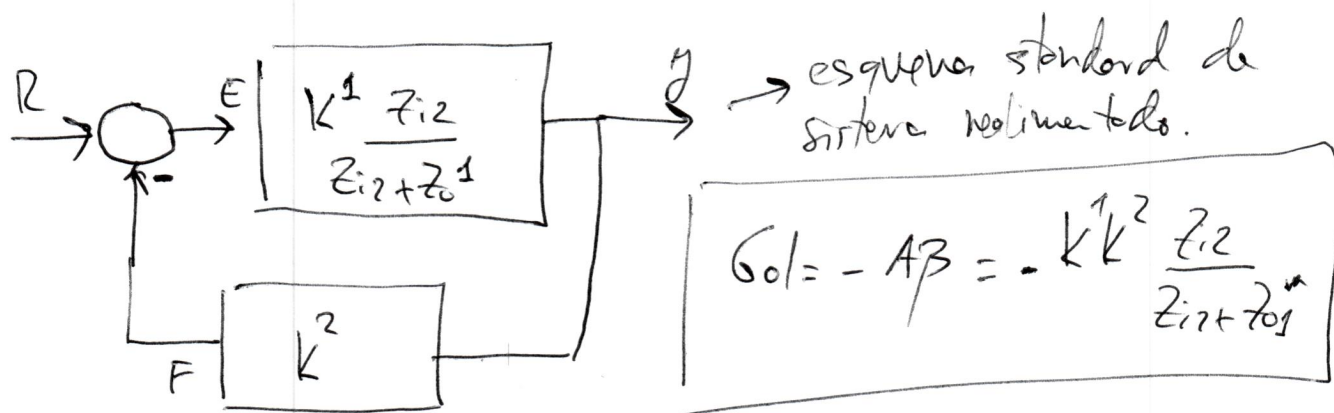El diagrama de bloques consiste en representar (1), (2), (3) gráficamente



e) modo 1

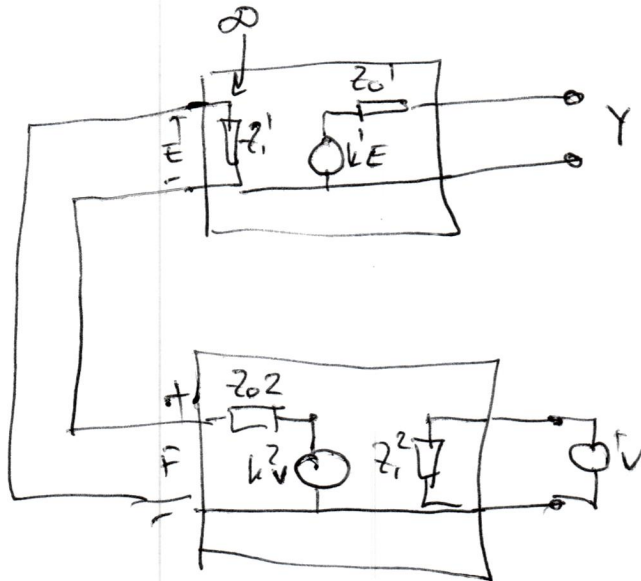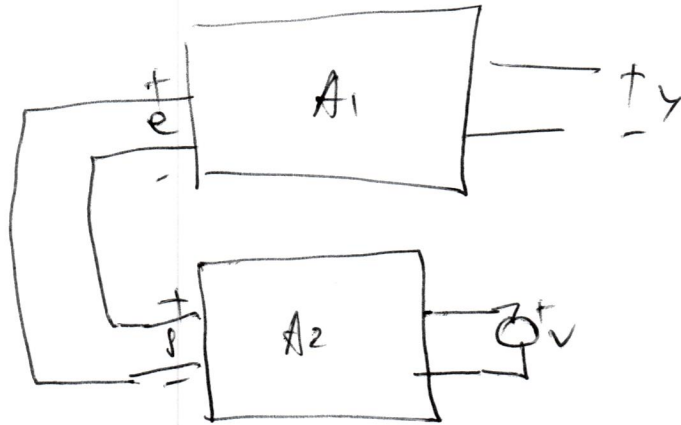

$$\begin{aligned} F &= k^2 V \\ E &= -F \\ Y &= k^1 E \end{aligned}$$

$$\Rightarrow \frac{Y}{V} = -k^1 k^2 = G_1$$

$G_0 = G_1$ solo si

$$\frac{z_{12}}{z_{12} + z_{01}} = 1$$

que ocurre solo si $z_{01} = 0$ o $z_{12} = \infty$.

modo 2

ida pero $Y(s) = \frac{z_a}{z_a + z_{01}}$

$$G_2 = -k^1 k^2 \frac{z_a}{z_a + z_{01}}$$

$G_2 = G_0$ si eligimos

$$z_a = z_{12}$$

