
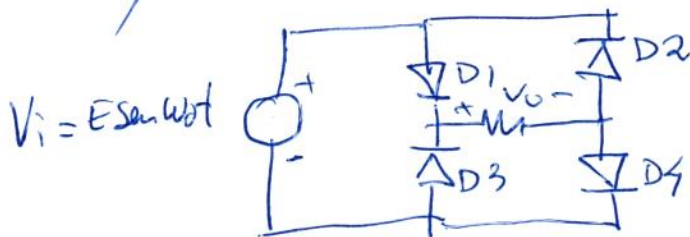


Problema 1.

a)

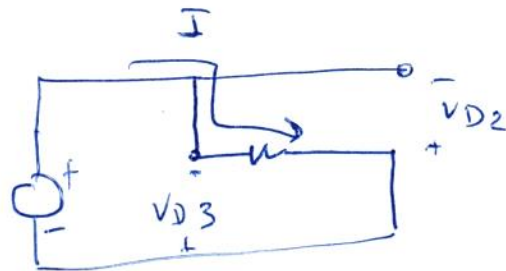

Si  $V_i > 0$   $D_1, D_3$  ON,  $D_2, D_4$  OFF




$$I = \frac{V_i}{R} > 0 \quad I_{D1} = I_{D3} = I > 0 \checkmark$$

$$V_{D3} = V_{D2} < 0 \checkmark$$


Si  $V_i < 0$   $D_2, D_4$  ON,  $D_1, D_3$  OFF


$$I = \frac{V_i}{R} < 0$$

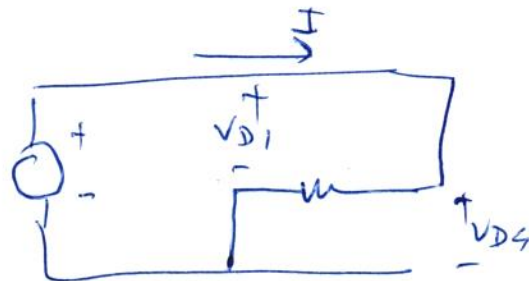

$$I_{D2} = I_{D4} = -I > 0 \checkmark$$

$$V_{D1} = V_{D3} = V_i < 0 \checkmark$$

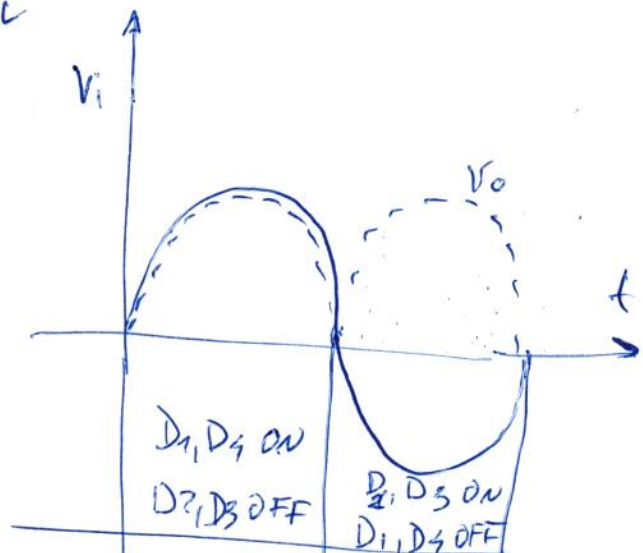

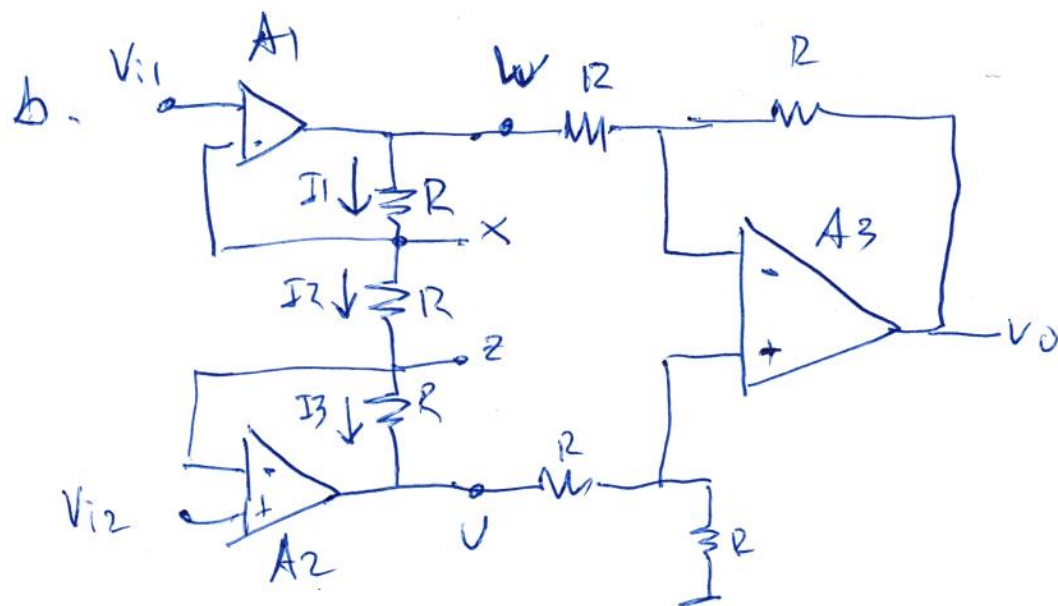

A3 es un amplificador diferencial respecto de  $W, U$ :

$$V_o = U - W.$$

Se cumple  $I_1 = I_2 = I_3$

y las tensiones  $X = V_{i1}$   $Z = V_{i2}$  por tierra virtual de  $A_1, A_2$


$$\Rightarrow I_2 = \frac{X - Z}{R} = \frac{V_{i1} - V_{i2}}{R} \quad y$$

$$W - U = 3R I_2 = 3[V_{i1} - V_{i2}]$$

$$\Rightarrow \boxed{V_o = -3[V_{i1} - V_{i2}]}$$

# Problema 4

Torno 1

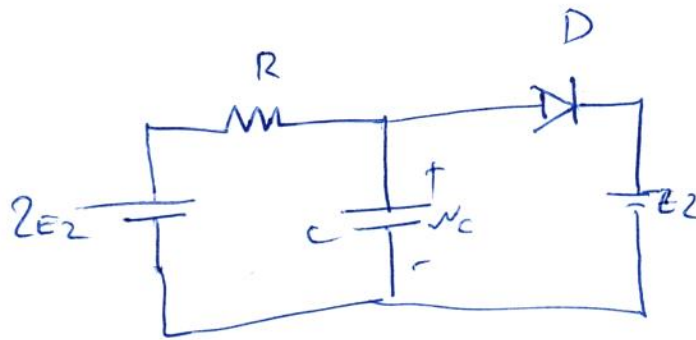


$V_c$  inicialmente  $V_c = 0$

D OFF  $V_c = 2E2 (1 - e^{-t/\tau})$   $\tau = RC$

Se verifica  $V_D = V_c - E2 < 0$

$\Rightarrow V_c < E2$

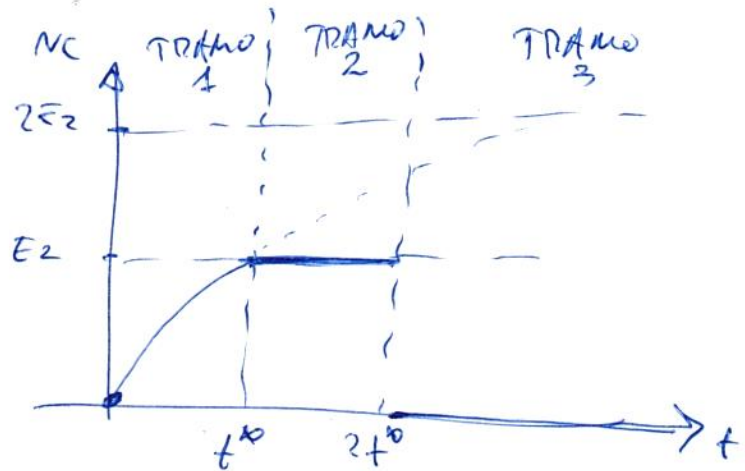


$t^*$  es tal que

$V_c(t^*) = E2$

$2E2 (1 - e^{-t^*/\tau}) = E2$

Torno 2  $\Rightarrow t^* = \tau \ln 2$

$t > t^*$  D ON

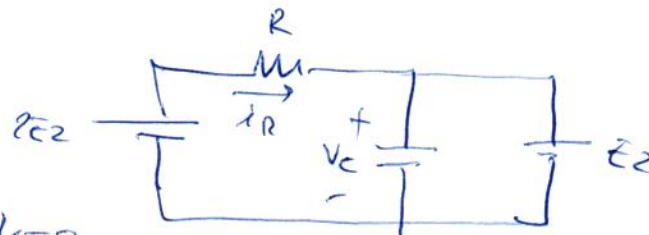


$V_c = E2$   $\Rightarrow i_c = 0$

$i_R = \frac{E2}{R}$

$i_D = i_R > 0 \quad \checkmark$

Trans 3  $t > 2t^0$

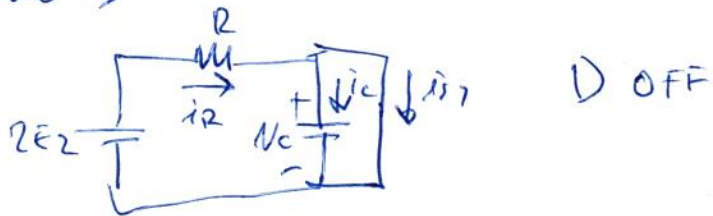

$$\begin{cases} i_R = \frac{2E_2}{R} & \forall t > 2t^0 \\ v_C = 0 \end{cases}$$

$$i_C = C \frac{dv_C}{dt} = -CE_2 \delta(t - 2t^0)$$

$$i_{S2} = i_R - i_C = \frac{2E_2}{R} + CE_2 \delta(t - 2t^0)$$

