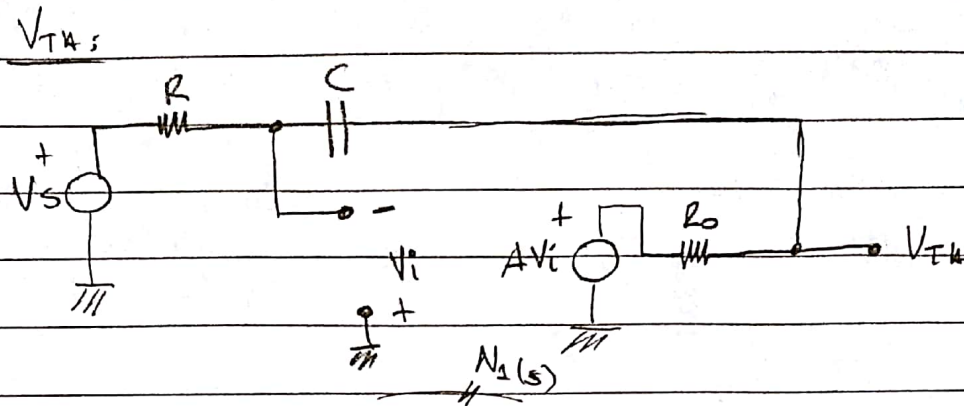


Problema 3

2)



$$V_{TH}(s) = \frac{R_o V_s + (1/s + R) A V_i}{R_o + R + 1/s}$$

$$D(s)$$

$$V_i = \frac{N_2(s)}{D(s)}$$


$$-V_i(s) = \frac{R A V_i(s) + (R_o + 1/s) V_s}{R_o + R + 1/s}$$

$$D(s)$$

$$\Rightarrow V_i(s) = \frac{N_2(s) V_s}{D(s) [D(s) - R A]}$$

$$\Rightarrow V_{TH}(s) = \frac{D(s) [D(s) - R A] R_o + N_1(s) N_2(s) A}{D(s)^2 [-D(s) - R A]} V_s$$

Z_TH:

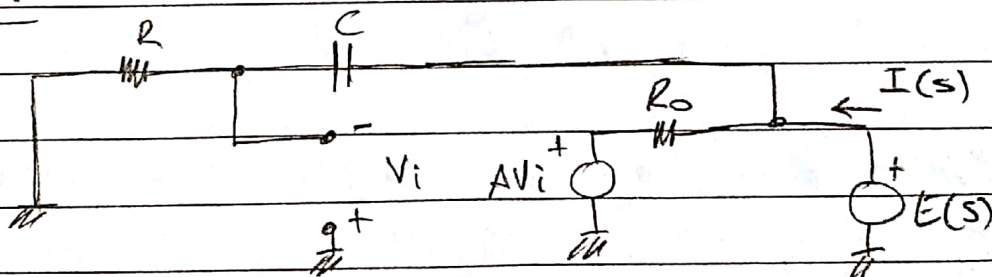

$$I(s) = \frac{E - A V_i}{R_o} + \frac{E}{N_1(s)} ; V_i = -\frac{R}{N_1(s)} E$$

$$\Rightarrow Z_{TH}(s) = \frac{R_o N_1(s)}{N_1(s) + A R + R_o}$$

b)

$$Z_{TH} = 0 \Omega \text{ (op. ideal)}$$

$$V_{TH} = V_y(s) = C(sI - A)^{-1} B V_i(s)$$

$$= [1 \ 0] \begin{bmatrix} \frac{1}{s+2} & \frac{4}{(s+1)(s+2)} \\ 0 & \frac{1}{(s+1)} \end{bmatrix} \begin{bmatrix} 1 \\ 1 \end{bmatrix} V_i(s)$$

$$= \left(\frac{1}{s+2} + \frac{4}{(s+1)(s+2)} \right) V_i(s) = \frac{s+5}{(s+1)(s+2)} V_i(s)$$

c)

$$i.) \quad I(s) = \frac{V_{TH}^1 - V_{TH}^2}{Z_{TH}^1}$$

$$\begin{cases} V_1(s) = sL_1 I_1(s) + M s I_2(s) \\ V_2(s) = sL_2 I_2(s) + M s I_1(s) \end{cases}$$

Donc :

$$V_1(s) = V_{TH}^1 ; \quad I_2(s) = - \frac{V_2(s)}{R}$$

$$\Rightarrow \left| V_2(s) = \frac{MR}{L_1 R + s(L_1 L_2 - M^2)} V_{TH}^1 \right|$$

$$V_o(s) = -V_2(s) = \frac{-MR}{L_1 R + s(L_1 L_2 - M^2)} \frac{(s+5)}{(s+1)(s+2)} V_i(s)$$

$$H(s)$$

ii.) Transfère en propre (extra)

$$\text{poles : } \left\{ -1, -2, \frac{-L_1 R}{L_1 L_2 - M^2} \right\} \quad \left\{ \text{SI BIBO} \right\}$$