

## Prob 2

- a. Def reciprocidad. ver teórico del curso  
 b. El cuadripolo tiene una fuente dependiente. No se puede aplicar el teorema


$$c. \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{1}{R_1 + R_2}$$

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = \frac{1}{Ls}$$

$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = 0$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

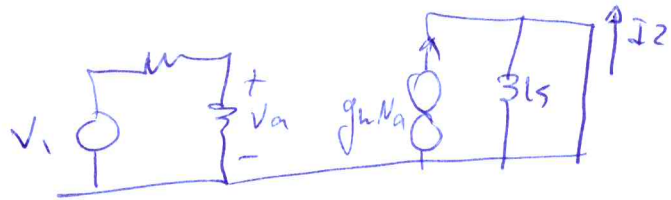


$$V_a = \frac{R_2}{R_1 + R_2} V_1$$

$$I_2 = -g_m N_a = -\frac{g_m R_2}{R_1 + R_2} V_1$$


$$\Rightarrow Y_{21} = -\frac{g_m R_2}{R_1 + R_2}$$

2

2

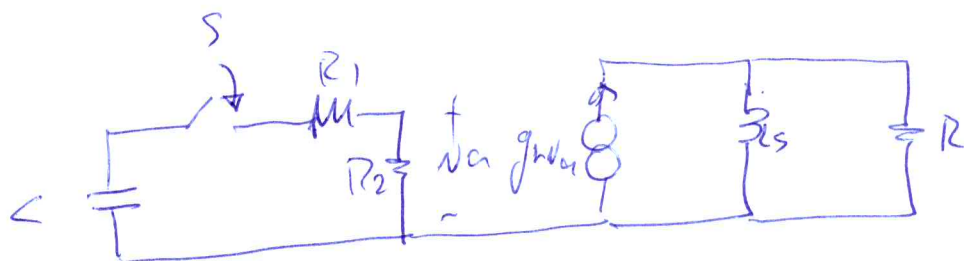

find  $v_2$  for  $0 \leq t < L/R$ .

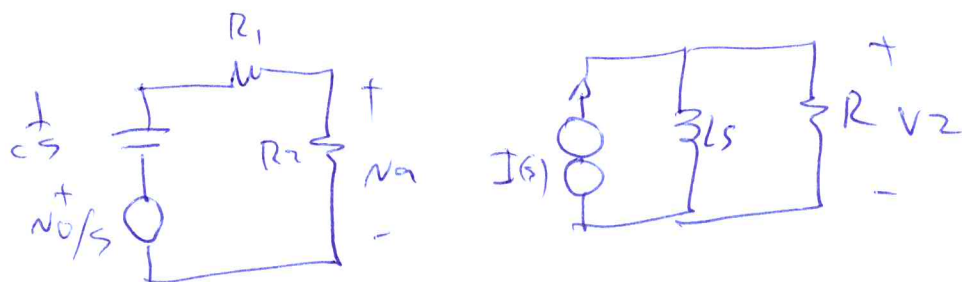

$$V_2(s) = \frac{V_0}{s} \cdot \frac{R_2}{R_1 + R_2 + 1/s} = \frac{R_2 C s}{R C s + 1} \cdot \frac{V_0}{s} = \frac{R_2 C V_0}{R C s + 1}$$

$$V_2(s) = \frac{L s}{R + L s} I(s) = \frac{L s}{R + L s} g_m \frac{R_2 C V_0}{R C s + 1}$$

$$= \frac{g_m R_2 L C V_0 s}{(R + L s)(R C s + 1)} = \frac{g_m \frac{R_2}{R} V_0 s}{\left(s + \frac{R}{L}\right)\left(s + \frac{1}{R C}\right)}$$

$$\left\{ \begin{array}{l} V_2(t) = V_0 e^{-\frac{t}{RC}} \quad t \in [0, L/R] \\ V_2(t) = g_m \frac{R_2 V_0}{R} [1 - e^{-\omega_0 t}] e^{-\omega_0 t} \quad t \in [L/R, \infty) \end{array} \right.$$


$$\frac{R}{L} = \frac{1}{RC} \triangleq \omega_0$$

TRAMO 2  $t \geq L/R = RC = \omega_0^{-1}$

3

$$\begin{cases} v_0(t) = 0 \\ v_c(t) = v_c(L/R) = v_0/e \end{cases}$$

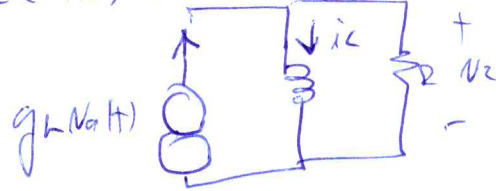Precisamos el dato previo:  $i_L(L/R)$  antes de abrir la llave



$$i_L(t) = g_m v_0(t) - \frac{v_2(t)}{R}$$

$$\Rightarrow i_L(L/R) = \underset{\text{en el tramo I}}{g_m v_0(L/R)} - \frac{v_2(L/R)}{R} = g_m \frac{v_0 R_2}{R} e^{-t/LR} - \underbrace{g_m \frac{R_2 v_0}{R} \left(1 - \frac{\omega_0}{\omega_0}\right)}_{=0} e^{-t/LR}$$

$$\Rightarrow \boxed{i_L(L/R) = g_m \frac{R_2 v_0}{R} e^{-t/LR}}$$

$$i_L(t) = g_m \frac{R_2 v_0}{R} e^{-t/LR} \quad t \geq L/R$$

$$\boxed{v_2(t) = -R i_L(t) = -\frac{g_m R_2 v_0}{e} e^{-\omega_0(t-L/R)} \quad \forall t \geq L/R}$$

