
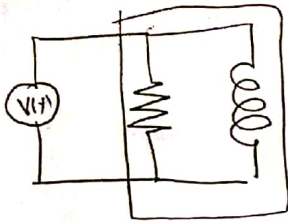


18

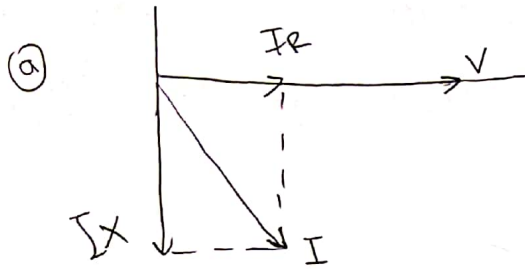

$V_{rms} = 220 \text{ 50Hz}$
 $I_{rms} = 80 \text{ A}$
 $P = 10,56 \text{ kW}$



(b) R y X

$P = V_{rms} I_{rms} \cos(\varphi) = 10,56 \text{ kW}$
 $17600 \cos(\varphi) = 10,56 \times 10^3 \text{ W}$


$\cos(\varphi) = 0,6 \rightarrow \varphi = 53,1^\circ$ → La potencia proviene solo por la resistencia

$P = VI_R = P \quad I_R = \frac{P}{V} = 48 \text{ A} \rightarrow R = \frac{V}{I_R} = 4,58 \Omega$

$I_X = I \sin(\varphi) = 64 \text{ A} \rightarrow X_A = \frac{V}{I_X} = 3,44 \Omega$

(c)

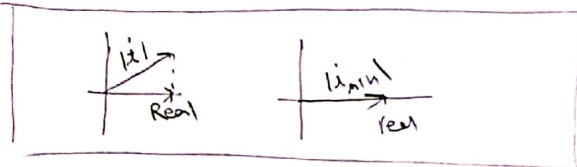$Z_T = \left[\frac{1}{R} + \frac{1}{jX} + j\omega C \right]^{-1}$ → Anular parte imaginaria para que V e I esten en fase. Entonces $\text{Im} = 0$ se cumple.




$\frac{1}{jX} + j\omega C = 0 \quad \cdot \frac{1}{X} = \omega C$

$C = \frac{1}{\omega^2 L} = 0,925 \mu\text{F}$

→ como la parte que queda en la real

$I_{rms} = 48 \text{ A} \rightarrow$ por la parte (b)

(d)

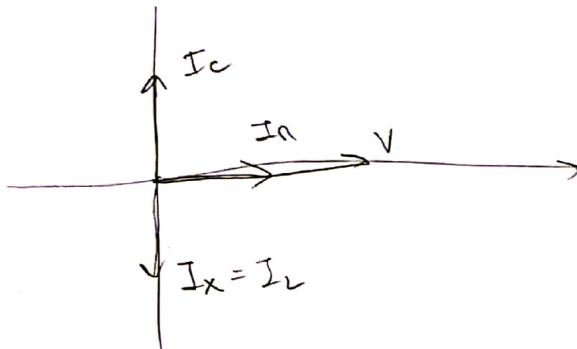


(11)

$V_0 = 300V$

$f = 50Hz$

$r = 5 \Omega$

$L = 0.1H$

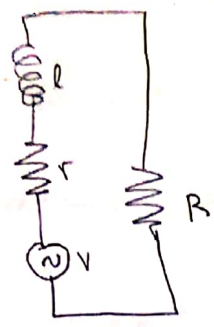

(a) $P = \frac{1}{2} \text{Re}[VI^*]$

$Z = r + R + j\omega L$

$I = \frac{V_0}{Z_T} = \frac{V_0}{r + R + j\omega L}$

$P_0 = \frac{1}{2} \text{Re} \left[\frac{V_0^2}{R_T - j\omega L} \right] = \frac{|V_0|^2}{2R_T (1 + (\frac{\omega L}{R_T})^2)}$
generador

(b)

diferencia de potencial en la resistencia

$V_R = Z_R I = \frac{RV}{r + R + j\omega L} = \frac{RV e^{j\phi_R}}{\sqrt{R_T^2 + (\omega L)^2}}$


$v_R(t) = |V_R| \cos(\omega t + \phi)$
donde $\tan \phi_R = -\frac{\omega L}{R_T}$
↓
274V

(c)

$P = \frac{1}{2} \text{Re}[Z_R |I|^2] = \frac{R |V_0|^2}{2R_T^2 (1 + (\frac{\omega L}{R_T})^2)} = 374W$

$P_0 = P_R + P_r$

(d)

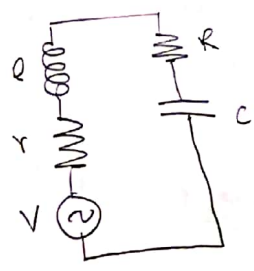

$Z'_T = Z_r + Z_R + Z_L + Z_C = (r + R + j)(\omega L - \frac{1}{\omega C})$

$I' = \frac{V_0}{Z'_T} = \frac{V_0}{R_T + j(\omega L - \frac{1}{\omega C})}$

$\bar{P}'_0 = \frac{1}{2} \text{Re}[V_0 I'^*] = \frac{|V_0|^2}{2R_T (1 + \frac{1}{R_T^2} (\omega L - \frac{1}{\omega C})^2)}$

$C = \frac{1}{\omega^2 L} = 101 \mu F$

(e)

$P'_0 = \frac{|V_0|^2}{2R_T} = 429W$

↓
 $P'_R = P'_0 \frac{R}{R_T} = 409W$