
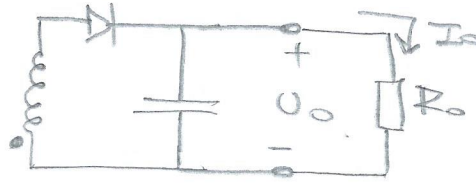


Solución Problema 2

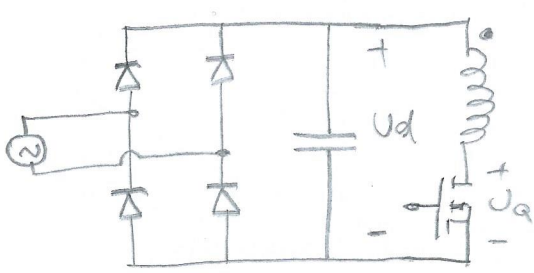


$U_o = 24V$
 $I_{o\text{máx}} = 5A$
 $f = 100kHz$

$D \rightarrow 0,12 \text{ a } 0,60$

$U_{d\text{máx}} = \sqrt{2} \cdot 230 \cdot 1,2 = 390,32V$ $T_{\text{enc}} = 40\mu s$

$U_{d\text{min}} = \sqrt{2} \cdot 110 \cdot 0,8 = 124,45V$

→ Trabajo en HCD

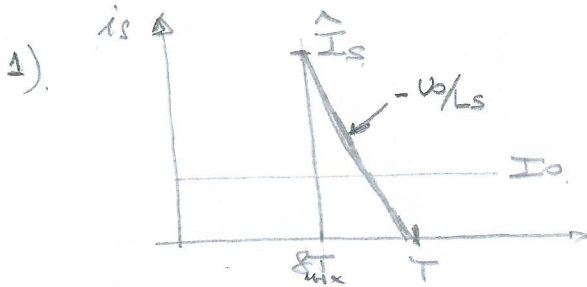

Para minimizar \hat{I}_s es necesario que a carga máxima con $U_d = U_{d\text{min}}$ el convertidor este en el LCC

$$I_o = \frac{1}{T} \int_0^T i_s dt = \frac{1}{T} \cdot \frac{1}{2} (1 - D_{\text{máx}}) T \cdot \hat{I}_s \Rightarrow I_o = \frac{(1 - D_{\text{máx}})^2}{2} \cdot \frac{U_o T}{L_s}$$

$$\hat{I}_s = \frac{U_o (1 - D_{\text{máx}}) T}{L_s}$$


$$\Rightarrow L_s = \frac{U_o (1 - D_{\text{máx}})^2}{2 I_o f} = \frac{24 (1 - 0,6)^2}{2 \cdot 5 \cdot 100 \times 10^3} \Rightarrow \boxed{L_s = 3,84 \mu H}$$

2) Corriente de pico máxima por la llave:

$P_o = 24 \cdot 5 = 120W$

Como los componentes son ideales:

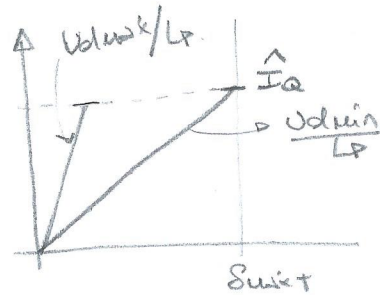$P_o = P_{in} = \frac{1}{2} \cdot L_p \cdot \hat{I}_a^2 \cdot f$



$\hat{I}_a = \frac{U_{d\text{min}} \cdot D_{\text{máx}} \cdot T}{L_p}$

$L_p = \frac{U_{d\text{min}} \cdot D_{\text{máx}} \cdot T}{\hat{I}_a} \Rightarrow P_o = \frac{1}{2} \frac{U_{d\text{min}} \cdot D_{\text{máx}}}{\hat{I}_a} \cdot \hat{I}_a^2 \cdot f$

$\hat{I}_a = \frac{2 P_o}{U_{d\text{min}} \cdot D_{\text{máx}}} = \frac{2 \cdot 120}{124,45 \cdot 0,6} = 3,21A < I_D = 7,8A$ ✓

Tensión máxima sobre la llave:

$U_q = U_d + \frac{n_p}{n_s} \cdot U_o \Rightarrow U_{q\text{máx}} = U_{d\text{máx}} + \frac{n_p}{n_s} \cdot U_o$

Solución Problema 2 (cont.)

Como se impuso LCC para carga inductiva y $U_d = U_{dmin}$


$$\Rightarrow \frac{U_o}{U_{dmin}} = \frac{n_s}{n_p} \cdot \frac{I_{aux}}{1 - I_{aux}} \Rightarrow \frac{n_s}{n_p} = \frac{(1 - I_{aux})}{I_{aux}} \frac{U_o}{U_{dmin}}$$

$$\frac{n_s}{n_p} = \frac{0,4}{0,16} \frac{24}{124,45} \Rightarrow \boxed{\frac{n_s}{n_p} = 0,129}$$

$$U_{aux} = 390,32 + \frac{24}{0,129} \Rightarrow U_{aux} = 577V < V_{DSS} = 800V. \checkmark$$

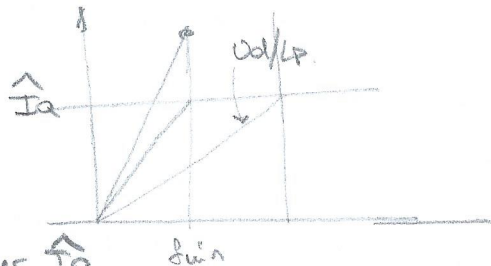3) Ahora $U_d = \sqrt{2} \cdot 230 \cdot 1,4 = 455,38V.$

$$L_p = L_s \left(\frac{n_p}{n_s} \right)^2 = \frac{3,84}{0,129^2} = 230,76 \mu H.$$




Asumo que el control puede mantener \hat{I}_a

$$\hat{I}_a = \frac{U_d}{L_p} \cdot \delta T \Rightarrow \delta = \frac{\hat{I}_a \cdot L_p \cdot f}{U_d} = \frac{3,21 \cdot 230,76 \times 10^{-6} \cdot 100 \times 10^3}{455,38}$$

$$\delta = 0,163 < \delta_{min} = 0,18.$$

$$\Rightarrow \hat{I}_a = \frac{U_d}{L_p} \cdot \delta T = \frac{455,38 \cdot 0,18}{230,76 \times 10^{-6} \cdot 100 \times 10^3} = 3,54 A < I_D = 7,8 V$$

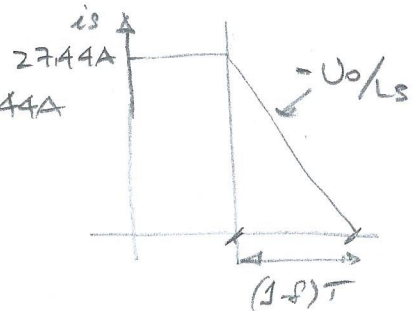Ahora $\hat{I}_s = \frac{n_p}{n_s} \cdot \hat{I}_a = \frac{3,54}{0,129} \Rightarrow \hat{I}_s = 27,44A$



$$\hat{I}_s = \frac{U_o}{L_s} (1 - \delta) \cdot T$$

$$(1 - \delta) = \frac{\hat{I}_s \cdot L_s \cdot f}{U_o} = \frac{27,44 \cdot 3,84 \times 10^{-6} \cdot 100 \times 10^3}{24}$$

$$(1 - \delta) = 0,439 \Rightarrow \boxed{\text{continúa en 4CD}}$$

$$\frac{U_o}{U_d} = \sqrt{\frac{RT}{2L_p}} \cdot \delta$$

Carga en condiciones nominales: $U_o = R \cdot I_o \Rightarrow R = \frac{24}{5} = 4,8 \Omega$

$$U_o = U_d \cdot \delta \sqrt{\frac{RT}{2L_p}} = 455,38 \cdot 0,18 \sqrt{\frac{4,8}{2 \cdot 230,76 \times 10^{-6} \cdot 100 \times 10^3}}$$

$$\Rightarrow \boxed{U_o = 26,43V}$$

Solución Problema 2 (cont.)

$$U_Q = 455,38 + \frac{26,43}{0,129} = 660,3 \text{ V} < V_{DSS} = 800 \text{ V} \checkmark$$

4) Pérdidas en el MOSFET: $P_H = P_{on} + P_{cond} + P_{off}$
 Operación MCD.

$$P_{cond} = R_{DS(on)} \cdot I_{a,eff}^2$$

$$I_{a,eff}^2 = \frac{1}{T} \int_0^T i_a^2(t) dt = \frac{1}{T} \int_0^{8T} \frac{\hat{I}_a^2}{8^2 T^2} \cdot t^2 dt = \frac{1}{T} \frac{\hat{I}_a^2}{8^2 T^2} \frac{8^3 T^3}{3}$$

$$P_{cond} = \frac{\hat{I}_a^2 \cdot 8}{3}$$

$$P_{off} = \frac{1}{2} \cdot U \cdot \hat{I}_a \cdot t_f \quad \Rightarrow \quad P_{off} = \frac{1}{2} \left(U_d + \frac{n_p}{n_s} U_o \right) \cdot \hat{I}_a \cdot t_f$$

$$U = U_d + \frac{n_p}{n_s} U_o$$

$$P_{MOSFET} = \frac{\hat{I}_a^2 \cdot 8}{3} + \frac{1}{2} \left(U_d + \frac{n_p}{n_s} U_o \right) \hat{I}_a \cdot t_f$$

Expreso P_{MOSFET} en función de U_d para analizar su evolución:


$$\frac{\hat{I}_a}{L_p} = \frac{U_d \cdot 8T}{L_p} \Rightarrow s = \frac{L_p \cdot \hat{I}_a}{U_d T}$$

$$P_{MOSFET} = \frac{\hat{I}_a^3 \cdot L_p}{3 U_d \cdot T} + \frac{1}{2} U_d \cdot \hat{I}_a \cdot t_f + \frac{1}{2} \frac{n_p}{n_s} U_o \hat{I}_a \cdot t_f$$

$$P_{MOSFET} = \frac{A}{U_d} + B \cdot U_d + C$$

El mínimo se da en $U_d = U_{d,mín}$ o

$$U_d = U_{d,mín}$$

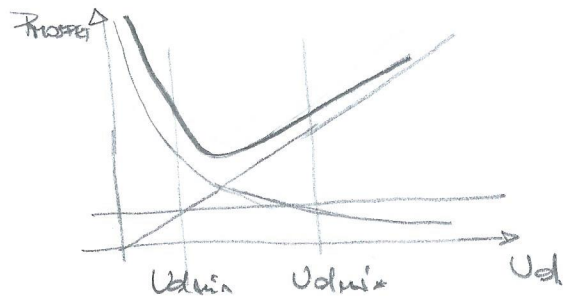

De las hojas de datos:

$$R_{DS(on)} = 1,2 \cdot 2,2 = 2,64 \Omega \quad t_f = 39 \text{ ns}$$

$$\text{en condiciones nominales: } \hat{I}_a = 3,21 \text{ A}$$

→ Para $U_d = U_{d,mín} = 390,32 \text{ V}$:

$$P_{MOSFET} = \frac{3,21^3 \cdot 23076 \times 10^{-6} \cdot 100 \times 10^3}{3 \cdot 390,32} + \frac{1}{2} \left(390,32 + \frac{24}{0,129} \right) 3,21 \cdot 39 \times 10^{-9} \cdot 100 \times 10^3$$

$$P_{MOSFET} = 0,652 + 3,608 = 4,26 \text{ W}$$

Solve Problems 2 (cont.)

→ $P_{\text{as Ud}} = U_d u_{\text{in}}$

$$P_{\text{roster}} = \frac{3,21^3 \cdot 230,76 \times 10^{-6} \cdot 100 \times 10^3}{124,45} + \frac{1}{2} \left(124,45 + \frac{24}{0,129} \right) \cdot 3,21 \cdot 39 \times 10^{-9} \cdot 100 \times 10^3$$

$P_{\text{roster}} = 6,13 + 1,94 = 8,07 \text{ W}$ ← por caso

$T_j - T_d = P_{\text{roster}} (R_{\text{ojc}} + R_{\text{ecs}} + R_{\text{osa}})$

Hoys de datos:


$R_{\text{ojc}} = 0,65 \text{ } ^\circ\text{C/W}$

$R_{\text{ecs}} = 0,24 \text{ } ^\circ\text{C/W}$

$R_{\text{osa}} = \frac{T_j - T_d}{P_{\text{roster}}} - R_{\text{ojc}} - R_{\text{ecs}}$

$R_{\text{osa}} = \frac{120 - 40}{8,07} - 0,65 - 0,24 \Rightarrow R_{\text{osa}} = 9,02 \text{ } ^\circ\text{C/W}$

5) Snubber

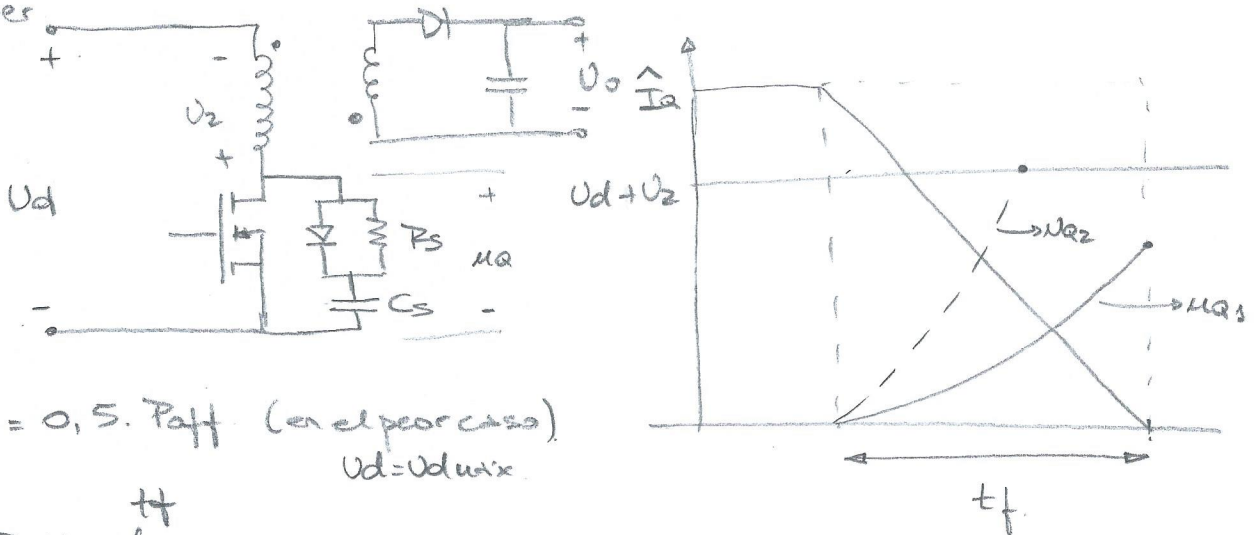

$P_{\text{off}S} = 0,5 \cdot P_{\text{off}}$ (en el peor caso)
 $U_d = U_d u_{\text{in}}$

Ahora $P_{\text{off}} = \int_0^{t_f} u_a \cdot i_a$

$i_a = \hat{I}_a - \frac{\hat{I}_a \cdot t}{t_f}$

$u_a(t) = \int_0^t \frac{i_c(\theta) d\theta}{C}$

$i_c(\theta) = \frac{\hat{I}_a \theta}{t_f}$

$\Rightarrow u_a(t) = \int_0^t \frac{\hat{I}_a \theta}{t_f C} d\theta = \frac{\hat{I}_a}{t_f \cdot C} \frac{t^2}{2}$

$P_{\text{off}} = \frac{1}{T} \int_0^{t_f} \frac{\hat{I}_a t^2}{2 t_f C} \left(\hat{I}_a - \frac{\hat{I}_a t}{t_f} \right) dt = \left(\frac{\hat{I}_a^2}{2 t_f C} \frac{t^3}{3} - \frac{\hat{I}_a^2}{2 t_f C} \frac{t^4}{4} \right) \cdot f$

$P_{\text{off}} = \frac{\hat{I}_a^2 t_f^2 f}{24 C} \left(\frac{1}{6} - \frac{1}{8} \right) = \frac{\hat{I}_a^2 \cdot t_f^2 \cdot f}{24 C}$

Solución Problema 2 (cont.)

$$P_{\text{off}} = \frac{I_a^2 \cdot t_f^2}{24C} = 0,13608$$

$$C = \frac{3,21^2 \cdot (39 \times 10^{-9})^2 \cdot 100 \times 10^3}{24 \cdot 0,13608} = 181 \text{ pF}$$

$$\text{Verifico: } u_Q(t_f) = \frac{I_a \cdot t_f^2}{2C t_f} = \frac{3,21 \cdot 39 \times 10^{-9}}{2 \cdot 181 \times 10^{-12}} = 345,8 \text{ V} < 577 \text{ V} \checkmark$$

$$3RC \leq 8T \Rightarrow R \leq \frac{8T}{3C}$$

$$S = \frac{I_a}{U_d} = \frac{230,76 \times 10^{-6}}{390,32} = 0,19$$

$$R \leq \frac{0,19}{3 \cdot 181 \times 10^{-12} \cdot 100 \times 10^3} = 3,5 \text{ k}\Omega \Rightarrow \boxed{R \leq 3,5 \text{ k}\Omega}$$

$$\underline{\underline{P_R}} = \frac{E_C}{T} = \frac{1}{2} C \cdot V^2 \cdot f = \frac{1}{2} \cdot 181 \times 10^{-12} \cdot 577^2 \cdot 100 \times 10^3 = \underline{\underline{3 \text{ W}}}$$