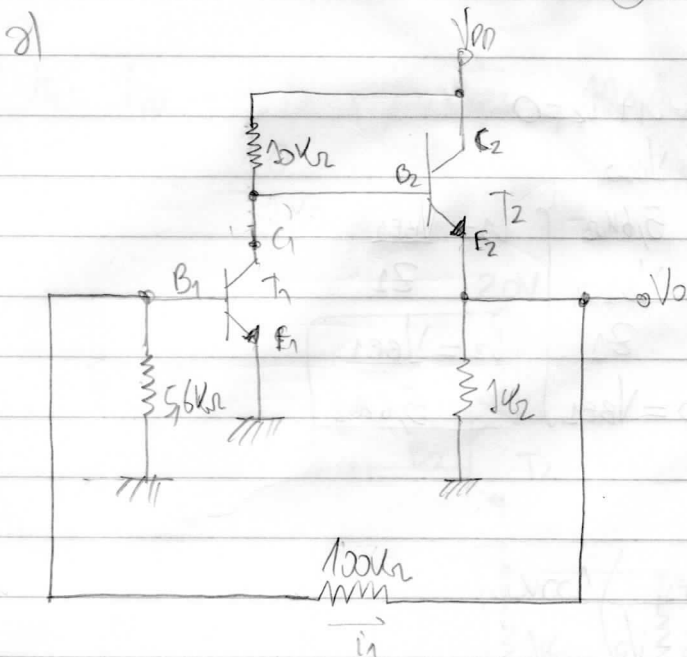


Exercice 3 Pratique 1:

(H) T_1 et T_2 sont en Z.A.



appliquer le théorème de Miller

$$K = \frac{V_o}{V_{e1}} \quad i_n = \frac{V_{e1} - V_o}{Z} \Rightarrow i_n = \frac{V_{e1} - K V_{e1}}{Z} = \frac{(1-K)V_{e1}}{Z}$$


$$Z = 100k\Omega \quad i_n = \frac{V_{e1}}{Z} = \frac{V_{e1}}{Z_1} ; \text{car } Z_1 = \frac{Z}{1-K}$$

$$\text{soit } Z_2 = \frac{K}{K-1} Z$$

$$Z_1 = \frac{100k\Omega}{1 - \frac{V_o}{V_{e1}}} ; Z_2 = \frac{V_o/V_{e1}}{\frac{V_o}{V_{e1}} - 1} 100k\Omega$$

$$Z_1 = \frac{100k\Omega}{\frac{V_{e1} - V_o}{V_{e1}}} ; Z_2 = \frac{V_o/V_{e1}}{\frac{V_o - V_{e1}}{V_{e1}}} 100k\Omega \Rightarrow Z_1 = \left(\frac{V_{e1}}{V_{e1} - V_o} \right) 100k\Omega$$
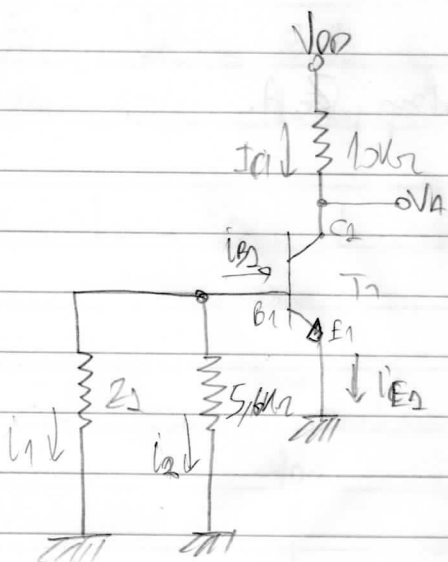
$$Z_2 = \frac{V_o}{V_o - V_{e1}} 100k\Omega$$



$$\begin{aligned}
 I_{B1} + I_1 + I_2 &= 0 \\
 I_{B1} &= \frac{V_{B10}}{100k\Omega} \\
 I_1 &= \frac{V_{B10}}{Z_1} \\
 V_{B10} &= V_{BE1} \\
 I_2 &= \frac{V_{BE1}}{5.6k\Omega}
 \end{aligned}$$

$$\begin{aligned}
 V_{B10} &= V_{BE1} \\
 Z_1 &= \left(\frac{V_{B10}}{V_{B10} - V_0} \right) 100k\Omega \Rightarrow Z_1 = \left(\frac{V_{BE1}}{V_{BE1} - V_0} \right) 100k\Omega
 \end{aligned}$$

$$I_1 = \frac{V_{B10} - V_0}{100k\Omega} \frac{V_{BE1}}{V_{BE1}} \Rightarrow I_1 = \frac{V_{BE1} - V_0}{100k\Omega}$$


$$V_{B10} = -I_1 - I_2 \Rightarrow I_{B1} = -\frac{(V_{BE1} - V_0)}{100k\Omega} - \frac{V_{BE1}}{5.6k\Omega}$$

$$\begin{aligned}
 I_{B1} &= \frac{V_0 - V_{BE1}}{100k\Omega} - \frac{V_{BE1}}{5.6k\Omega} \\
 I_{C1} &= \beta_1 I_{B1} \\
 I_{C1} &= \beta_1 \left(\frac{V_0 - V_{BE1}}{100k\Omega} - \frac{V_{BE1}}{5.6k\Omega} \right)
 \end{aligned}$$

$$I_{C1} = \frac{V_{DD} - V_A}{10k\Omega} \Rightarrow \frac{V_{DD} - V_A}{10k\Omega} = \beta_1 \frac{(V_0 - V_{BE1})}{100k\Omega} - \beta_1 \frac{V_{BE1}}{5.6k\Omega}$$

$$\frac{V_{DD}}{10k\Omega} - \frac{\beta_2 V_o}{10k\Omega} + \frac{\beta_2 V_{BE1}}{100k\Omega} + \frac{\beta_2 V_{BE2}}{5.6k\Omega} = \frac{V_A}{10k\Omega}$$
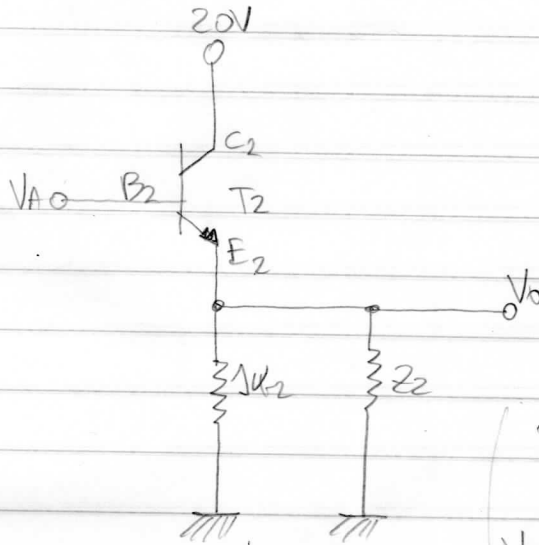
$$V_A = V_{DD} - \frac{\beta_2 V_o}{10} + \frac{\beta_2 V_{BE1}}{10} + \frac{10 \beta_2 V_{BE2}}{5.6k\Omega}$$



$$Z_2 = \frac{V_o}{V_o - V_{BE2}} 100k\Omega$$

$$V_{BE2} = V_{BE1}$$

$$\Rightarrow V_A - V_o = V_{BE2} \Rightarrow V_A = V_{BE2} + V_o$$

$$\Rightarrow Z_2 = \left(\frac{V_o}{V_o - V_{BE2}} \right) 100k\Omega$$

$$V_{BE2} + V_o = V_{DD} - \frac{\beta_2 V_o}{10} + \frac{\beta_2 V_{BE1}}{10} + \frac{10 \beta_2 V_{BE2}}{5.6}$$

$$V_o + \frac{\beta_2 V_o}{10} = V_{DD} - V_{BE2} + \frac{\beta_2 V_{BE1}}{10} + \frac{10 \beta_2 V_{BE2}}{5.6}$$

$$\Rightarrow \left(\frac{10 + \beta_2}{10} \right) V_o = V_{DD} - V_{BE2} + \frac{\beta_2 V_{BE1}}{10} + \frac{10 \beta_2 V_{BE2}}{5.6}$$

$$V_o = \frac{10 V_{DD}}{10 + \beta_2} - \frac{10 V_{BE2}}{10 + \beta_2} + \frac{10 \beta_2 V_{BE1}}{10 + \beta_2} + \frac{100 \beta_2 V_{BE2}}{10 + \beta_2} \cdot \frac{1}{5.6}$$

$$V_o = \frac{\beta_2}{10 + \beta_2} (V_{BE2} + 100 V_{BE2}) + \frac{10}{10 + \beta_2} (V_{DD} - V_{BE2})$$