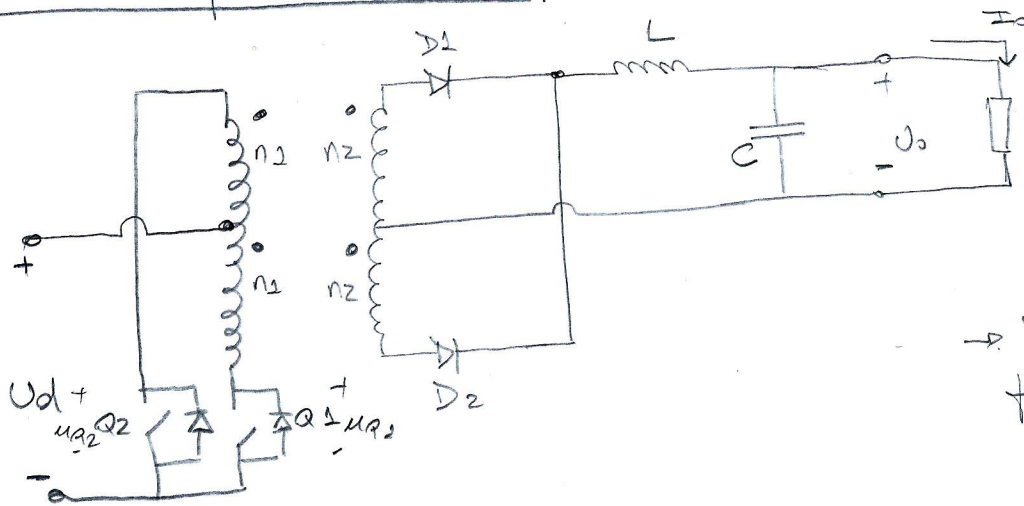


Solucion problema 1



$I_{out} = 20A$

$U_0 = 65V$

$U_{dmin} = 42V$

$L = 150\mu H$

$\Delta U_0 \leq 1\% U_0$

$\rightarrow MCC \neq I_0 \geq 2A$


$f = 20kHz$

$\delta_{max} = 0,45$

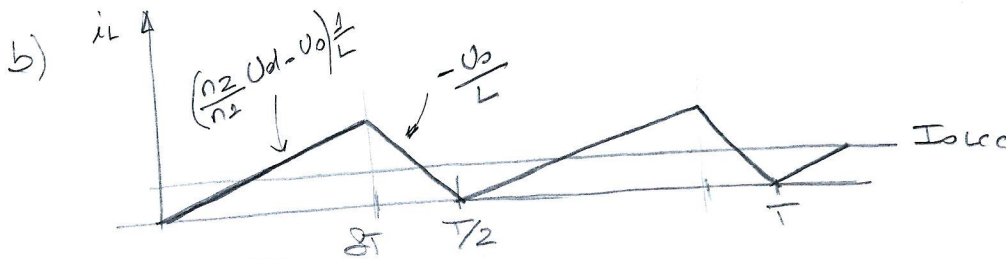a) $\frac{n_1}{n_2}$ en MCC: $\frac{U_0}{U_d} = \frac{2n_2}{n_1} \cdot \delta$

\rightarrow para utilizar δ máximo: $\delta_{max} \rightarrow U_d = U_{dmin}$

$\Rightarrow \frac{n_1}{n_2} = \frac{2 \delta_{max} \cdot U_{dmin}}{U_0} = \frac{2 \cdot 0,45 \cdot 42}{65} \Rightarrow \boxed{\frac{n_1}{n_2} = 0,582}$




$I_{oMCC} = \frac{2}{T} \int_0^{T/2} i_L(t) dt = \frac{2}{T} \cdot \frac{1}{2} \cdot \left(\frac{n_2 U_d - U_0}{L} \right) \frac{\delta T}{L} \cdot \frac{T}{2}$

$I_{oMCC} = \left(\frac{n_2 U_d - U_0}{n_1} \right) \frac{\delta T}{2L}$

A su vez, $U_0 = \frac{U_0}{U_d} = \frac{2n_2}{n_1} \cdot \delta \Rightarrow \delta = \frac{n_1 U_0}{2n_2 U_d}$

$\Rightarrow I_{oMCC} = \left(\frac{n_2 U_d - U_0}{n_1} \right) \cdot \frac{n_1 U_0}{2n_2 U_d} \cdot \frac{1}{2L} = \left(U_0 - \frac{n_1 U_0^2}{n_2 U_d} \right) \frac{1}{4Lf}$

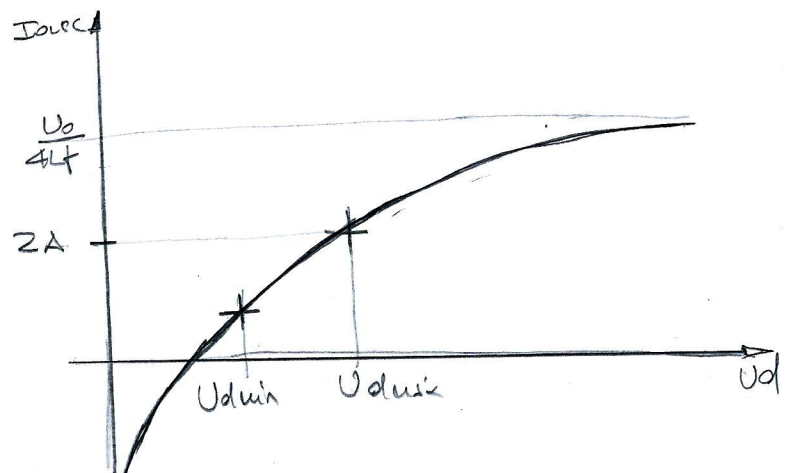$I_{oMCC} = \left(U_0 - \frac{n_1 U_0^2}{n_2 U_d} \right) \cdot \frac{1}{4Lf}$



Solución problema 1 (cont.)

$$I_{OLCC} = \left(U_0 - \frac{n_1}{n_2} \frac{U_0^2}{U_{dmax}} \right) \cdot \frac{1}{4Lf} = 2A$$

$$U_0 - \frac{n_1}{n_2} \frac{U_0^2}{U_{dmax}} = 8Lf \rightarrow \frac{n_2}{n_1} \frac{U_{dmax}}{U_0^2} = \frac{1}{U_0 - 8Lf}$$


$$U_{dmax} = \frac{n_1}{n_2} \frac{U_0^2}{U_0 - 8Lf} = \frac{0,582 \cdot 65^2}{65 - 8 \cdot 150 \times 10^{-6} \cdot 20 \times 10^3}$$

$$U_{dmax} \approx 60V$$

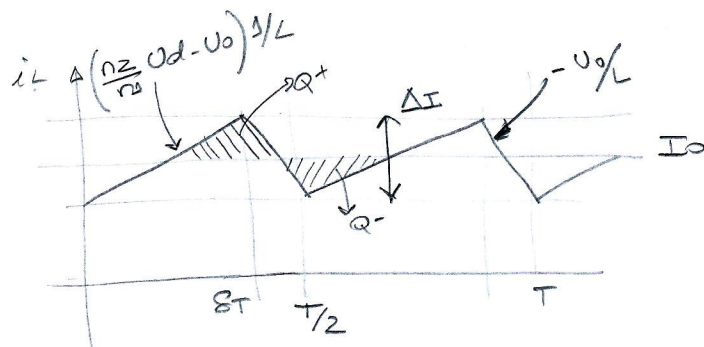c) $\Delta U_0 \leq 0,01 \cdot U_0 = 0,65V$

$$\Delta U_0 = \frac{Q^+}{C} = \frac{Q^-}{C}$$

$$Q^+ = \frac{1}{2} \cdot \frac{T}{4} \cdot \frac{\Delta I}{2} = \frac{\Delta I}{16 \cdot f}$$



$$\Delta I = \frac{U_0}{L} (T - 8T)$$

$$\Delta I_{min} \rightarrow d = d_{min} : d_{min} = \frac{1}{2} \frac{n_1}{n_2} \frac{U_0}{U_{dmax}} = \frac{0,582 \cdot 65}{2 \cdot 60} = 0,315$$

$$\Delta I = \frac{65 (0,5 - 0,315)}{16 \cdot 150 \times 10^{-6} \cdot 20 \times 10^3} \Rightarrow \Delta I_{min} = 4A$$

$$C = \frac{\Delta I}{16 \cdot f \cdot \Delta U_0} = \frac{4}{16 \cdot 20 \times 10^3 \cdot 0,65} \Rightarrow C = 194F$$

de la tabla: $C = 224F$ $ESR = 1,222\Omega \Rightarrow \Delta U_0 \approx ESR \cdot \Delta I \approx 5V \times$

$$\Rightarrow ESR \leq \frac{\Delta U_0}{\Delta I} = \frac{0,65}{4} = 0,163\Omega \Rightarrow \text{podría poner uno de } C = 2204F$$

$$ESR = 0,099\Omega$$

$I_0 = 20 \text{ A}$

$U_d = 48 \text{ V} \Rightarrow \delta = \frac{0,582 \cdot 65}{2 \cdot 48} = 0,394$

$\Delta I = \frac{65 (0,5 - 0,394)}{150 \times 10^{-6} \cdot 20 \times 10^3} = 2,3 \text{ A}$

$i_{L_{\text{máx}}} = I_0 + \frac{\Delta I}{2} = 21,15 \text{ A}$

$i_{L_{\text{mín}}} = I_0 - \frac{\Delta I}{2} = 18,85 \text{ A}$

$i_{Q_{\text{máx}}} = \frac{n_2}{n_1} i_{L_{\text{máx}}} = 36,3 \text{ A}$

$i_{Q_{\text{mín}}} = \frac{n_2}{n_1} i_{L_{\text{mín}}} = 32,4 \text{ A}$

