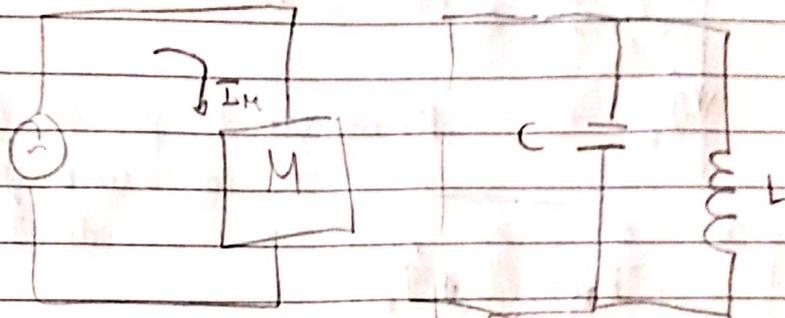


Ej 2



$V_{rms} = 170 \text{ V} \rightarrow V_0 = 169,7 \text{ V}$

$f = 50 \text{ Hz} \rightarrow \omega = 314,16 \text{ rad/s}$


$P_M = 0,5 \text{ kW}$

$\text{fac pot} = 0,6 \rightarrow \phi = 53,13^\circ$

Corriente adelantada el voltaje fuente

a)  $P = V_{rms} I_{rms} \cos \phi = I_{rms} = 4,91 \text{ A}$

b)

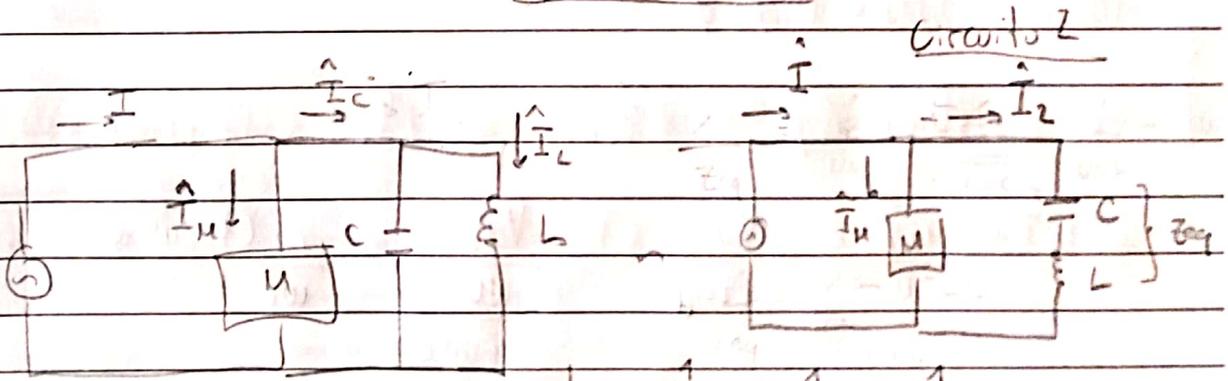

$\text{fac pot} = 1 \rightarrow \phi' = 0$

$\frac{1}{Z_{eq}} = \frac{1}{Z_L} + \frac{1}{Z_C}$

$\frac{1}{Z_{eq}} = \frac{1}{\omega L} + \frac{1}{\omega C}$

$\hat{I}_M$  es la corriente de la parte anterior


$\frac{1}{Z_{eq}} = \frac{1}{\omega L} + i\omega C = \frac{1 - \omega^2 LC}{\omega L}$

$|\hat{I}_M| = \sqrt{2} I_{rms} = 6,94 \text{ A}$

$\phi = 53,13^\circ$

$Z_{eq} = \frac{\omega L}{1 - \omega^2 LC}$

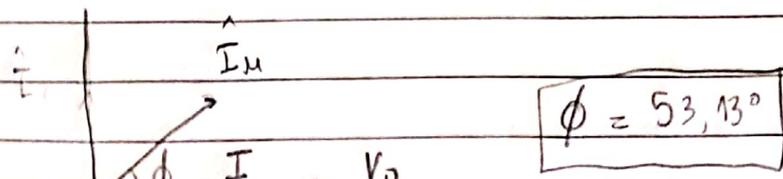porque sabemos que adelantado respecto al voltage (por letra)



En este sentido para que quede la componente imaginaria de  $\hat{I}_u$

Kirchoff 
$$\hat{I} = \hat{I}_u + \hat{I}_z$$

Circuito Z:  $V_0 - Z_{eq} \hat{I}_z = 0$

$$\hat{I}_z = \frac{V_0}{Z_{eq}} = \frac{V_0}{\frac{wL}{1-w^2LC}} = \frac{V_0 \cdot (1-w^2LC)}{wL}$$

$$|\hat{I}| = |\hat{I}_u| \cos \phi$$

$$0 = |\hat{I}_u| \sin \phi - |\hat{I}_z|$$

$$|\hat{I}_u| \sin \phi = \frac{V_0}{|Z_{eq}|} = \frac{V_0}{\frac{wL}{1-w^2LC}} = \frac{V_0 (1-w^2LC)}{wL}$$

$$5,55 = \frac{V_0 (1-w^2LC)}{wL} \Rightarrow 0,308 = 1-w^2LC$$

$$\Rightarrow w^2LC = 0,692 \Rightarrow C = 7,33 \times 10^{-4} F$$