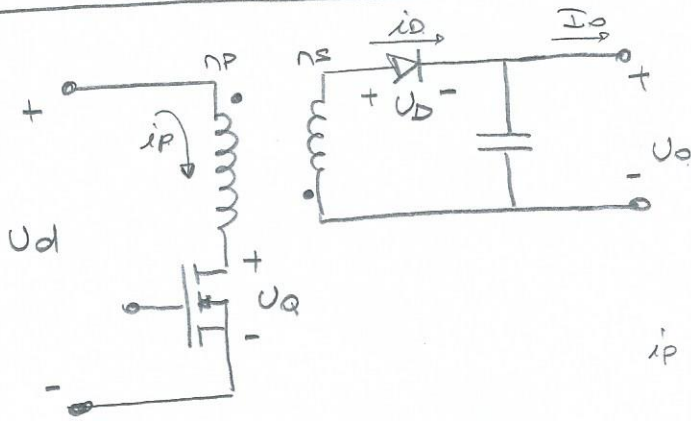


Solucion Problema 2




$U_o = 12V$ $I_{o\max} = 8A$
 $U_{d\min} = 80V$ $U_{d\max} = 140V$
 $f = 50kHz$ $\delta_{\max} = 0,42$
 $U_D = 1V$

e) \hat{I}_P, \hat{I}_S

$I_o = \langle i_D \rangle = \frac{1}{T} \int_0^{\delta T} \frac{1}{2} (1 - \delta) t \cdot \hat{I}_S dt$

$\Rightarrow \hat{I}_S = \frac{2 I_o}{1 - \delta} = \frac{2 \cdot 8}{1 - 0,42}$

$\hat{I}_S = 27,59 A$

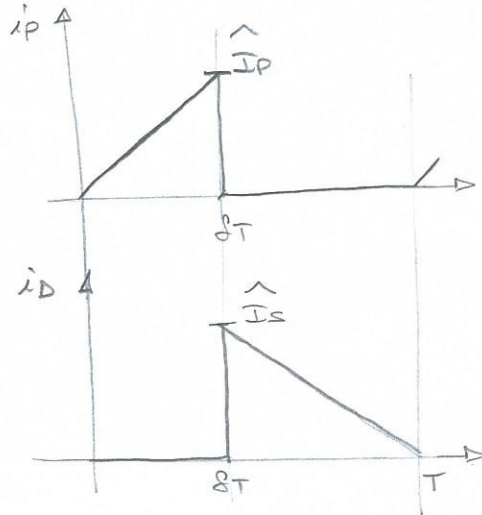

Condición
 LCC para
 carga máxima
 y $U_d = U_{d\min}$
 \Downarrow
 siempre trabajo
 en HCD

$P_{in} = P_o + P_D = 12 \cdot 8 + 1 \cdot 8 = 104W$

$P_{in} = \frac{1}{2} L_P \hat{I}_P^2 f \Rightarrow P_{in} = \frac{1}{2} L_P \cdot \frac{U_d^2 \delta^2}{L_P^2} \cdot f$

$\hat{I}_P = \frac{U_d \cdot \delta T}{L_P}$

$\Rightarrow L_P = \frac{U_d^2 \cdot \delta^2}{2 \cdot P_{in} \cdot f} = \frac{(80 \cdot 0,42)^2}{2 \cdot 104 \cdot 50 \times 10^3} = 108,55 \mu H$

$\hat{I}_P = \frac{80 \cdot 0,42}{108,55 \times 10^{-6} \cdot 50 \times 10^3} \Rightarrow \hat{I}_P = 6,19 A$

b) $n_S \hat{I}_S = n_P \hat{I}_P \Rightarrow \frac{n_S}{n_P} = \frac{\hat{I}_P}{\hat{I}_S} = \frac{6,19}{27,59}$

$\frac{n_S}{n_P} = 0,224$ $\frac{n_P}{n_S} = 4,457$

c) $U_{Q\max}, U_{D\max}$

Have OFF $\Rightarrow U_Q = -U_P + U_d$

$U_S = U_D + U_o \Rightarrow U_P = (-U_D - U_o) \cdot \frac{n_P}{n_S}$

$\Rightarrow U_{Q\max} = U_{d\max} + (U_D + U_o) \cdot \frac{n_P}{n_S}$

$U_{Q\max} = 140 + 13 \cdot 4,457$

$U_{Q\max} = 197,9 V$

Have ON $\Rightarrow U_D = U_S - U_o$

$U_S = -\frac{n_S}{n_P} \cdot U_d$

$\Rightarrow U_{D\max} = -\frac{n_S}{n_P} \cdot U_{d\max} - U_o = -0,224 \cdot 140 - 12$

$U_{D\max} = -43,36 V$

Solución Problema 2 (cont.)

d) cortocircuito a la salida \Rightarrow ahora $U_o = U_D = 1V$.

\hat{I}_P limitada $\approx 6,19A$.

\rightarrow Asumo MCC. $\frac{U_o}{U_d} = \frac{n_s}{n_p} \cdot \frac{d}{1-d} \Rightarrow d = \frac{\frac{n_p}{n_s} \cdot U_o/U_d}{1 + \frac{n_p}{n_s} \cdot U_o/U_d}$
 $\Rightarrow d = \frac{4,457 \cdot 1/80}{1 + 4,457 \cdot 1/80} \Rightarrow d = 0,053$

Wave OFF:

$U_q = U_{dmin} + \frac{n_p}{n_s} \cdot U_D$

$U_q = 80 + 4,457 \cdot 1 = 84,5V$

$\hat{I}_P = I_{min_p} + \frac{U_d \cdot \delta T}{L_p}$

$\Rightarrow I_{min_p} = \hat{I}_P - \frac{U_d \cdot \delta T}{L_p}$

$I_{min_p} = 6,19 - \frac{80 \cdot 0,053}{108,55 \times 10^{-6} \cdot 50 \times 10^3}$

$I_{min_p} = 5,41A$ \leftarrow MCC (OK)

e) $\hat{I}_s = 27,59A$

$I_{min_s} = \hat{I}_s - \frac{U_D (1-d) T}{L_s}$


$L_s = \left(\frac{n_s}{n_p}\right)^2 \cdot L_p = 0,224^2 \cdot 108,55 \times 10^{-6}$

$L_s = 5,45 \mu H$

$I_{min_s} = 27,59 - \frac{1 \cdot (1-0,053)}{5,45 \times 10^{-6} \cdot 50 \times 10^3} \Rightarrow I_{min_s} = 24,11A$ *

$\langle i_D \rangle = \frac{d}{T} \cdot \frac{d}{2} (\hat{I}_s + I_{min_s}) \cdot (1-d) T = \frac{27,59 + 24,11}{2} \cdot (1-0,053)$

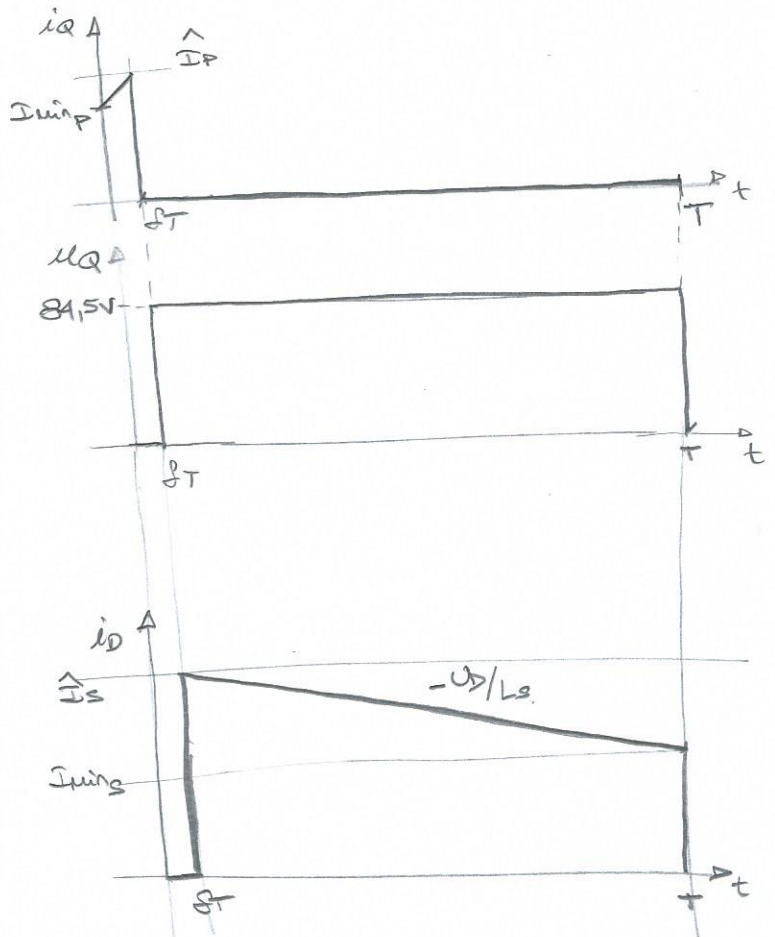$\Rightarrow \langle i_D \rangle = 24,48A$



* Otra: $I_{min_s} = \frac{n_p}{n_s} I_{min_p} = 4,457 \cdot 5,41$
 $I_{min_s} = 24,11A$ ✓