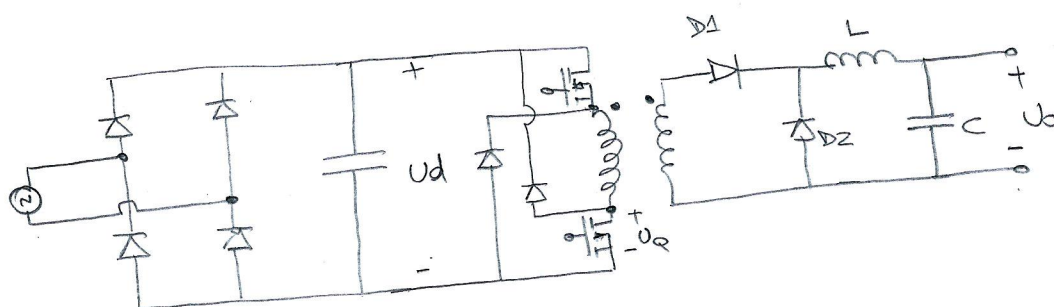


Solución Problema 2

a)



- $f = 50 \text{ kHz}$
- $L_m = 600 \mu\text{H}$
- $L = 80 \mu\text{H}$
- $U_o = 48 \text{ V}$
- $I_{o \text{ máx}} = 20 \text{ A}$
- $\frac{n_1}{n_2} = 1,25$
- $T_{o \text{ máx}} = 40^\circ\text{C}$

$U_{a \text{ máx}} = 2,8 \cdot 500 = 400 \text{ V}$

Como $U_{a \text{ máx}} = U_{d \text{ máx}} \Rightarrow \underline{U_{d \text{ máx}} = 400 \text{ V}}$

Si asumo HCC: $\frac{U_o}{U_d} = \frac{n_2}{n_1} \cdot \delta$


En este convertidor $\delta_{\text{máx}} = 0,5 \Rightarrow \frac{U_o}{U_{d \text{ mín}}} = \frac{n_2}{n_1} \cdot \delta_{\text{máx}}$

$\underline{U_{d \text{ mín}}} = \frac{U_o}{\delta_{\text{máx}}} \cdot \frac{n_1}{n_2} = \frac{48 \cdot 1,25}{0,5} = \underline{120 \text{ V}}$

En una red de 110V $\rightarrow U_d = \sqrt{2} \cdot 110 \approx 156 \text{ V}$

En una red de 230V $\rightarrow U_d = \sqrt{2} \cdot 230 \approx 325 \text{ V}$

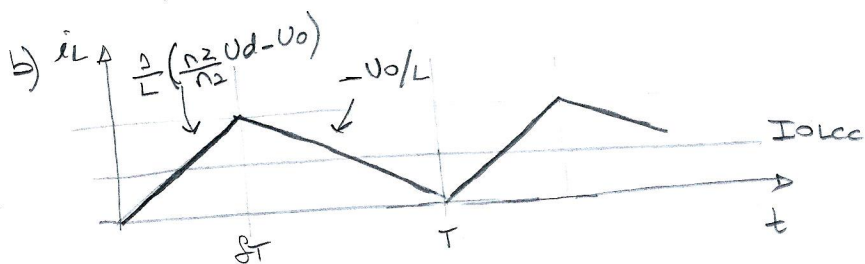Conectado a una red de 110V o de 230V, aún con tolerancia +/- 20%
(124,8V - 390V) \Rightarrow puede funcionar




$I_{o \text{ LCC}} = \frac{1}{T} \int_0^T i_{\text{LCC}}(t) dt$

$I_{o \text{ LCC}} = \frac{1}{T} \cdot \frac{1}{2} \cdot \frac{1}{L} \left(\frac{n_2}{n_1} U_d - U_o \right) \delta T$

En el LCC: $\frac{U_o}{U_d} = \frac{n_2}{n_1} \cdot \delta \Rightarrow \delta = \frac{n_1}{n_2} \cdot \frac{U_o}{U_d}$

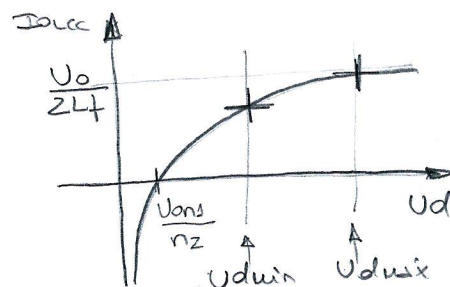$I_{o \text{ LCC}} = \frac{n_1}{n_2} \frac{U_o}{U_d} \cdot \frac{1}{2L} \left(\frac{n_2}{n_1} U_d - U_o \right) = \frac{1}{2Lf} \left(U_o - \frac{U_o^2 n_1}{U_d n_2} \right)$




Si se impone LCC para $U_d = U_{d \text{ máx}} \Rightarrow$ si la carga consume

$I_o > I_{o \text{ LCC}} \Rightarrow$ el convertidor estará en HCC $\forall U_d / U_{d \text{ mín}} \leq U_d \leq U_{d \text{ máx}}$

$\delta = \frac{n_1}{n_2} \frac{U_o}{U_{d \text{ máx}}} = \frac{1,25 \cdot 48}{400} = 0,15$

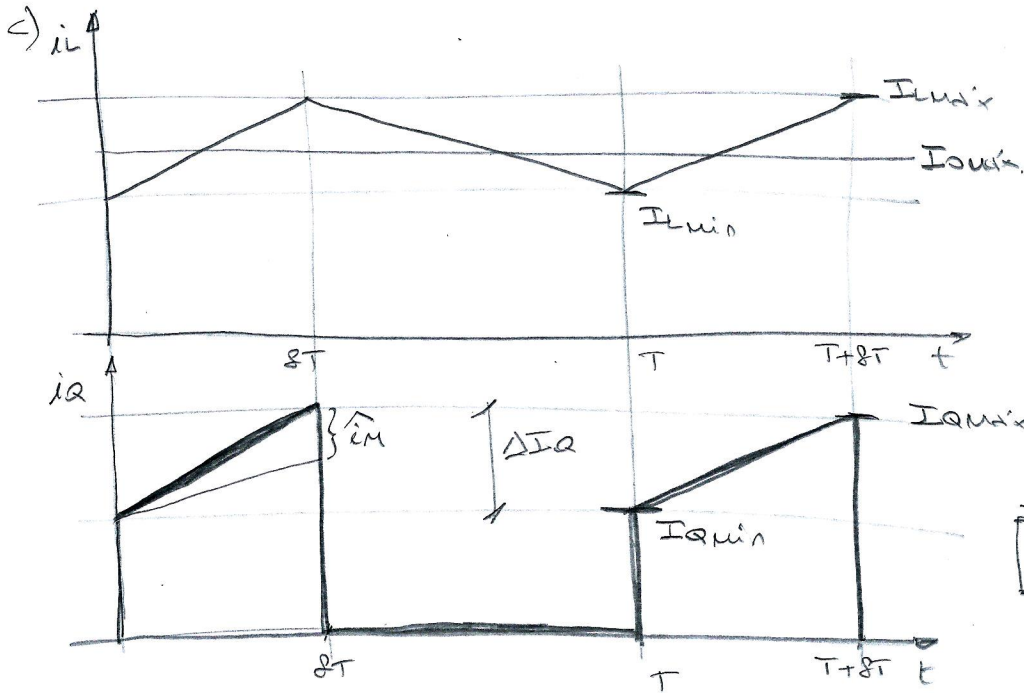$I_{o \text{ LCC}} = \left(48 - \frac{48^2}{400} \cdot 1,25 \right) \cdot \frac{1}{2 \cdot 80 \times 10^{-6} \cdot 50 \times 10^3} \Rightarrow \underline{I_{o \text{ LCC}} = 5,1 \text{ A}}$



$$I_{Lmin} = I_{Lmax} - \frac{\Delta I_{Lmax}}{2}$$

$$I_{Lmax} = I_{Lmin} + \frac{\Delta I_{Lmax}}{2}$$

$$I_{Lmin} = 20 - \frac{5,1}{2} = 17,45A$$

$$I_{Lmax} = 20 + \frac{5,1}{2} = 22,55A$$

$$I_{Dmin} = \frac{n_2}{n_1} I_{Lmin}$$

$$I_{Dmin} = \frac{17,45}{1,25} = 13,96A$$

$$I_{Dmax} = I_{Lmax} \cdot \frac{n_2}{n_1} + \frac{U_d \cdot 8T}{L_w} = \frac{22,55}{1,25} + \frac{40 \cdot 0,15}{600 \times 10^{-6} \cdot 50 \times 10^3} \Rightarrow I_{Dmax} = 20,04A$$

e) $T_j - T_a = P(R_{\theta jc} + R_{\theta cs} + R_{\theta ss})$ Si $T_{amb} = T_j = 150^\circ C$ (por caso)

$$\Rightarrow R_{\theta ss}(\Omega) = 2,5 \cdot 0,27 = 0,675 \Omega$$

$$P = P_{rec} + P_{sp} + P_{cond}$$

$$P_{rec} = \frac{U_{dmax} \cdot I_{Dmin} \cdot t_r \cdot f}{2} = \frac{400 \cdot 13,96 \cdot 59 \times 10^{-9} \cdot 50 \times 10^3}{2} = 8,24W$$

$$P_{sp} = \frac{U_{dmax} \cdot I_{Dmax} \cdot t_f \cdot f}{2} = \frac{400 \cdot 20,04 \cdot 58 \times 10^{-9} \cdot 50 \times 10^3}{2} = 11,62W$$

$$P_{cond} = R_{\theta ss}(\Omega) I_{Qeff}^2 \rightarrow i_D(t) = I_{Dmin} + \frac{\Delta I_D \cdot t}{8T} \rightarrow I_{Qeff}^2 = \frac{1}{T} \int_0^T i_D^2(t) dt$$

$$i_D^2(t) = I_{Dmin}^2 + \frac{\Delta I_D^2 t^2}{8T^2} + \frac{2 I_{Dmin} \Delta I_D t}{8T} \Rightarrow I_{Qeff}^2 = \frac{1}{T} \left(I_{Dmin}^2 \frac{T}{8T} + \frac{\Delta I_D^2 \frac{8T^3}{3}}{3 \cdot 8T^2} + \frac{2 I_{Dmin} \Delta I_D \frac{8T^2}{2}}{2 \cdot 8T} \right)$$

$$I_{Qeff}^2 = 8 \left(I_{Dmin}^2 + \frac{\Delta I_D^2}{3} + I_{Dmin} \Delta I_D \right)$$

$$P_{cond} = 0,675 \cdot 0,15 \left(13,96^2 + \frac{6,08^2}{3} + 13,96 \cdot 6,08 \right) = 29,57W$$

$$\Rightarrow P = 8,24 + 11,62 + 29,57 = 49,43$$

$$R_{\theta ss} = \frac{T_j - T_a}{P} - R_{\theta jc} - R_{\theta cs} = \frac{150 - 40}{49,43} - 0,45 - 0,24 = 1,54$$

Como el disipador instalado tiene $R_{\theta ss} = 1,3^\circ C/W < 1,54^\circ C/W \Rightarrow$ es suficiente para que no lleguen a la $T_{mix} = 150^\circ C$