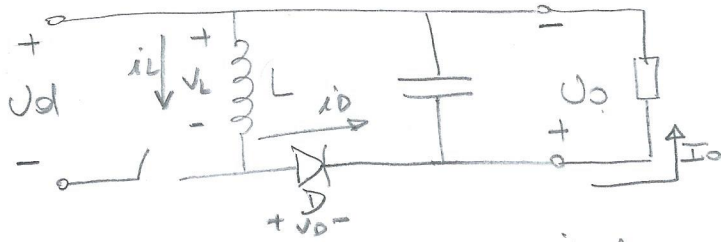


Solución Problema 2



$U_d = 24V \quad U_o = 42V \quad P_o = 60W$

$f = 100kHz \quad \Delta U_o = 0,01 \cdot 42V$

⇒ Funcionamiento en el LCC:

$I_o = \frac{P_o}{U_o} = \frac{60}{42} = 1,43A$


⇒ Vale que

$\frac{U_o}{U_d} = \frac{\delta}{1-\delta}$

$(1-\delta)U_o = \delta U_d$

$\Rightarrow \delta = \frac{U_o}{U_o + U_d} = \frac{42}{42 + 24}$

$\Rightarrow \delta = 0,636$

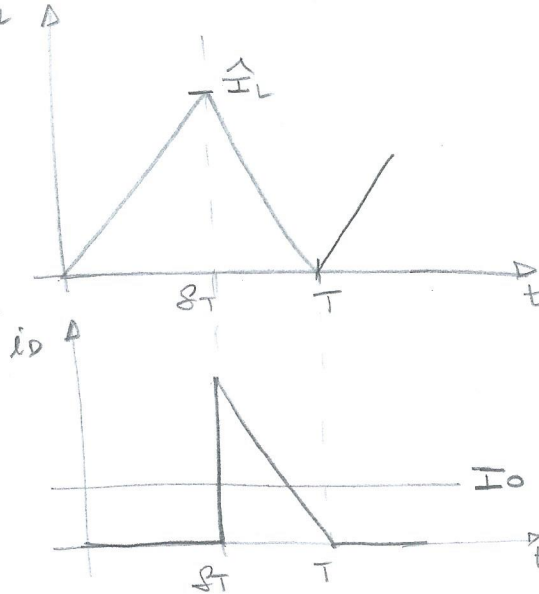


$P_{in} = P_{out}$

$P_{in} = \frac{1}{2} \cdot L \cdot \hat{I}_L^2 \cdot f \quad \Rightarrow \quad P_{in} = \frac{1}{2} f \frac{U_d^2 \delta^2 T^2}{L} = P_o$

$\hat{I}_L = \frac{U_d}{L} \delta T$

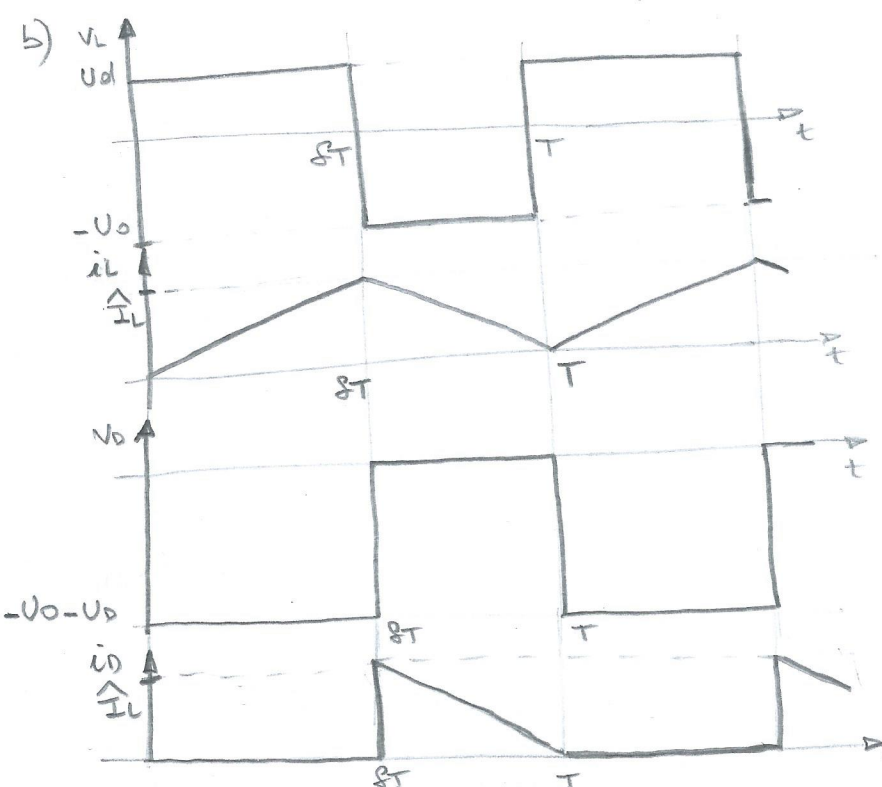$\Rightarrow L = \frac{U_d^2 \cdot \delta^2}{2 P_o f} = \frac{24^2 \cdot 0,636^2}{2 \cdot 60 \cdot 100 \times 10^3} \Rightarrow \boxed{L = 19,42 \mu H}$



$\hat{I}_L = \frac{U_d \delta}{L f} = \frac{24 \cdot 0,636}{19,42 \times 10^{-6} \cdot 100 \times 10^3}$

$\hat{I}_L = 7,86A$

Solución Problema 2 (cont)

e) $\Delta U_o = 0,01 \cdot 42 = 0,42V$


$\Delta U_o = \frac{Q}{C} \Rightarrow C = \frac{Q}{\Delta U_o}$

$Q = \frac{1}{2} \cdot \theta T (\hat{I}_L - I_o)$


$\frac{\theta T}{(1-\delta)T} = \frac{\hat{I}_L - I_o}{\hat{I}_L} \Rightarrow \theta T = \frac{\hat{I}_L - I_o}{\hat{I}_L} (1-\delta)T \Rightarrow Q = \frac{1}{2} \frac{(\hat{I}_L - I_o)^2 (1-\delta)T}{\hat{I}_L}$

$\Rightarrow C = \frac{1}{2} \frac{(\hat{I}_L - I_o)^2 (1-\delta)T}{\Delta U_o \cdot \hat{I}_L} = \frac{1}{2} \frac{(7,86 - 1,43)^2 (1 - 0,636)}{0,42 \cdot 7,86 \cdot 100 \times 10^3}$

$\Rightarrow \boxed{C = 22,79 \mu F}$

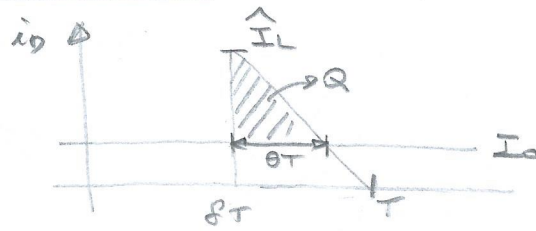

d) Convertidor Boost:

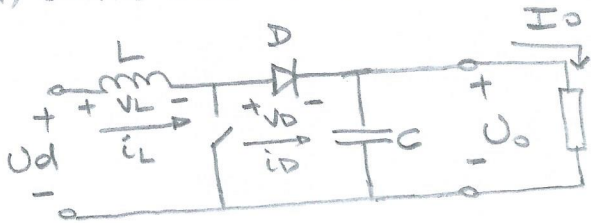

e) Assumo que el convertidor opera en MCC:


$\Rightarrow \frac{U_o}{U_d} = \frac{1}{1-\delta} \rightarrow 1-\delta = \frac{U_d}{U_o} \Rightarrow \delta = 1 - \frac{U_d}{U_o} = 1 - \frac{24}{42} = 0,43$



$\Delta I_L = \frac{U_d}{L} \cdot \delta T = \frac{24 \cdot 0,43}{19,42 \times 10^{-6} \cdot 100 \times 10^3} = 5,31A$

$\langle I_L \rangle \cdot U_d = P_{in} = P_o \Rightarrow \langle I_L \rangle = \frac{P_o}{U_d} = \frac{60}{24} = 2,5A$ pero $\frac{\Delta I_L}{2} = 2,66 > \langle I_L \rangle \Rightarrow$ el convertidor

está operando en MCD

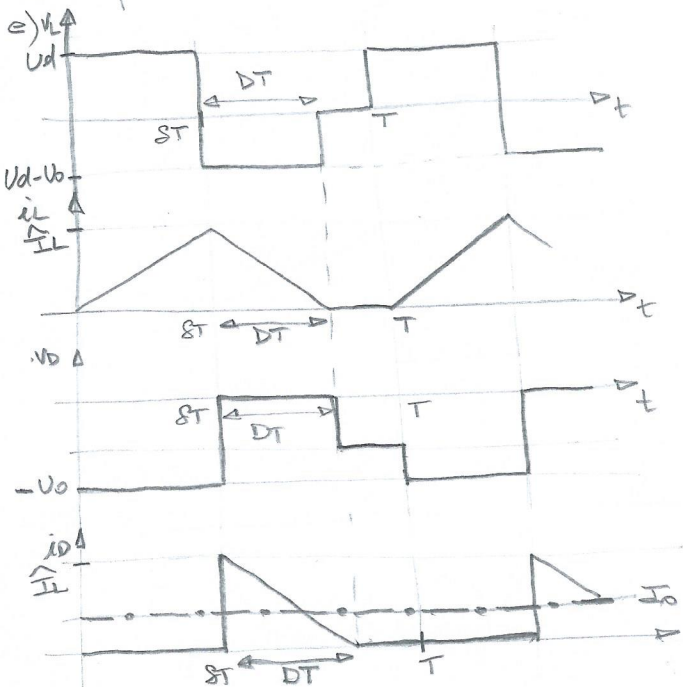

$I_o = \frac{1}{T} \int_0^{\delta T} \hat{I}_L dt$

$\hat{I}_L = \frac{U_d}{L} \cdot \delta T$

$U_d \cdot \delta T = (U_o - U_d) \delta T \Rightarrow \delta T = \frac{U_d \delta T}{U_o - U_d}$

$\Rightarrow I_o = \frac{1}{T} \int_0^{\delta T} \frac{U_d}{L} \cdot \delta T dt = \frac{U_d}{L} \cdot \delta T$

$I_o = \frac{U_d^2 \cdot \delta^2}{2(U_o - U_d) \cdot L \cdot f}$

$\delta = \sqrt{\frac{2 I_o (U_o - U_d) \cdot L \cdot f}{U_d^2}}$

$\delta = \sqrt{\frac{2 \cdot 1,43 (42 - 24) \cdot 19,42 \times 10^{-6} \cdot 100 \times 10^3}{24^2}}$

$\boxed{\delta = 0,417}$

Solución Problema 2 (cont. 1)

$$\hat{I}_L = \frac{U_d \cdot \delta T}{L} = \frac{24 \cdot 0,417}{19,42 \times 10^{-6} \cdot 100 \times 10^3} = 5,15 \text{ A}$$

$$DT = \frac{24 \cdot 0,417}{(42 - 24) \cdot 100 \times 10^3} = 5,56 \mu\text{s}$$

f) $C = 45,59 \mu\text{F}$

$$\Delta U_o = \frac{Q}{C}$$

$$Q = \frac{1}{2} \delta T \cdot (\hat{I}_L - I_o)$$

$$\Rightarrow Q = \frac{1}{2} \frac{(\hat{I}_L - I_o)^2 \delta T}{\hat{I}_L} \Rightarrow \Delta U_o = \frac{(\hat{I}_L - I_o)^2 \cdot \delta T}{2 \cdot \hat{I}_L \cdot C}$$

$$\Rightarrow \Delta U_o = \frac{(5,15 - 1,43)^2 \cdot 5,56 \times 10^{-6}}{2 \cdot 5,15 \cdot 45,59 \times 10^{-6}}$$

$$\Rightarrow \Delta U_o = 0,32 \text{ V}$$

↓
el ripple es 0,78% < 1% ✓

