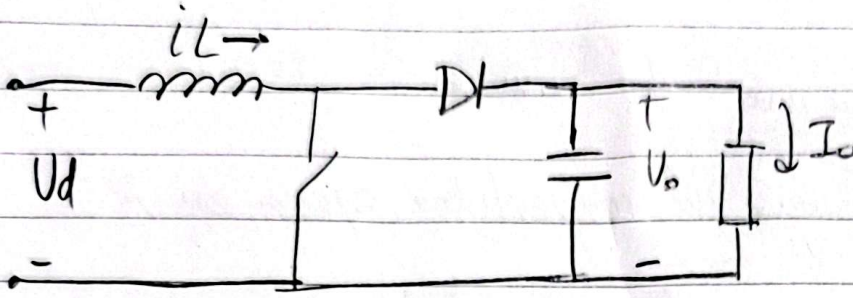


PROBLEMA 2



$$P_{\text{max}} = 3 \text{ kW}$$



$$V_o = 300 \text{ V}$$

$$V_{d\text{min}} = 100 \text{ V}$$

$$V_{d\text{max}} = 250 \text{ V}$$

$$f = 100 \text{ kHz}$$

A) En el límite de conducción Continua.

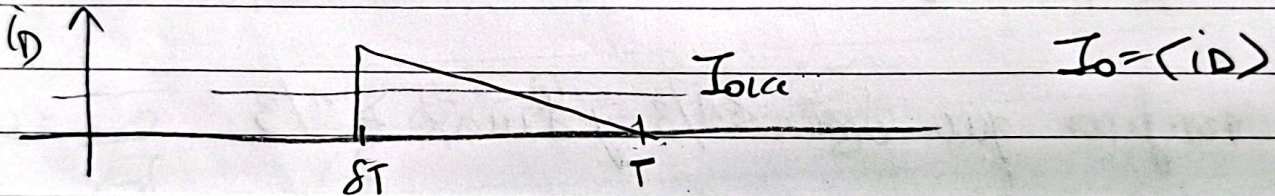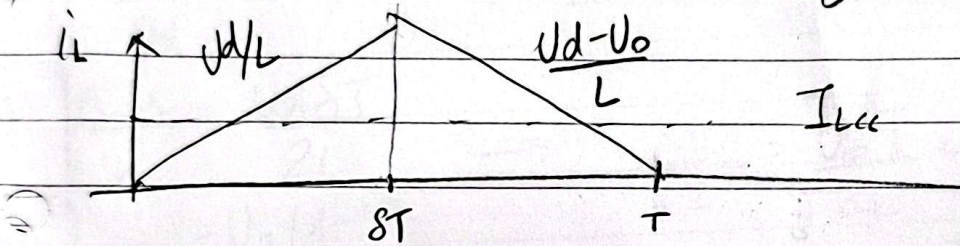

$$I_{L\text{cc}} = \frac{1}{T} \int_0^T i_{L\text{cc}}(t) dt = \frac{1}{T} \cdot \frac{T}{2} \cdot \frac{V_d \delta T}{L} = \frac{V_d \delta T}{2L}$$

Es válida la transferencia en MCC: $\frac{V_o}{V_d} = \frac{1}{1-\delta}$

$$V_d = V_o(1-\delta)$$


$$\Rightarrow I_{L\text{cc}} = \frac{V_o \delta (1-\delta)}{2Lf}$$

Además: $I_{o\text{cc}} = \frac{1}{T} \cdot \frac{1}{2} (1-\delta) T \cdot \frac{V_d \delta T}{L} = \frac{(1-\delta) \delta V_d}{2Lf}$

$$I_{o\text{cc}} = \frac{(1-\delta)^2 \delta V_o}{2Lf}$$

Impongo que $I_{O_{\max}} = \frac{1}{2} I_{O_{\max}}$

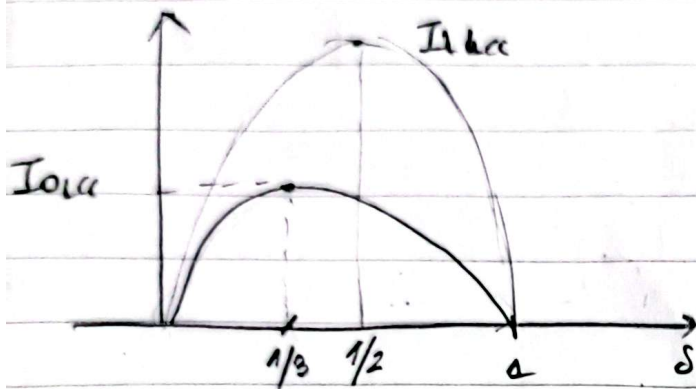∴ $I_O > \frac{1}{2} I_{O_{\max}}$ el convertidor opera en MOC.



Debo verificar que $\delta_{\min} < 1/3$ y $\delta_{\max} > 2/3$

$$\frac{V_O}{V_{d_{\max}}} = \frac{1}{1 - \delta_{\min}} \rightarrow \delta_{\min} = 1 - \frac{V_{d_{\max}}}{V_O}$$

$$\delta_{\min} = 1 - \frac{V_{d_{\max}}}{V_O} = 1 - \frac{250}{300} = 0.166$$

$$\delta_{\max} = 1 - \frac{V_{d_{\min}}}{V_O} = 1 - \frac{100}{300} = 0.666$$


$$I_{O_{\max}} = \frac{P_{O_{\max}}}{V_O} = \frac{3000W}{300V} = 10A \quad \frac{I_{O_{\max}}}{2} = \frac{V_O \delta^* (1 - \delta^*)^2}{2Lf}$$

$$L = \frac{V_O \delta^* (1 - \delta^*)^2 \cdot 2}{2f I_{O_{\max}}} = 44 \mu H$$

$$L = \frac{300 (1/3) (2/3)^2 \cdot 2}{2 \cdot (100 \times 10^3) (10)} = 44 \mu H$$

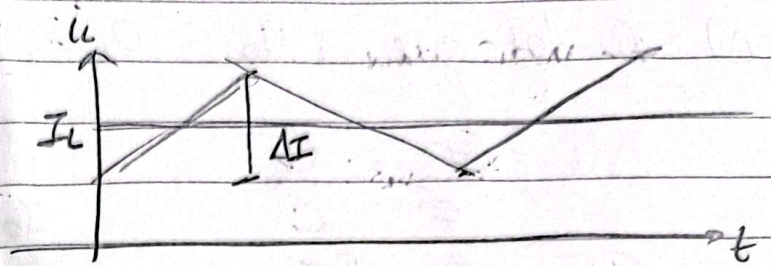b) Corriente por el MOSFET

$$\hat{I}_Q = I_L + \frac{\Delta I_L}{2}$$



$$P_{in} = P_{out} \rightarrow V_d I_L = V_o I_o$$

$$I_L = \frac{V_o}{V_d} I_o = \frac{I_o}{(1-\delta)}$$

$$\left\{ \begin{array}{l} \frac{\Delta I_L}{2} = \frac{V_d \delta T}{2L} \\ V_d = V_o (1-\delta) \end{array} \right. \rightarrow \frac{\Delta I_L}{2} = \frac{V_o T}{2L} \delta (1-\delta)$$

$$I_Q = \frac{I_o}{1-\delta} + \frac{V_o T}{2L} \delta (1-\delta) = I_L + \frac{\Delta I_L}{2}$$

- $I_L \uparrow$ con δ
- ΔI_L tiene un máximo en $\delta = 1/2$

Corresponde ver qué pasa para $\delta = 1/2$ y $\delta = 0,66$


$$\begin{aligned} \delta = 0,5 \quad I_Q &= \frac{10}{1-0,5} + \frac{300 \cdot (0,5)(1-0,5)}{2 \cdot (100 \times 10^3)(44 \times 10^{-6})} = 28,43 \text{ A} \\ \delta = 0,66 \quad I_Q &= \frac{10}{1-0,66} + \frac{300(0,66)(1-0,66)}{2 \cdot (100 \times 10^3)(44 \times 10^{-6})} = 37,5 \text{ A} \end{aligned}$$

$$I_{Qmax} = 37,5 \text{ A}$$

c) R tal que $\Delta V_o < 0,001 V_o$

$$\Delta V_o = \frac{Q^-}{C} = \frac{Q^+}{C}$$

$$Q^- = I_o \cdot \Delta T$$


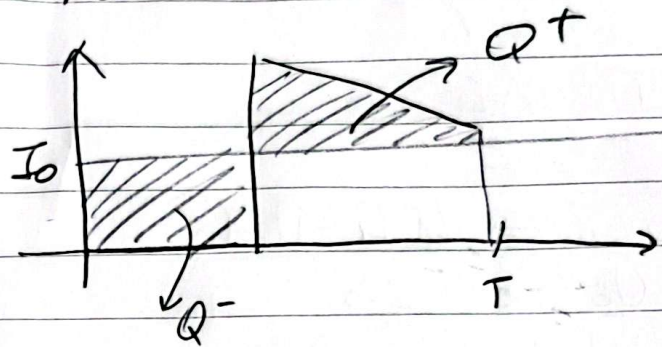


$$\Delta V_{o\text{max}} = \frac{Q^-}{C} = \frac{I_o \Delta t_{\text{max}} T}{C}$$

$$C = \frac{I_o \Delta t_{\text{max}} T}{\Delta V_{o\text{max}}} = \frac{(10) \cdot (0,66)}{0,001 \cdot 300 \cdot (100 \times 10^3)} = 222 \mu\text{F}$$

d) Circuito Snubber de Apagado

$$t_f = 67 \text{ ns}$$

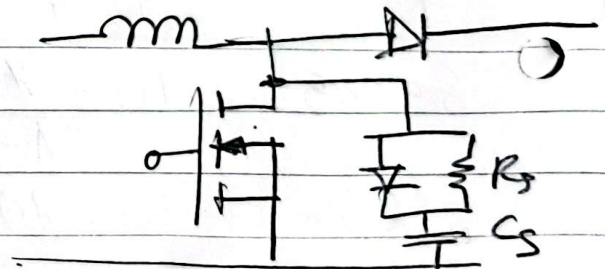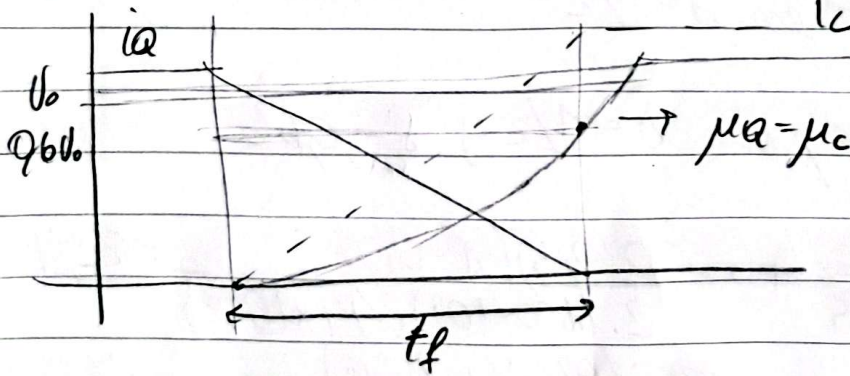

$$\Delta \mu_c = Q / C_s$$

$$Q = \int_0^{t_f} i_c(t) dt$$

$$i_c(t) = \frac{I_{a\text{max}} t}{t_f}$$

$$Q = \frac{I_{a\text{max}} t_f^2}{2} = \frac{I_{a\text{max}} t_f}{2}$$

$$\Delta v_c = \frac{I_{\text{max}} t_f}{2C_s}$$

$$C_s = \frac{I_{\text{max}} t_f}{2\Delta v_c}$$

$$C_s = \frac{(137,5 \text{ A}) \cdot (67 \times 10^{-9})}{2 \cdot (0,6 \times 300)} = 6,9 \text{ nF}$$

• Tiempo mín de descarga del condensador: $S_{\text{min}} T$

$$3R_s C_s \leq S_{\text{min}} T \Rightarrow R_s \leq \frac{S_{\text{min}} T}{3C_s} = 79 \text{ m}\Omega$$

$$P_{RS} = \frac{E_C}{T} = \frac{1}{T} \frac{1}{2} C_s V^2 = \frac{(6,9 \times 10^{-9}) \cdot (300^2) \cdot (100 \times 10^3)}{2}$$

$$P_{RS} = 31,4 \text{ W}$$