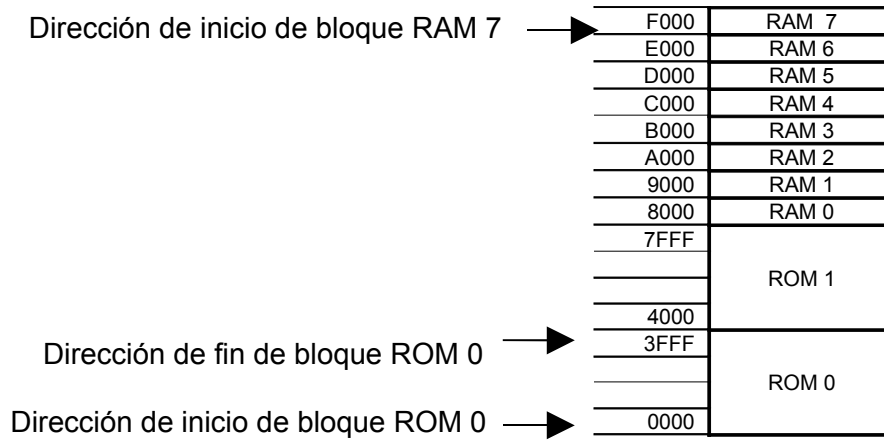


## Practico 4 Memorias

### Ejercicio 1

Se usaran 8 chips de memoria RAM y 2 chips de ROM.




### Ejercicio 2


E000	CS07
C000	CS06
A000	CS05
8000	CS04
6000	CS03
4000	CS02
2000	CS01
0000	CS00

### Ejercicio 3


Caso 1

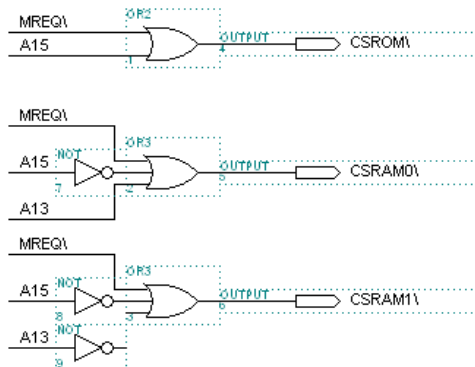

Caso 2

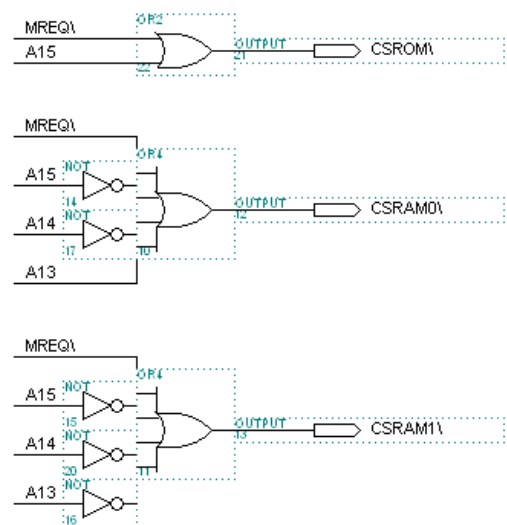

**Ejercicio 5**

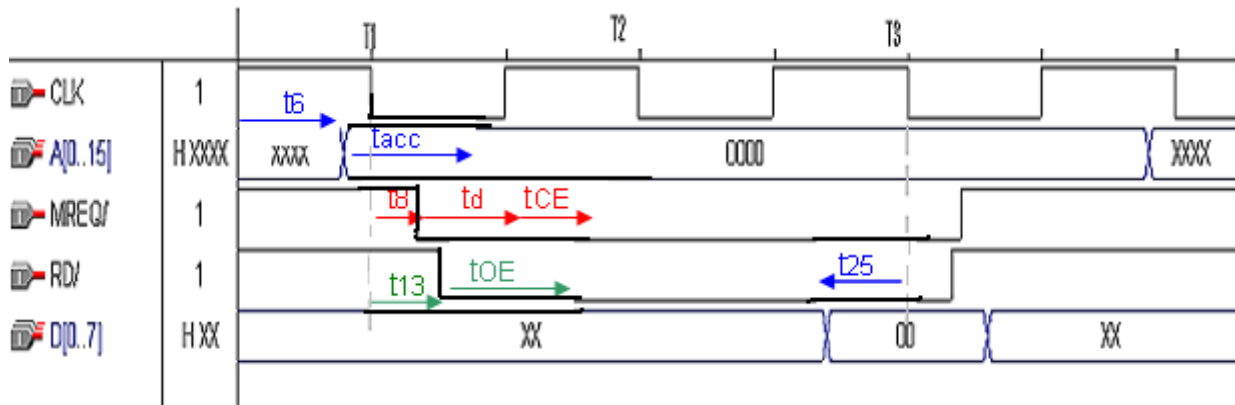

datos de letra:  
 $T = 162\text{ns}$   
 $Td_{\text{max}} = 30\text{ns}$

datos de cartilla del Z80:  
 $t6_{\text{max}} = 90\text{ns}$   
 $t13_{\text{max}} = 80\text{ns}$   
 $t8_{\text{max}} = 70\text{ns}$   
 $t25_{\text{min}} = 40\text{ns}$

- 1)  $T1 + T2 + T3/2 > t6_{\text{max}} + tacc_{\text{max}} + t25_{\text{min}} \rightarrow tacc_{\text{max}} < 275\text{ns}$
- 2)  $T1/2 + T2 + T3/2 > t13_{\text{max}} + tOE_{\text{max}} + t25_{\text{min}} \rightarrow tOE_{\text{max}} < 204\text{ns}$
- 3)  $T1/2 + T2 + T3/2 > t8_{\text{max}} + td_{\text{max}} + tCE_{\text{max}} + t25_{\text{min}} \rightarrow tCE_{\text{max}} < 184\text{ns}$   
 $T1 + T2 + T3/2 > t6_{\text{max}} + td_{\text{max}} + tCE_{\text{max}} + t25_{\text{min}} \rightarrow tCE_{\text{max}} < 245\text{ns}$

La memoria más lenta de la tabla, que cumple con todas las restricciones es: 27128-1.