

Solución problema 2

**MS1**

Un.MS1	6000 V
fn.MS1	50 Hz
Sn.MS1	210 kVA
Xs.MS1	0.2 p.u.
E/i @ fn.MS1	1000 V/A

**MS2**

Un.MS2	400 V
fn.MS2	50 Hz
Sn.MS2	200 kVA
Xs.MS2	0.1 p.u.
E/i @ fn.MS2	100 V/A

**T**


Upn.T	6.3 kV
Usn.T	0.4 kV
Sn.T	500 kVA
Uz.T	0.05 p.u.

U.red	0.4 kV
-------	--------

**Planta**

S.Planta	300 kVA
cos.Phi.Planta	0.8 i

parte (1) →

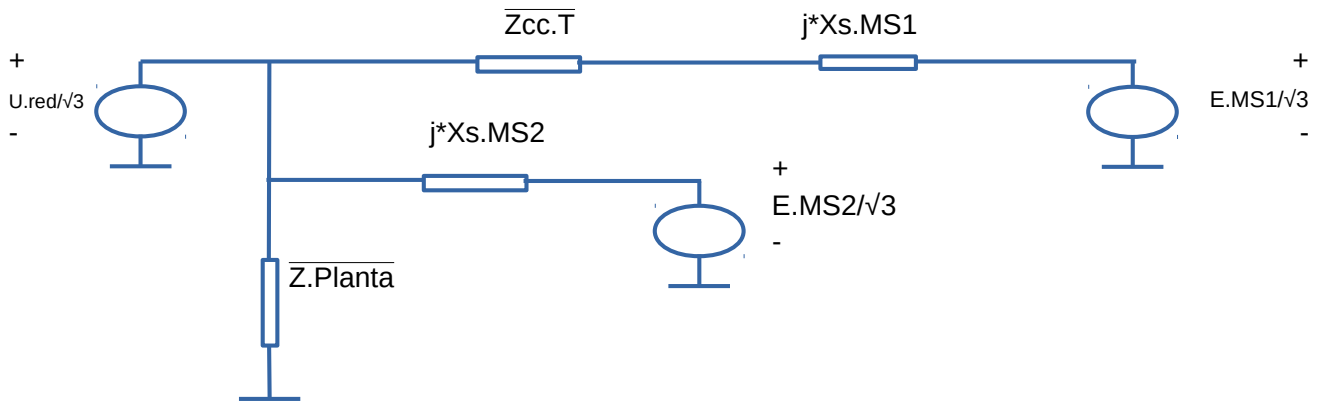

$\frac{U.red}{Z.Planta}$	$= \frac{U.red^2}{S.Planta} < ACOS(cos.Phi.Planta)$	
	$= \frac{(0.4kV)^2}{(300kVA) < ACOS(0.8)}$	
	0.4266666666666667+0.32j	Ohm
	<b>Rect: 0.4267+0.32j</b>	
	<b>Polar: 0.5333 &lt; 36.87°</b>	
$Zcc.T$	$= (Uz.T * (Usn.T)^2 / Sn.T)*j$	
	$= (0.05p.u. * (0.4kV)^2 / 500kVA)*j$	
	0.016j	Ohm
	<b>Rect: 0.016j</b>	
	<b>Polar: 0.016 &lt; 90°</b>	
$j*Xs.MS1.6000$	$= (Xs.MS1 * (Un.MS1)^2 / Sn.MS1)*j$	
	$= (0.2p.u. * (6000V)^2 / 210kVA)*j$	
	34.2857142857143j	Ohm
	<b>Rect: 34.29j</b>	
	<b>Polar: 34.29 &lt; 90°</b>	
$Xs.MS1.6000$	34.29 Ohm	
$Xs.MS1$	$= Xs.MS1.6000 * (Usn.T / Upn.T)^2$	
<b>Xs.MS1</b>	<b>0.138 Ohm</b>	

$$j \cdot X_s.MS2 = (X_s.MS2 \cdot (U_n.MS2)^2 / S_n.MS2) \cdot j$$

$$= (0.1 \text{ p.u.} \cdot (400 \text{ V})^2 / 200 \text{ kVA}) \cdot j$$

$$0.08j$$

Rect: 0.08j  
Polar: 0.08 < 90°

Ohm


**X<sub>s</sub>.MS2 = 0.08 Ohm**

parte (2) →

P.MS1 = 200 kW  
Q.MS1 = 0 kVAr  
S.MS1 = 200 kVA  
I.MS1 = S.MS1 / (√3 · U.red)  
= 200 kVA / (√3 · 0.4 kV)  
= 288.7 A

E.400.MS1/√3

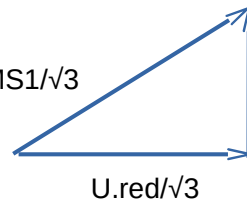(X<sub>s</sub>.MS1 + IM(Z<sub>cc</sub>.T)) · I.MS1



E.400.MS1 = √3 · √( (U.red/√3)<sup>2</sup> + (I.MS1 · (X<sub>s</sub>.MS1 + IM(Z<sub>cc</sub>.T)))<sup>2</sup> )  
= 407.4 V

E.400/i = 63.49 V/A

**i.MS1 = 6.416 A**

In.MS2 = S<sub>n</sub>.MS2 / (√3 · U.red)  
= 200 kVA / (√3 · 0.4 kV)  
= 288.7 A

E.MS2/√3

U.red/√3

0.75 · I<sub>n</sub>.MS2 · X<sub>s</sub>.MS2



75% = 216.5 A

E.MS2 = √3 · ( U.red/√3 + 0.75 · I<sub>n</sub>.MS2 · X<sub>s</sub>.MS2 )  
= 430.00 V

**i.MS2 = 4.300 A**

parte (3) →

P.generadores = 200 kW  
Q.generadores = 150 kVAr  
P.Planta = 240 kW  
Q.Planta = 180 kVAr  
P.a.la.red = -40 kW  
Q.a.la.red = -30 kVAr  
PF.visto.desde.red = COS( ATG(Q.a.la.red/P.a.la.red) )  
**0.8 inductivo**

parte (4) →

P.MS2 = 0 kW  
Q.MS2 = 180 kVAr  
S.MS2 = 180 kVA  
I.MS2 = S.MS2 / (√3 · U.red)  
= 180 kVA / (√3 · 0.4 kV)  
= 259.8 A

E.MS2/√3

U.red/√3

I.MS2 · X<sub>s</sub>.MS2



E.MS2 = √3 · ( U.red/√3 + I.MS2 · X<sub>s</sub>.MS2 )  
= 436.0 V

**i.MS2 = 4.360 A**