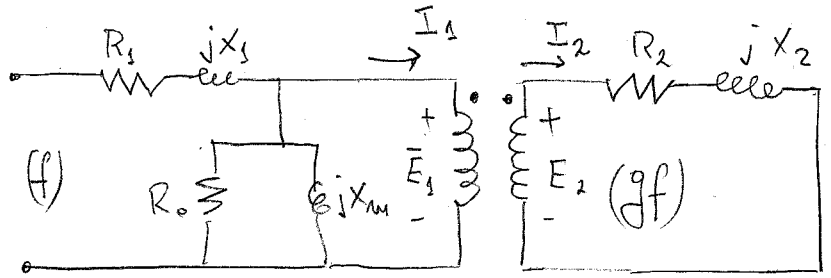


# Motor de Inducción

Modelo:

$$\begin{cases} \frac{\bar{E}_1}{N_1} = \frac{\bar{E}_2}{N_2} \\ N_1 \bar{I}_1 = N_2 \bar{I}_2 \end{cases}$$



$$X_2 = 2\pi g f L_{f2} = g X_2' \quad \text{con } X_2' = 2\pi f L_{f2}$$


Se pase la impedancia de C.C. de rotor al estator:

$$\bar{E}_2 = \bar{z}_2 \bar{I}_2 \quad \text{con } \bar{z}_2 = R_2 + j g X_2'$$


$$\Rightarrow g \frac{N_2}{N_1} \bar{E}_1 = \bar{z}_2 \frac{N_1}{N_2} \bar{I}_1 \Rightarrow \frac{\bar{E}_1}{\bar{I}_1} = \left(\frac{N_1}{N_2}\right)^2 \frac{\bar{z}_2}{g} = \left(\frac{N_1}{N_2}\right)^2 \frac{R_2}{g} + j \left(\frac{N_1}{N_2}\right)^2 \frac{g X_2'}{g}$$

$$\Rightarrow \frac{\bar{E}_1}{\bar{I}_1} = \bar{z}_v = \frac{R_{2e}}{g} + j X_{2e} \quad \text{con: } \begin{cases} R_{2e} = \left(\frac{N_1}{N_2}\right)^2 R_2 \\ X_{2e} = \left(\frac{N_1}{N_2}\right)^2 X_2' \end{cases}$$

Entonces el circuito queda:

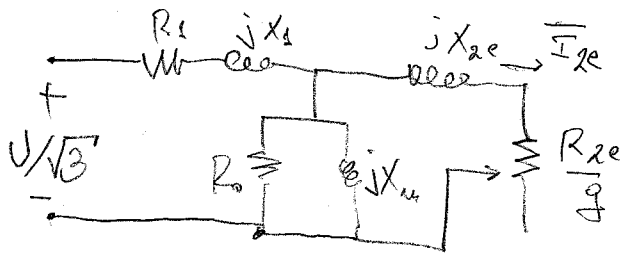


Circuito Equivalente Aproximado:

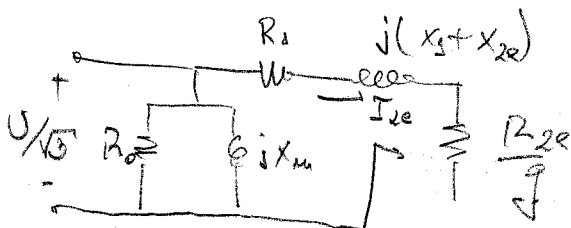

Este circuito se usará para la resolución de los problemas del práctico:

# Curva Par-velocidad

## Balace de Potencia:

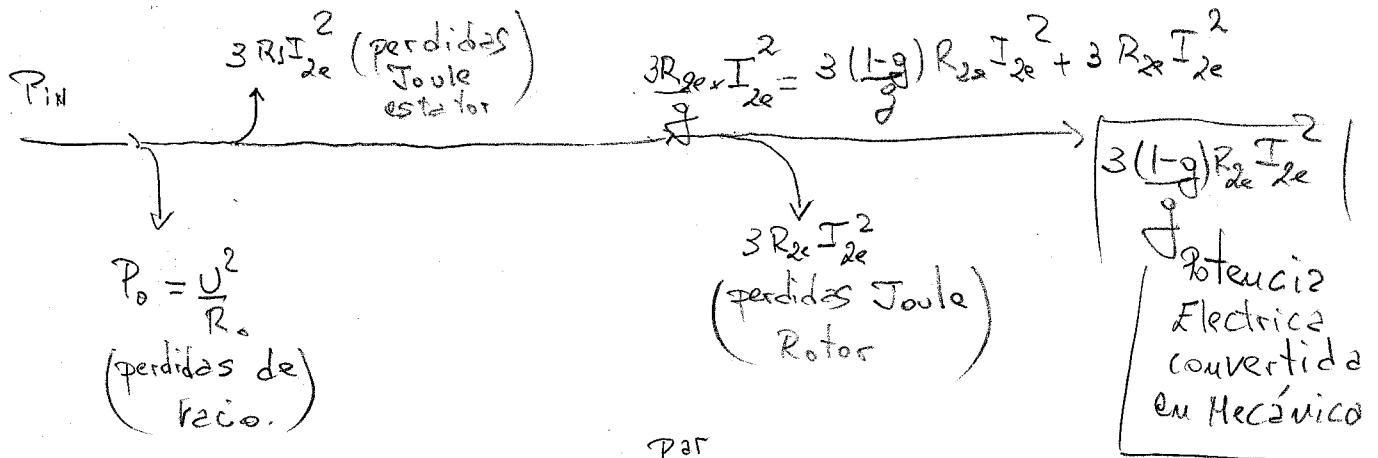


Entonces:  $P_m = 3R_{2e} \frac{(1-g)}{g} I_{2e}^2 = C \times \omega$

Deslizamiento:  $g = \frac{\omega_s - \omega}{\omega_s} = \frac{n_s - n}{n_s} \Rightarrow \omega = (1-g)\omega_s$

$\Rightarrow \left| C = \frac{3}{\omega_s} \frac{R_{2e}}{g} I_{2e}^2 \right| \neq$

$I_{2e} = \frac{U/\sqrt{3}}{(R_1 + \frac{R_{2e}}{g}) + j(X_1 + X_{2e})}$

$|I_{2e}| = \frac{U/\sqrt{3}}{(R_1 + \frac{R_{2e}}{g})^2 + (X_1 + X_{2e})^2} \Rightarrow \left| C = \frac{R_{2e}}{g \omega_s} \frac{U^2}{(R_1 + \frac{R_{2e}}{g})^2 + (X_1 + X_{2e})^2} \right|$

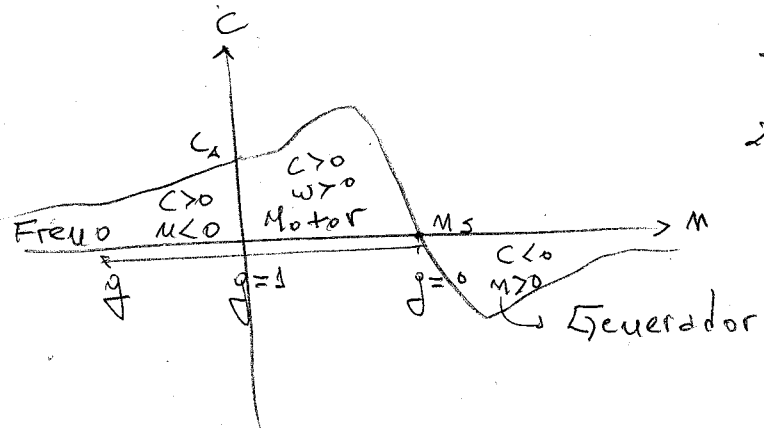

1) Par:  $C \propto U^2 !!$

2) Tres zonas de funcionamiento

- Motor  $P_m > 0$   $\begin{cases} C > 0 \\ \omega > 0 \end{cases}$

- Generador  $P_m < 0$   $\begin{cases} C < 0 \\ \omega > 0 \end{cases}$

- Freno  $P_m < 0$   $\begin{cases} C > 0 \\ n < 0 \end{cases}$