
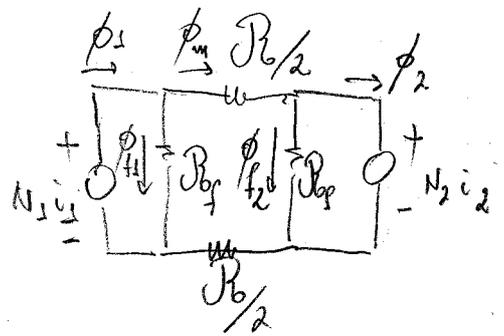


Transformador Real

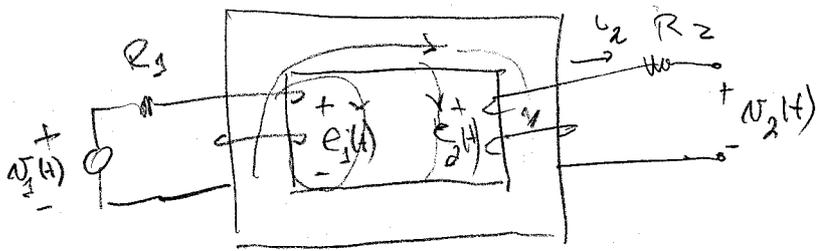

$$v_1(t) = R_1 i_1 + e_1(t)$$

$$v_2(t) = R_2 i_2 + e_2(t)$$

$$e_1(t) = N_1 \frac{d\phi_1}{dt}$$

$$e_2(t) = N_2 \frac{d\phi_2}{dt}$$

$$\phi_1 = \phi_{l1} + \phi_m$$

$$\phi_2 = \phi_m - \phi_{l2}$$

$$\Rightarrow v_1 = R_1 i_1 + N_1 \frac{d\phi_1}{dt} + N_1 \frac{d\phi_m}{dt}$$

$$v_2 = -R_2 i_2 - N_2 \frac{d\phi_2}{dt} + N_2 \frac{d\phi_m}{dt}$$

$$\phi_{l1} = \frac{N_1 i_1}{\mathcal{R}_f}$$

$$\phi_{l2} = \frac{N_2 i_2}{\mathcal{R}_f}$$

$$\left. \begin{aligned} N_1 \frac{d\phi_m}{dt} &= v_p \\ N_2 \frac{d\phi_m}{dt} &= v_s \end{aligned} \right\} \Rightarrow \left[\begin{array}{c} v_p \\ v_s \end{array} \right] = \left[\begin{array}{c} N_1 \\ N_2 \end{array} \right] \frac{d\phi_m}{dt}$$

Reluctancia por aire (\$\mu_0\$)

$$\Rightarrow v_1 = R_1 i_1 + \frac{N_1^2}{\mathcal{R}_f} \frac{di_1}{dt} + v_p$$

$$v_2 = -R_2 i_2 - \frac{N_2^2}{\mathcal{R}_f} \frac{di_2}{dt} + v_s$$

$$\frac{N_1^2}{\mathcal{R}_f} = L_{f1}$$

$$\frac{N_2^2}{\mathcal{R}_f} = L_{f2}$$

Regimen Sinusoidal:


$$\bar{V}_1 = R_1 \bar{I}_1 + jX_1 \bar{I}_1 + V_p$$

$$\bar{V}_2 = -R_2 \bar{I}_2 - jX_2 \bar{I}_2 + V_s$$

$$\frac{V_p}{N_1} = \frac{V_s}{N_2}$$

$$X_1 = \omega L_{f1}$$

$$X_2 = \omega L_{f2}$$

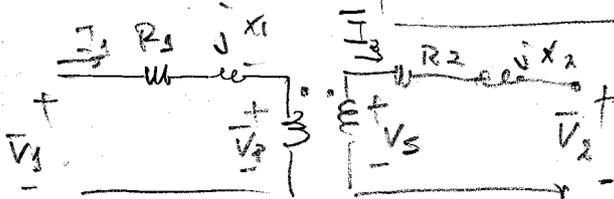


reluctancia del circ. magnetico (hierro)

$$\text{Ademas: } N_1 i_1 - N_2 i_2 = \mathcal{R}_0 \phi_m \Rightarrow N_1 i_m = \mathcal{R}_0 \phi_m$$


$$\text{con } i_m = i_1 - \frac{N_2}{N_1} i_2$$

$$\Rightarrow v_p = N_1 \frac{d\phi_m}{dt} = \frac{N_1^2}{\mathcal{R}_0} \frac{di_m}{dt} = L_m \frac{di_m}{dt} \Rightarrow \left[\begin{array}{l} V_p = jX_m \bar{I}_m \\ \bar{I}_m = \bar{I}_1 - \frac{N_2}{N_1} \bar{I}_2 \end{array} \right]$$

Autouces:

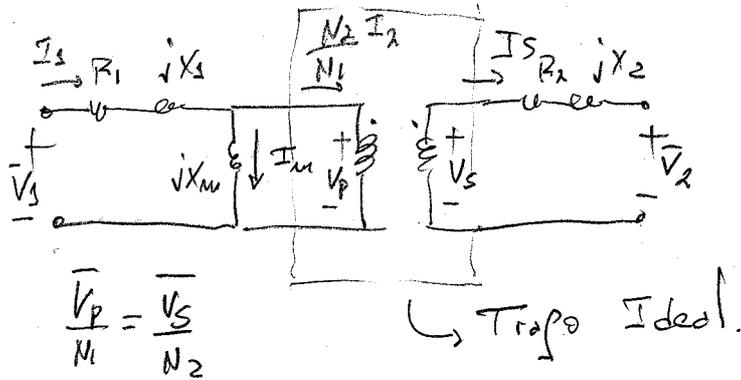

Trafo Real: Aproximacion:

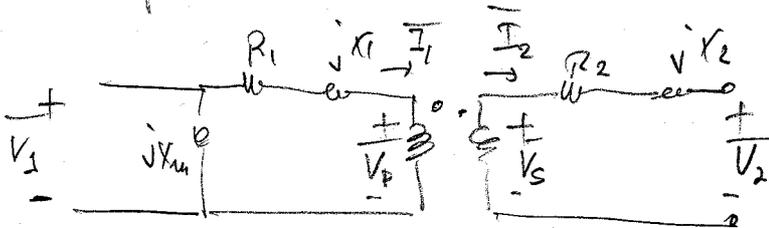


Trafo Real: Perdidas en el hierro.

$$P_{Fe} = (\alpha_f + b_f \rho^2) \phi^2 \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \quad P_{Fe} = \left(\frac{\alpha_f}{f} + b_f \right) V^2 = \frac{V^2}{R_o}$$


$$V = k_f \phi$$

↳ dependo de f!!

⇒ Para modelar agrega R_o en paralelo:

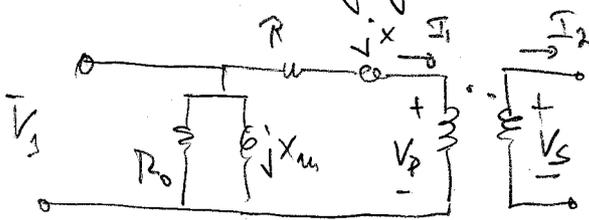


Modelo a usar en el curso

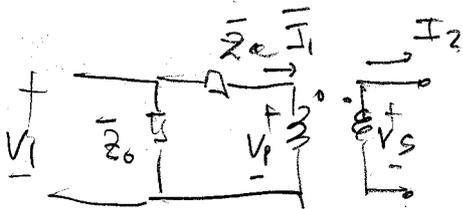


$$\left\{ \begin{array}{l} \frac{\bar{V}_p}{N_1} = \frac{\bar{V}_s}{N_2} \\ N_1 \bar{I}_1 = N_2 \bar{I}_2 \\ R = R_1 + \left(\frac{N_1}{N_2} \right)^2 R_2 \\ X = X_1 + \left(\frac{N_1}{N_2} \right)^2 X_2 \end{array} \right.$$

Ensayos:

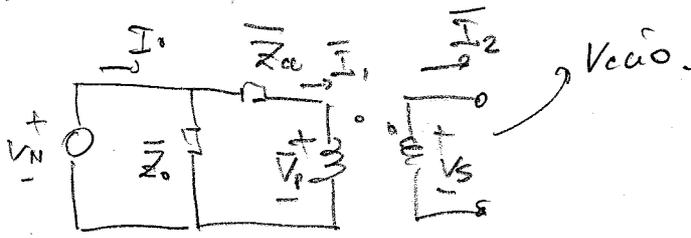1) Ensayo de vacío: Se hace a $V_1 = V_N$ $f = f_N$



$I_2 = 0 \Rightarrow I_1 = 0$

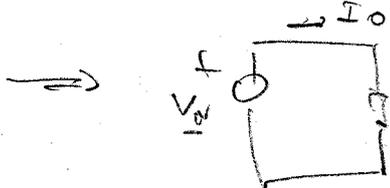


Se mide V_0, I_0, P_0

$P_0 = \frac{V_0^2}{R_0} \Rightarrow R_0$

$Q_0 = \sqrt{(V_0 I_0)^2 - P_0^2}$

$Q_0 = \frac{V_0^2}{X_m} \Rightarrow X_m$

Se puede usar:

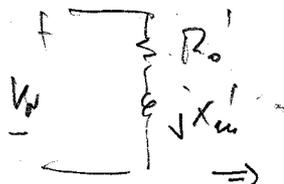


Pero:

$P_0 = R_0' I_0^2$


$Q_0 = X_m' I_0^2$

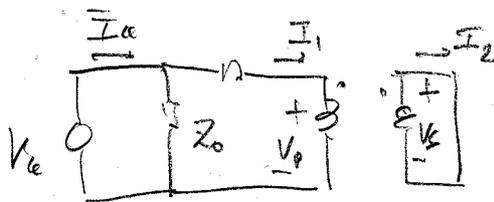2) Ensayo Cortocircuito: @ $V \ll V_N / I_a \leq I_N$




$\hookrightarrow 2\% - 15\%$

$V_s = 0 \Rightarrow V_p = 0$

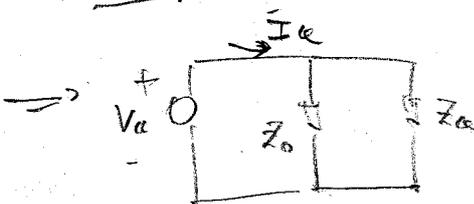

$Z_0 \gg Z_c$

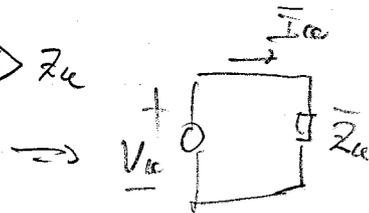

Mido:

V_a, I_a, P_{cc}

$\bar{Z}_a = \frac{V_a}{I_a} \angle \text{Arco} \left(\frac{P_{cc}}{V_a I_a} \right)$

Ejemplo: Tipo 6300 V / 440 V 60 Hz 100 kVA

1) Ensayo de Vacío: 220 V 50 Hz 5 A 1 kW

$\textcircled{220V}$
 $\textcircled{50Hz}$

$$R_{01} = \frac{220^2}{1000} = 48,4 \Omega$$

$$X_{01} = \frac{220^2}{458,3} = 105,6 \Omega$$

$$Q_0 = \sqrt{(220 \times 5)^2 - 1000^2} = 458,3 \text{ VAR}$$

El ensayo fue realizado alimentando el transformador desde el bobinado de B.T. pero a una tensión menor a la nominal

$$\phi_{440,60} = \frac{440}{k \cdot 60} = \frac{7,3}{k}$$

$$\phi_{220,50} = \frac{220}{k \cdot 50} = \frac{4,4}{k}$$

$\Rightarrow \phi_{220,50} < \phi_{440,60} \Rightarrow \text{No sirve}$
 $\Rightarrow L_m = \frac{N^2}{\phi} = \text{cte} \quad X_0 = \omega L_m$

$\textcircled{440,60}$

$\Rightarrow X_{02} = \frac{6}{5} X_{01} = 126,7 \Omega$
histeresis

$$P_0 = (a_f + b_f \phi^2) \phi^2 = \left(\frac{a_1}{f} + \frac{b_1}{f} \right) V^2 = P_H + P_F$$


Suponemos $P_H = P_F = 500 \text{ W}$

$\textcircled{220V, 50Hz}$

$$\Rightarrow \left\{ \begin{array}{l} \frac{a_1}{50} \times 220^2 = 500 \rightarrow a_1 = 0,52 \\ b_1 = \frac{500}{220^2} \rightarrow b_1 = 0,01 \end{array} \right.$$

$$P_{0, 440,60} = \left(\frac{0,52}{60} + 0,01 \right) 440^2 \approx 3614 \text{ W} = \frac{440^2}{R_{02}} \Rightarrow R_{02} = 53,6 \Omega$$

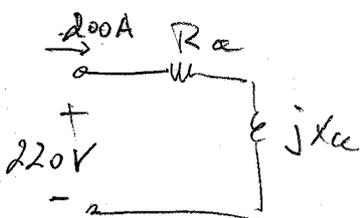2) Ensayo Cortocircuito: 220 V 50 Hz 15 A 8 kW



obs. 220V es $\approx 3,5\%$ de 6300V y 50% de 440V \Rightarrow el ensayo fue hecho alimentando el trazo desde el bobinado de AT.

$$\Rightarrow \bar{Z}_{ca} = \frac{220}{15} \angle \arcsin \frac{1500}{220 \times 15} = 14,7 \angle 63^\circ = (6,7 - j 13,1) \Omega$$

efecto pelicular

R_{ca1} X_{ca2}

@ 220V, 50Hz

$$R_a = R_w + R_{ad} \approx R_{cu} \Rightarrow R_{ca2} = R_{ca1}$$


↓ \hookrightarrow depende de f

No depende de V o f

$$X_{ca1} = 2\pi \times 50 \text{ } \mu\text{p} = \frac{N^2}{P_{op} f} \Rightarrow X_{ca2} = \frac{6}{5} X_{ca1} = 15,72 \Omega$$

$\hookrightarrow \mu_0 \Rightarrow$ No saturar

Modelo:

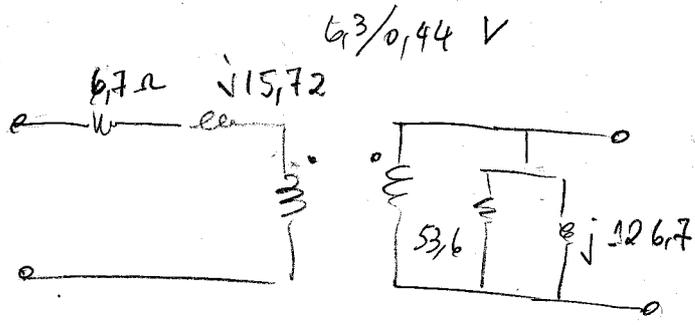

Presendo todo @ BT.

$$R_{aBT} = \left(\frac{440}{6300}\right)^2 \times 6,7 = 0,033 \Omega$$

$$X_{caBT} = \left(\frac{440}{6300}\right)^2 \times 15,72 = 0,077 \Omega$$

