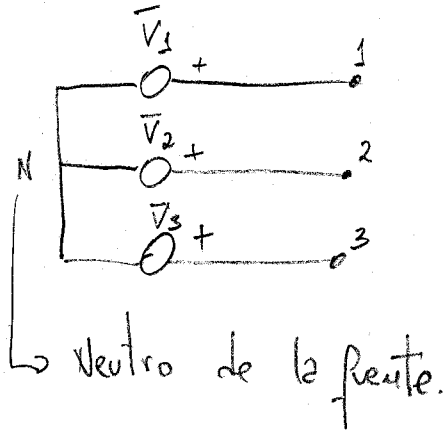


Circuitos Trifasicos.


Fuente.



$$\left. \begin{aligned} \bar{V}_1 &= V \angle 0^\circ \\ \bar{V}_2 &= V \angle -120^\circ \\ \bar{V}_3 &= V \angle 120^\circ \end{aligned} \right\} \text{Fuente trifasica perfecta.}$$


↳ tensiones fase neutro \Rightarrow tensiones de fase
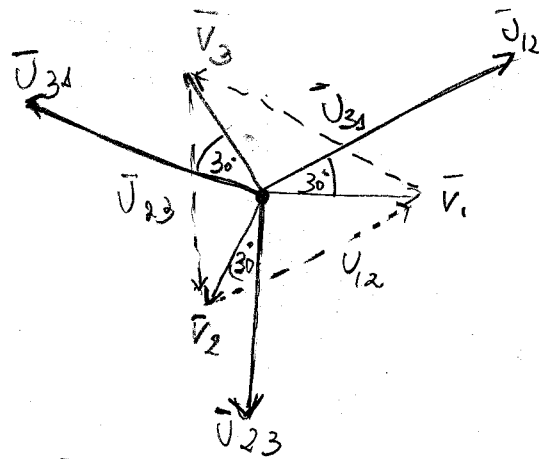
$$\left. \begin{aligned} \bar{U}_{12} &= \bar{V}_1 - \bar{V}_2 \\ \bar{U}_{23} &= \bar{V}_2 - \bar{V}_3 \\ \bar{U}_{31} &= \bar{V}_3 - \bar{V}_1 \end{aligned} \right\} \text{Tensiones de linea o compuestas.}$$




$$|\bar{U}_{12}| = |\bar{U}_{23}| = |\bar{U}_{31}| = \sqrt{3} V$$

Cargas:

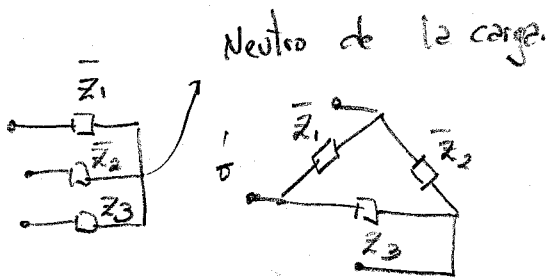

Si adem\u00e1s $\bar{Z}_1 = \bar{Z}_2 = \bar{Z}_3 = \bar{Z}$
 \Rightarrow Cargas Equilibradas.

Corrientes de linea y de fase

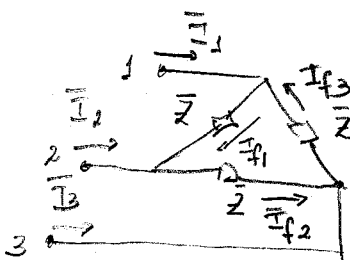

$\bar{I}_1, \bar{I}_2, \bar{I}_3$ - Corrientes de linea.



$\bar{I}_{f1}, \bar{I}_{f2}, \bar{I}_{f3}$ - Corrientes de fase.

$$\left\{ \begin{aligned} \bar{I}_1 &= \bar{I}_{f1} - \bar{I}_{f3} \\ \bar{I}_2 &= \bar{I}_{f2} - \bar{I}_{f1} \\ \bar{I}_3 &= \bar{I}_{f3} - \bar{I}_{f2} \end{aligned} \right.$$

$\bar{Z} = Z \angle \varphi$

tensión de línea: U

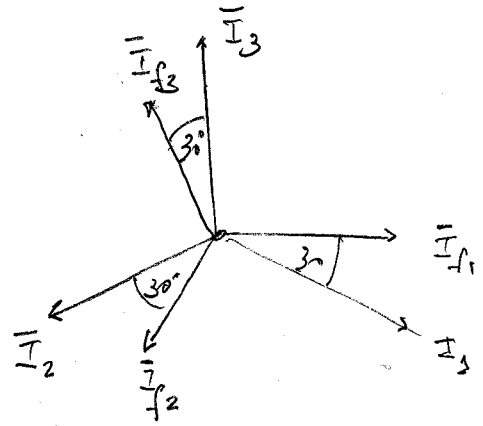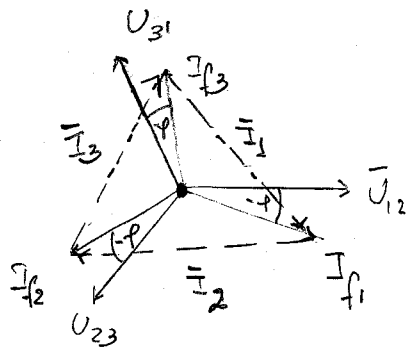
$$\begin{cases} \bar{I}_{f1} = \frac{\bar{U}_{12}}{Z \angle \varphi} = \frac{U}{Z} \angle -\varphi \\ \bar{I}_{f2} = \frac{\bar{U}_{23}}{Z \angle \varphi} = \frac{U}{Z} \angle -120 - \varphi \\ \bar{I}_{f3} = \frac{\bar{U}_{31}}{Z \angle \varphi} = \frac{U}{Z} \angle 120 - \varphi \end{cases}$$




Entonces: $|\bar{I}_1| = |\bar{I}_2| = |\bar{I}_3| = \sqrt{3} \frac{U}{Z}$

con $|\bar{I}_{f1}| = |\bar{I}_{f2}| = |\bar{I}_{f3}| = \frac{U}{Z}$

Circuito Monofásico Equivalente.

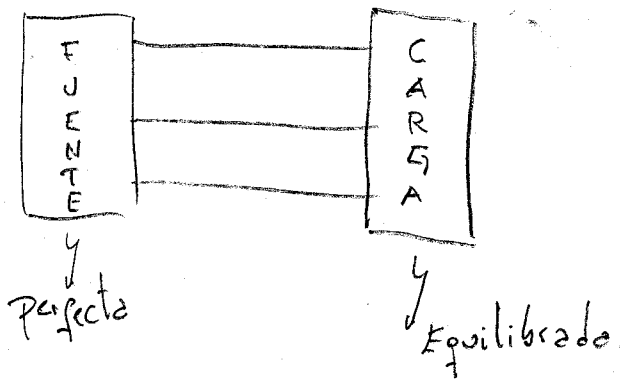

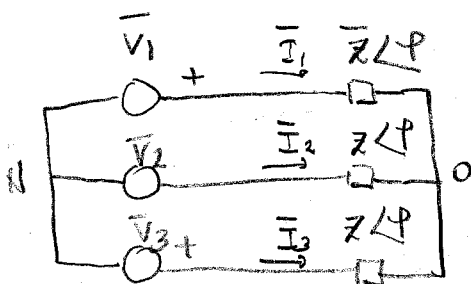- La fuente siempre se puede representar en 1
- La carga siempre se puede representar en 1



$$\begin{aligned} \bar{V}_1 &= \bar{Z} \bar{I}_1 + \bar{V}_{0N} \\ \bar{V}_2 &= \bar{Z} \bar{I}_2 + \bar{V}_{0N} \\ \bar{V}_3 &= \bar{Z} \bar{I}_3 + \bar{V}_{0N} \end{aligned}$$

$$\begin{cases} \bar{V}_1 = V \angle 0^\circ \\ \bar{V}_2 = V \angle -120^\circ \\ \bar{V}_3 = V \angle 120^\circ \end{cases}$$

$$\bar{V}_1 + \bar{V}_2 + \bar{V}_3 = \bar{Z}(\bar{I}_1 + \bar{I}_2 + \bar{I}_3) + 3\bar{V}_{0N} \Rightarrow \bar{V}_{0N} = 0 \Rightarrow \underline{\underline{\bar{V}_0 = 0}}$$

|| fuente perfecta || Kirchhoff


El neutro de la fuente está a la misma tensión que el neutro de la carga.

$\Rightarrow \bar{I}_1 = \frac{\bar{V}_1}{\bar{Z}}$




$\Rightarrow \bar{I}_1 = \frac{V}{Z} \angle -\varphi$

$$\bar{I}_2 = \frac{\bar{V}_2}{2}$$

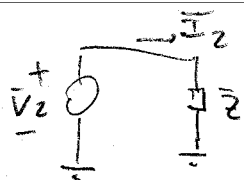


$$\Rightarrow \bar{I}_2 = \frac{V}{2} \angle -120^\circ - \varphi$$

$$\bar{I}_3 = \frac{\bar{V}_3}{2}$$

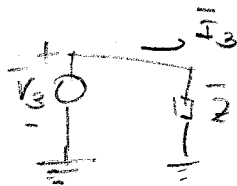


$$\Rightarrow \bar{I}_3 = \frac{V}{2} \angle 120^\circ - \varphi$$

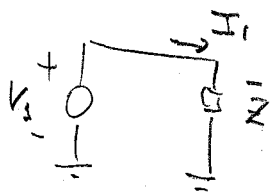- observar:
- Las tres corrientes tienen el mismo modulo.
 - La fase de \bar{I}_2 y \bar{I}_3 se puede obtener de \bar{I}_1 restando 120° y sumando 120° a la fase de esta ultima.
 - Solo resolvio:



Circuito Monofasico Equivalente

Ejemplo


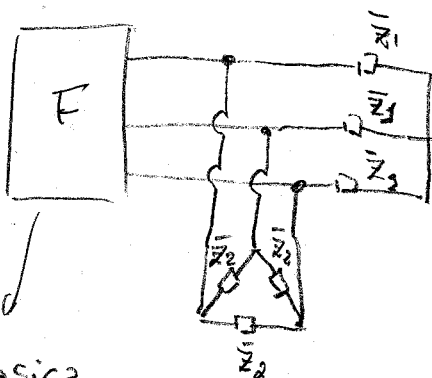


$$\bar{Z}_1 = 3j \Omega$$

$$\bar{Z}_2 = 9j \Omega$$

Determinar corriente entregada por la fuente

Trifasica perfecta tension de linea 380V

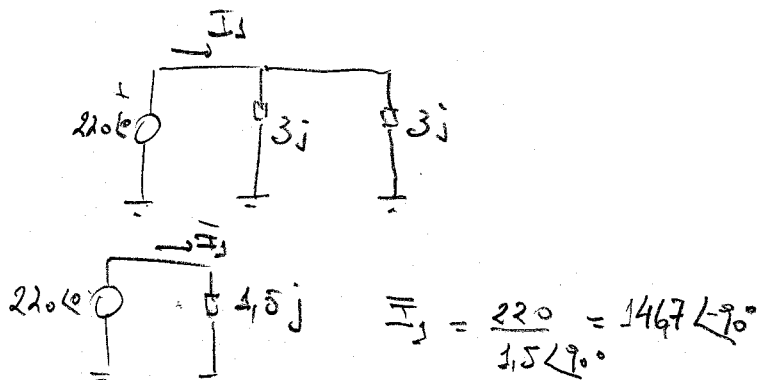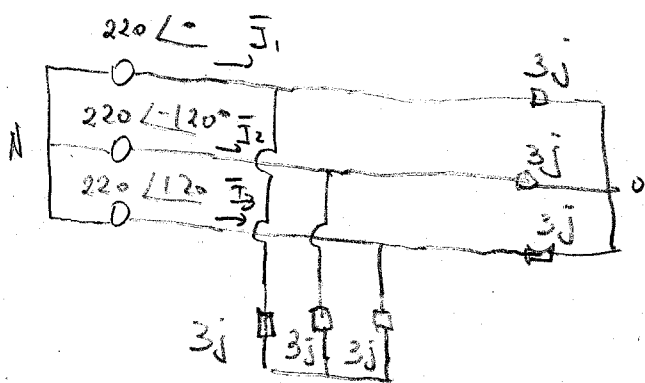

$$\bar{I}_1 = \frac{220}{1.5} \angle 90^\circ = 146.7 \angle 90^\circ$$

$$\Rightarrow \bar{I}_2 = 146.7 \angle -120^\circ - 90^\circ = 146.7 \angle -210^\circ$$

$$\bar{I}_3 = 146.7 \angle 120^\circ - 90^\circ = 146.7 \angle 30^\circ$$

