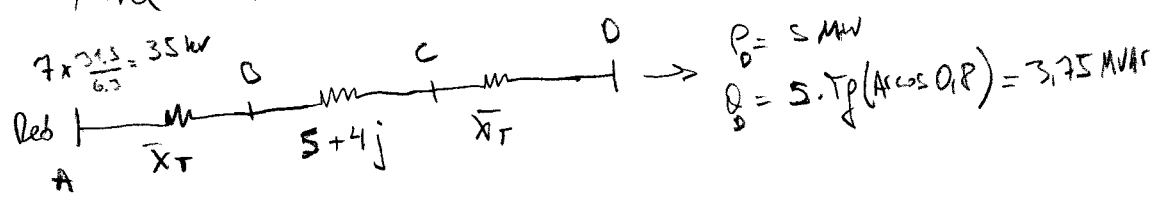


Problema 1

Nivel 31,5 kV



$$\bar{X}_T = 0,08 \times \frac{31,5^2}{10} j = 7,938 j$$


$$U_A^2 = U_D^2 + \frac{z^2}{U_D^2} (P_D^2 + Q_D^2) + 2z [P_D \cos \varphi + Q_D \sin \varphi]$$

$$\bar{z} = 5 + 4j + 2\bar{X}_T = 5 + 19,88j = 20,5 \angle 75,88^\circ (\Omega)$$

$$U_D = \begin{matrix} 31,77 \text{ kV} \checkmark \\ 4,032 \text{ kV} \times \end{matrix}$$



$$U_C = \left| U_D + \frac{\bar{X}_T}{U_D} \hat{S}_D \right| = 32,73 \text{ kV}$$

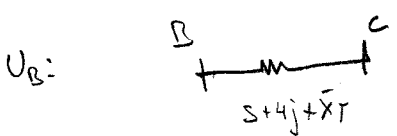


$$U_B = \left| U_D + \frac{(5 + 4j + \bar{X}_T)}{U_D} \hat{S}_D \right| = 33,99 \text{ kV}$$

$$\Delta V_{BC} = 33,99 - 32,73 = 1,26 \text{ kV}$$

Problema 2

Nivel 31,5 kV

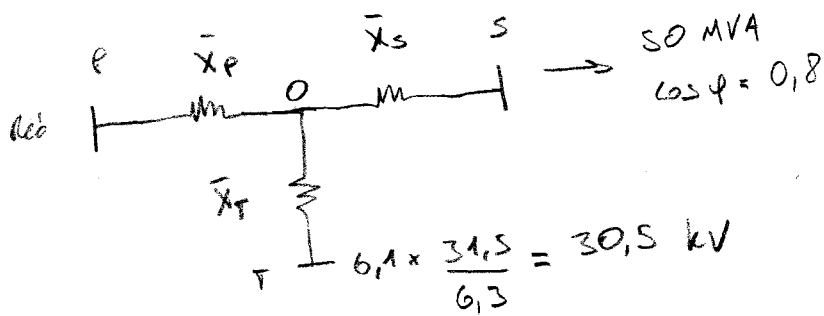

$$P_s = 50 \times 0,8 = 40 \text{ MW}$$

$$Q_s = 50 \times \sin(\arccos 0,8) = 30 \text{ MVAR}$$


$$U_0 = U_t = 30,5 \text{ kV}$$

$$\bar{X}_{ps} = 0,11 \times \frac{31,5^2}{120} j = 0,9096 j \text{ } (\Omega)$$

$$\bar{X}_{pt} = 0,35 \times \frac{31,5^2}{120} j = 2,894 j \text{ } (\Omega)$$

$$\bar{X}_{st} = 0,25 \times \frac{31,5^2}{120} j = 2,067 j \text{ } (\Omega)$$

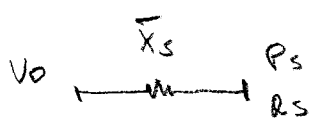
$$\bar{X}_p = 0,8683 j \quad \bar{X}_s = 0,0413$$



$$U_0^2 = U_s^2 + \frac{X_s^2}{U_s^2} \cdot (P_s^2 + Q_s^2) + 2X_s Q_s$$

$$U_s = 30,46 \text{ kV}$$

$$0,678 \text{ kV} \times$$

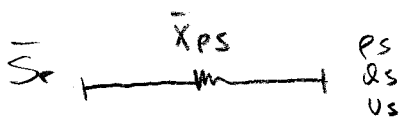

$$\bar{S}_p = \bar{S}_s + \frac{\bar{X}_s}{U_s^2} \cdot S_s^2 = 40 + 32,45j \text{ (MVA)}$$

$$40 + 49,77j \text{ (MVA)} \times$$