

1) Para que en p.u. nos quede un trafico de relacion 1:1 $\Rightarrow \begin{cases} \frac{V_{base2}}{V_{base1}} = \frac{V_{PT1}}{V_{ST1}} & , \quad \frac{V_{base2}}{V_{base3}} = \frac{V_{PT2}}{V_{ST2}} \\ S_{base1} = S_{base2} = S_{base3} \end{cases}$

Elijo: $\begin{cases} S_{base} = 200 \text{ MVA} \\ U_{base1} = 150 \text{ kV} \end{cases}$

$\Rightarrow U_{base2} = \frac{500}{150} \times 150 = 500 \text{ kV}$

$\Rightarrow U_{base3} = \frac{150}{525} \times 500 = 142,86 \text{ kV}$

Impedancias trafos: $Z_{base2} = \frac{U_{base2}^2}{S_{base2}} = \frac{500^2}{200} = 1250 \Omega$

\rightarrow Como los valores base son iguales a los nominales de $T_1 \Rightarrow \boxed{x_{T1} = 0,02 \text{ p.u.}}$


\rightarrow no es así para $T_2 \rightarrow \boxed{x_{T2} = 0,02 \times \frac{525^2}{200} \times \frac{1}{Z_{base2}} = 0,022 \text{ p.u.}}$

2) $\begin{cases} \bar{z} = (r + j\omega l) \cdot L \cdot \frac{1}{Z_{base2}} \\ \bar{y} = (g + j\omega c) \cdot L \cdot \frac{1}{Y_{base2}} \rightarrow Y_{base2} = \frac{1}{Z_{base2}} \end{cases} \Rightarrow \begin{cases} \bar{z} = 0,016 + j0,131 \text{ p} \\ \bar{y} = j1,571 \text{ pu} \end{cases}$

$\bar{\theta} = \sqrt{\bar{z}\bar{y}} = 0,028 + j0,454$

$\bar{z}_{\pi} = \bar{z} \cdot \frac{\sinh(\bar{\theta})}{\bar{\theta}} = 0,015 + j0,126 \text{ p.u.}$

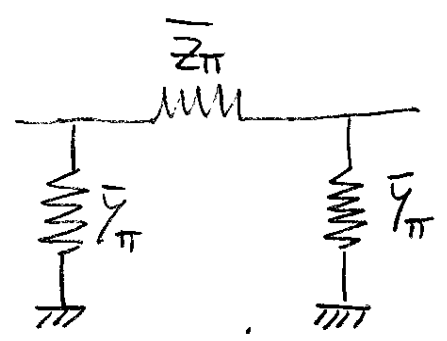$\bar{y}_{\pi} = \bar{y} \cdot \frac{\cosh(\bar{\theta}) - 1}{\bar{\theta} \cdot \sinh(\bar{\theta})} = 0,002 + j0,799 \text{ p.u.}$



3) Despreciando impedancias de los trafos, sólo nos queda la línea.

$$P.u. \begin{cases} \bar{A} = \cosh(\bar{\theta}) = 0,899 + j0,012 \\ \bar{B} = \bar{Z} \cdot \frac{\sinh(\bar{\theta})}{\bar{\theta}} = 0,015 + j0,126 \text{ p.u.} \\ \bar{C} = \bar{Y} \cdot \frac{\sinh(\bar{\theta})}{\bar{\theta}} = -0,006 + j1,518 \text{ p.u.} \\ \bar{D} = \cosh(\bar{\theta}) = 0,899 + j0,012 \end{cases}$$

$$\bar{S}_A = 150 - j50 \text{ MVA} \Rightarrow \bar{S}_A = 0,75 - j0,25 \text{ p.u.}$$

usando fórmula compleja $\bar{\mu}_B = \bar{D} \mu_A - \frac{\bar{B} \hat{S}_A}{\mu_A} \rightsquigarrow \bar{\mu}_A = \frac{150 \text{ kV}}{150 \text{ kV}} = 1 \text{ p.u.}$

$\Rightarrow \mu_B = 0,923 \text{ pu} \rightarrow$ la barra B está en la zona 3

$$\Rightarrow \boxed{U_B = \mu_B \times U_{\text{base } 3} = 131,9 \text{ kV}}$$

ahora halló P_B usando fórmula compleja:

$$\bar{S}_B = \hat{A} \cdot \bar{D} \cdot \bar{S}_A + \bar{B} \cdot \hat{C} \cdot \hat{S}_A - \hat{C} \cdot \bar{D} \cdot \mu_A^2 - \frac{\hat{A} \cdot \bar{B} \cdot S_A^2}{\mu_A^2} = 0,734 + j1,122 \text{ p.u.}$$

$\Rightarrow P_B = 0,734$ $\text{perd} = P_A - P_B = 0,75 - 0,734 = 0,016 \text{ p.u.}$

$$\boxed{P_{\text{perd}} = 0,016 \times P_{\text{base}} = 3,2 \text{ MW}}$$