

TRAMO 1 $t \in [0, T/2]$

$i_L(0^-) = 0$ (llave abierta)

$$\Rightarrow \begin{cases} i_s(t) = \frac{E}{r} (1 - e^{-t/\tau_1}) \\ v_s(t) = 0 \end{cases} \quad \tau_1 = \frac{L}{r} \quad t \in [0, T/2]$$

$$i_s(T/2) = \frac{E}{r} (1 - e^{-T/2\tau_1}) \approx \frac{E}{r}$$

TRAMO 2 $t \in [T/2, T]$


Delo pruvio

$$i_L(T/2^-) = i_s(T/2) = \frac{E}{r}$$


$$i_L(t) = i_s(t) = 0 \quad t \in [T/2, T]$$

$$\Rightarrow \frac{di_s}{dt} = -\frac{E}{r} \delta(t - T/2)$$

$$v_s = E \gamma(t) - L \frac{di_s}{dt} \underset{0}{=} -v_s(t) = E \gamma(t) + L \frac{E}{r} \delta(t - T/2) \quad t \in [T/2, T]$$

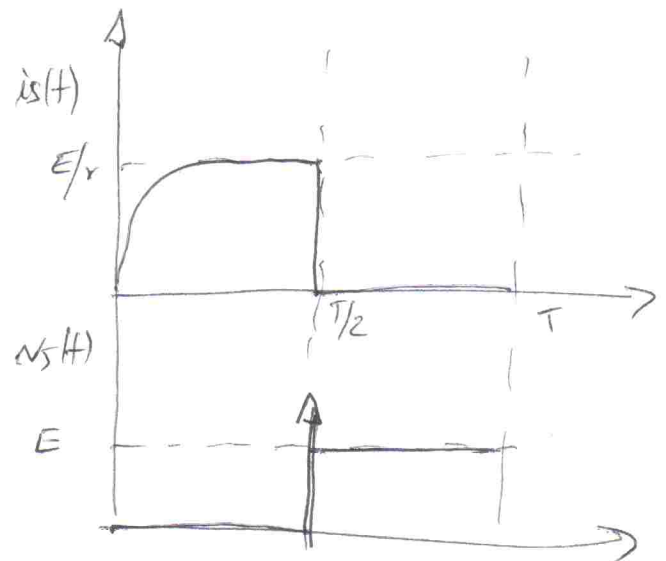

parte 2

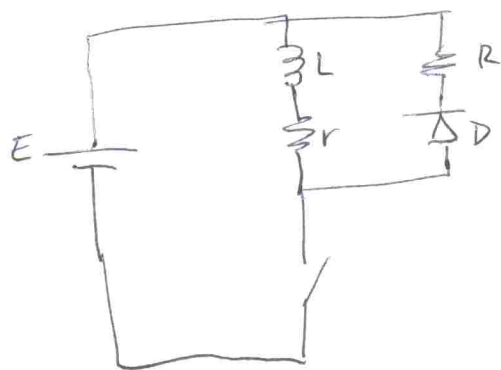

TRAMO 1 $t \in [0, T/2]$

Dato previo $i_L(0^-) = 0$, a verificar a posteriori.

D OFF

con S ON,
$$\begin{cases} i_L(t) = \frac{E}{r} (1 - e^{-t/\tau_1}) \\ i_D(t) = i_L(t) \\ v_D(t) = 0 \end{cases} \quad \tau_1 = \frac{L}{r} \quad t \in [0, T/2]$$

$v_D = -E$ D OFF

$$i_D(t) = 0$$


$$t \in [0, T/2]$$

TRAMO 2 $t \in [T/2, T]$

Dato previo $i_L(T/2^-) \approx \frac{E}{r}$ pues $\tau_1 \ll T/2$

S OFF

D ON

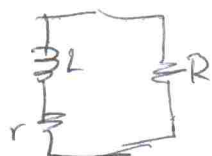

$$i_L(t) = \frac{E}{r} e^{-t'/\tau_2} \quad \tau_2 = \frac{L}{r+R} \ll \frac{L}{r} \ll T/2$$


$$v_D = E + R i_L(t) = E + R \frac{E}{r} e^{-t'/\tau_2}$$

$$t \in [T/2, T]$$

$$i_D = i_L(t) = \frac{E}{r} e^{-t'/\tau_2}$$

$$t' = t - T/2$$

$$i_D(t) = 0$$

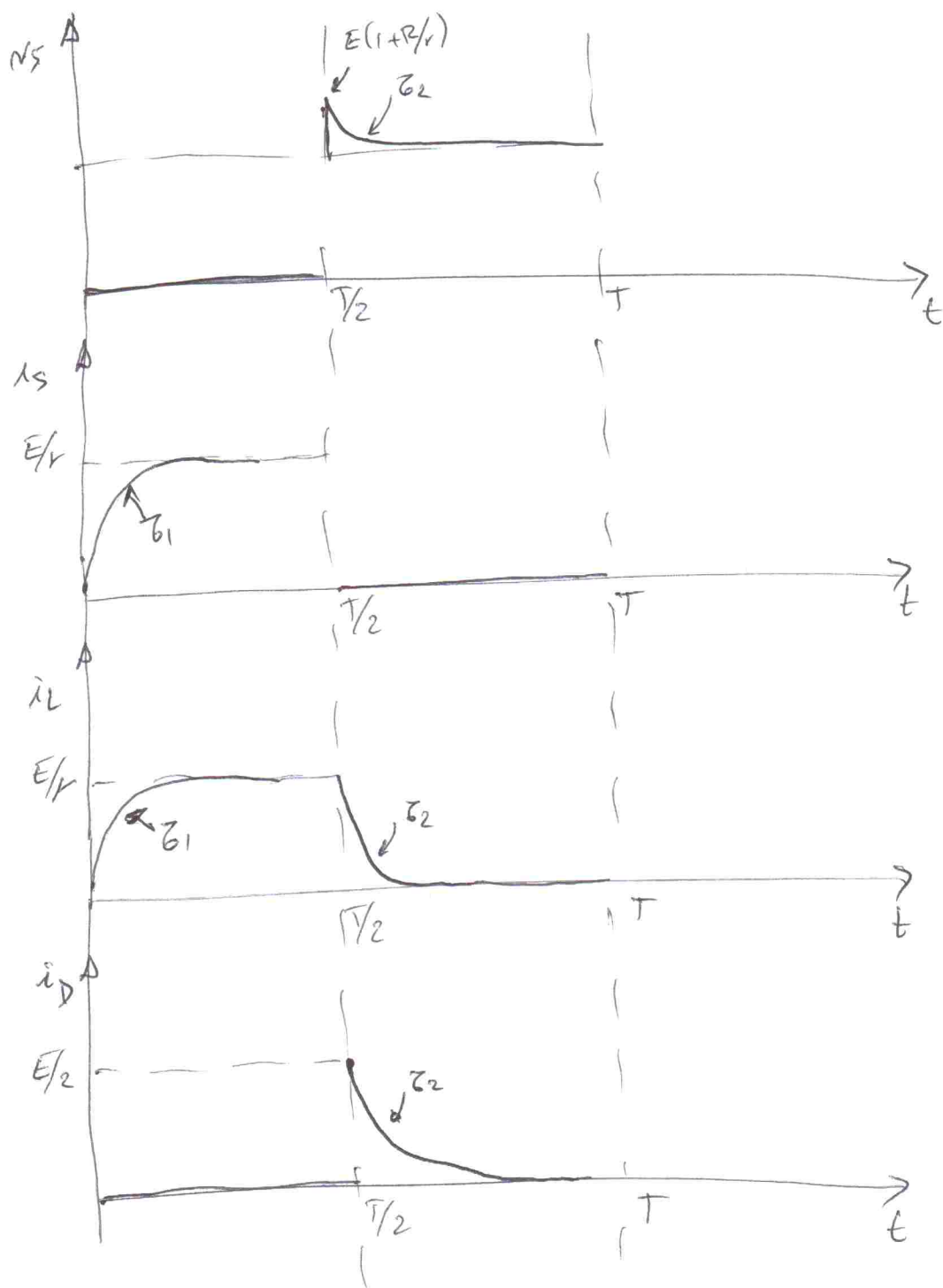

se vérifie $i_L(T^-) = i_L(0^-) = 0$ pues $\tau_2 \ll T/2$

$$2.b \quad E_L(T/2) = \frac{1}{2} L i_L^2(T/2) = \frac{1}{2} L \left[\frac{E}{r} \right]^2.$$

Problema 3

parte 3

a.
$$\left. \begin{aligned} P_D(t) &= V_D i_D(t) = 0 \\ P_S(t) &= V_S i_S(t) = 0 \end{aligned} \right\} \text{ pues siempre la corriente o la tensión es nula, } \forall t$$

$$\bar{P}_L = \frac{1}{T} \int_0^T N_L i_L dt = \frac{1}{2} \left. E_L(i_L) \right|_{i_L(0)}^{i_L(T)} = 0 \text{ por régimen periódico}$$

$\bar{P}_D = \bar{P}_S = 0$ pues $P_D(t) = P_S(t) = 0 \forall t$.

$$\begin{aligned} \bar{P}_R &= \frac{1}{T} \int_0^T R i_R^2 dt = \frac{1}{T} \int_{T/2}^T R i_D^2 dt = \frac{1}{T} R \int_{T/2}^T \left(\frac{E}{r}\right)^2 e^{2(t-T/2)/\tau_2} dt \\ &= \frac{R}{T} \frac{E^2}{r^2} e^{2t/\tau_2} \Big|_{T/2}^T = \frac{R E^2}{T r^2} \frac{\tau_2}{2} \text{ pues } \tau_2 \ll T/2 \end{aligned}$$

$$\boxed{\bar{P}_R = \frac{R}{R+r} \frac{L}{2} \frac{E^2}{r^2 T}}$$

b. Tellegen: $P_E(t) + P_R(t) + P_i(t) + P_L(t) + P_S(t) + P_D(t) = 0 \forall t$.

Dados P_D, P_S de la parte a: $P_E(t) + P_R(t) + P_i(t) + P_L(t) = 0 \forall t$

c. Cuando tomamos valores medios en un periodo:

$$\bar{P}_E + \bar{P}_R + \bar{P}_i + \bar{P}_L = 0 \Rightarrow \bar{P}_i = -\bar{P}_E - \bar{P}_R$$

$$\eta = \frac{\bar{P}_r}{\bar{P}_E} = \frac{\bar{P}_E + \bar{P}_R}{\bar{P}_E} = 1 + \frac{\bar{P}_R}{\bar{P}_E}$$

note que \bar{P}_E es negativo
pues $P_r \geq 0$
 $P_R \geq 0$