

1) a) $r \leq R$ Utilizo Gauss $\oint \vec{E} \cdot d\vec{s} = \frac{q_{enc}}{\epsilon_0}$

$$2\pi r L E_{in} = \frac{-\lambda L + \rho L \pi r^2}{\epsilon_0} \quad \therefore \quad \vec{E}_i = \left(\frac{\rho r}{2\epsilon_0} - \frac{\lambda}{2\pi r \epsilon_0} \right) \hat{e}_r$$

$r \geq R$

$$E_{out} = \left(\frac{\rho R^2}{2\epsilon_0 r} - \frac{\lambda}{2\pi \epsilon_0 r} \right) \hat{e}_r$$

b) ~~$r \leq R$~~ $\int_R^r dV = V(r) - V(R) = - \int_R^r \vec{E}_{in} \cdot d\vec{r} = - \left[\frac{\rho}{4\epsilon_0} (r^2 - R^2) + \frac{\lambda}{2\pi \epsilon_0} \ln\left(\frac{r}{R}\right) \right]$

~~$r \geq R$~~ $\int_R^r dV = V(r) - V(R) = - \int_R^r \vec{E}_{out} \cdot d\vec{r} = - \left(\frac{\rho R^2 \pi - \lambda}{2\pi \epsilon_0} \right) \ln\left(\frac{r}{R}\right)$

c) Esto se cumple si $\vec{E}_{in} = 0 \hat{e}_r$ si $r^* = \sqrt{\frac{\lambda}{\rho \pi}}$

Ademós $r^* \leq R \quad \therefore \quad R \geq \sqrt{\frac{\lambda}{\rho \pi}} \quad \therefore \quad \frac{\lambda}{\rho} \leq \pi R^2$

Solución problema 2; Examen F3 Julio 2017

a) Campo eléctrico entre placas de área A (Gauss): $AE = \frac{\pi D^2 E}{4} = q/\epsilon_0 \Rightarrow E = \frac{4q}{\pi \epsilon_0 D^2}$.

Flujo de E a través de un área interior de radio r : $\phi_E(r) = \pi r^2 E = \frac{4qr^2}{\epsilon_0 D^2} \Rightarrow \frac{d\phi_E}{dt} = \frac{4r^2}{\epsilon_0 D^2} i(t)$.

Ley de Ampère en ausencia de corriente: $\oint \vec{B} \cdot d\vec{S} = 2\pi r B = \mu_0 \epsilon_0 \frac{d\phi_E}{dt} \Rightarrow B(r) = \frac{2\mu_0}{\pi D^2} r i(t)$.

b) Capacitancia del capacitor: $C = \epsilon_0 A/d = \epsilon_0 \frac{\pi D^2}{4d}$.


Descarga de un condensador a través de una resistencia: $q(t) = Q_0 \exp(-t/\tau)$ con $\tau = RC$.

Corriente eléctrica en el circuito: $i(t) = \frac{dq}{dt} = -\frac{Q_0}{\tau} \exp(-t/\tau) \Rightarrow B(r, t) = | -\frac{2\mu_0 Q_0}{\pi D^2 \tau} r \exp(-t/\tau) |$,

explícitamente: $B(r, t) = \frac{8\mu_0 Q_0 d}{\pi^2 \epsilon_0 R D^4} r \exp(-\frac{4d}{\pi \epsilon_0 D^2 R} t)$

3

a)

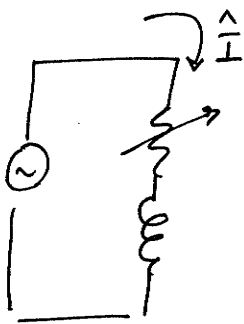

$$\hat{I}_{RMS} = \frac{V}{\sqrt{R^2 + X^2}}$$

$$\bar{P} = R \hat{I}_{RMS}^2 = V^2 \frac{R}{R^2 + X^2} \Rightarrow$$


$$\Rightarrow R^2 - \frac{V^2 R}{\bar{P}} + X^2 = 0 \Rightarrow$$

$$R_{\bar{P}_{min}} = \begin{cases} 112,5 \Omega \\ 450 \Omega \end{cases}$$

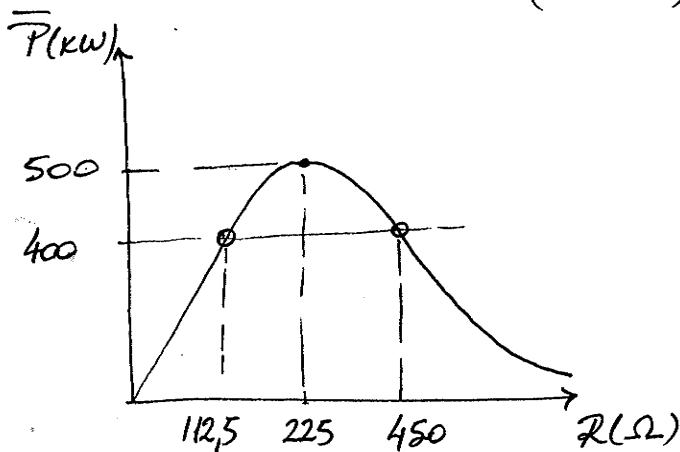b) Busco el máximo de $\bar{P}(R) = V^2 \frac{R}{R^2 + X^2}$:

$$\frac{\partial \bar{P}}{\partial R} = V^2 \frac{R^2 + X^2 - R \cdot 2R}{(R^2 + X^2)^2} = V^2 \frac{X^2 - R^2}{(R^2 + X^2)^2} = 0 \Leftrightarrow R_{\bar{P}_{max}} = X = 225 \Omega \Rightarrow$$

$$\Rightarrow \bar{P}_{max} = 500 \text{ kW}$$



$$c) \hat{V} = (R + jX) \hat{I} \Rightarrow \hat{I} = \frac{\hat{V}}{R + jX} = \frac{V}{\sqrt{R^2 + X^2}} \angle -\varphi = -\varphi$$

$$\underline{\bar{P}_{max}}: \hat{I}_{\bar{P}_{max}} = 47,1 \text{ A} \angle -45^\circ \quad (\cos \varphi = 1/\sqrt{2})$$

$\underline{\bar{P}_{min}}$: Si $R = 112,5 \Omega \Rightarrow \varphi = 63^\circ \Rightarrow \cos \varphi < 1/\sqrt{2} \Rightarrow$
 Descarto esa solución.

$$R = 450 \Omega \Rightarrow \hat{I}_{\bar{P}_{min}} = 29,8 \text{ A} \angle -27^\circ$$

$$(\cos \varphi \approx 0,9)$$

