

CALCULOS PARCIAL MAYO 2018:

Cable 30 kV 1x500 Al desde Mdeo Z:

$$Z_{Ld30} := (0.082 + 0.108i) \cdot 0.3$$

$$Z_{Ld30} = 0.025 + 0.032i \text{ ohm}$$

$$U := 31.5 \text{ kV}$$

$$X_{Fd} := \frac{U^2}{665} \cdot 1j \quad X_{Fd} = 1.492i \text{ ohm} \quad \text{Mdeo Z Pccmax} = 665 \text{ MVA}$$

$$I_{cc3F} := \frac{\frac{U}{\sqrt{3}}}{X_{Fd} + Z_{Ld30}} \quad |I_{cc3F}| = 11.928 \text{ kA}$$

Cable 30 kV 1x500 Al desde Mdeo C:

$$Z_{Ld30} := (0.082 + 0.108i) \cdot 4$$

$$Z_{Ld30} = 0.328 + 0.432i \text{ ohm}$$

$$U := 31.5 \text{ kV}$$

$$X_{Fd} := \frac{U^2}{1278} \cdot 1j \quad X_{Fd} = 0.776i \text{ ohm} \quad \text{Mdeo C Pccmax} = 1278 \text{ MVA}$$

$$I_{cc3F} := \frac{\frac{U}{\sqrt{3}}}{X_{Fd} + Z_{Ld30}} \quad |I_{cc3F}| = 14.524 \text{ kA}$$

... la maxima Icc trifasica es cuando se conecta la estacion desde Mdeo C

$$U := 6.4 \text{ kV}$$

$$X_{Td} := 0.12 \cdot \frac{U^2}{15} \cdot 1j \quad X_{Td} = 0.328i \text{ ohm} \quad X_{To} := X_{Td}$$

$$X_{Fd} := \frac{U^2}{1278} \cdot 1j \quad X_{Fd} = 0.032i \text{ ohm} \quad \text{Mdeo C Pccmax} = 1278 \text{ MVA}$$

Corriente maxima de cortocircuito 3-F en 6,4 kV : $Z_{Ld30} = 0.328 + 0.432i$ (desde Mdeo C)

$$Z_{Ld} := Z_{Ld30} \cdot \left(\frac{6.4}{31.5} \right)^2 \quad Z_{Ld} = 0.014 + 0.018i$$

$$I_{cc3F} := \frac{\frac{U}{\sqrt{3}}}{X_{Fd} + Z_{Ld} + \frac{X_{Td}}{2}} \quad |I_{cc3F}| = 17.254 \text{ kA}$$

Corriente maxima de cada transformador (para eleccion de corriente nominal de interruptores):

$$I_{30} := \frac{15}{\sqrt{3} \cdot 31.5} \cdot 1.33 \quad I_{30} = 0.366 \text{ kA}$$

$$I_{int_1y2} := 2 \cdot I_{30} = 0.731 \text{ kA} \quad I_{int_3_4y5} := I_{30} = 0.366 \text{ kA}$$

$$I_{int_6} := 415 \cdot 1.2 = 498 \text{ kA}$$

Interruptor N°	Tensión nominal (kV)	Corriente nominal (A)	Poder de corte/corriente limite térmica (3 seg) (kA)	Corriente limite dinámica (kAcr)
1	36	800	12,5	31.5
2	36	800	16	40
3	36	630	16	40
4	36	630	16	40
5	36	630	16	40
6	12	630	20	50